

**R18**

CodeNo:151AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

**B.Tech I Year I Semester Examinations, May/June -  
2019 BASIC ELECTRICAL ENGINEERING  
(Common to EEE, CSE, IT)**

**Time:3 hours Max.Marks:75****Note:**This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.


**PART-A****(25Marks)**

- State Thevenin's theorem. [2]
- What is meant by apparent power? [2]
- Why the copper losses are more in a transformer? [2]
- What is necessity of rotating magnetic field in the induction motor? [2]
- What is the difference between fuse unit and switch fuse unit? [2]
- What is meant by capacitor charging current, obtain its expression in terms of time constant in case of R-C circuit? [3]
- An alternating voltage  $e = 300 \sin(\omega t + \frac{\pi}{4})$ , what is its instantaneous voltage at  $t = 1$  ms and 10 ms for 50 Hz frequency? [3]
- What is the difference between ideal transformer and practical transformer? [3]
- What are the advantages of armature winding placing in its stator? [3]
- What are the characteristics of batteries for longer life? [3]

**PART-B****(50Marks)**


2.a)

State Kirchhoff Current Law and Voltage law, determine the values for  $I_x$  and  $V_y$  in the following given circuit shown in figure 1.

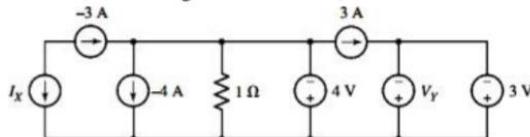**Figure:1**


- b) In the following given circuit shown in figure 2, calculate i)  $v_1$ ,  $v_2$  and  $v_3$  delivered to  $R_1$ ,  $R_2$  and  $R_3$ .

[5+5]

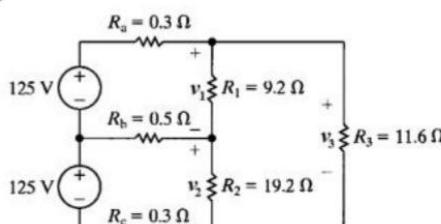
**Figure: 2**

**Figure:1**

- b) In the following given circuit shown in figure 2, calculate i)  $v_1$ ,  $v_2$  and  $v_3$  delivered to  $R_1$ ,  $R_2$  and  $R_3$ . ii) power [5+5]

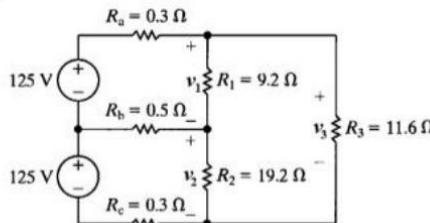**Figure: 2**

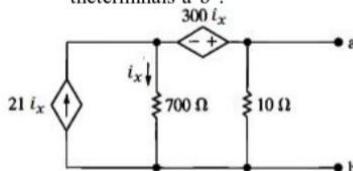- 3.a) Find the Norton equivalent circuit of the following given circuit shown in figure 3 with respect to the terminals 'a-b'?



OR

- b) State and explain superposition theorem.

[5+5]

- 4.a) Describe phasor representation of RL series circuit? If admittance of a series circuit is  $(0.010 + j0.004)$  S. Determine the values of the circuit components for the frequency value of 50 Hz?  
 b) Balanced Y-connected load of 10 kW at 0.8 power factor lagging supplied by a 50-Hz, 300-V, three-phase system. Find the line current delivered by the source. Draw the phasor diagram. [5+5]

OR

- 5.a) Explain how the sinusoidal waveform is represented as phasor quantity with example.  
 b) A coil is connected in series with a capacitor of  $20\text{ }\mu\text{F}$  to a 200 V variable frequency supply. The current is a maximum at 50 A, when the frequency is set to 50 Hz. Determine the resistance and inductance of the coil. [5+5]

- 6.a) Draw and explain the phasor diagram of single phase transformer on lagging load.

- b) A 50kVA, 1000/10000V, 50Hz single phase transformer has iron loss of 1200W. The copper loss with 5A in the high voltage winding is 500W. Calculate the efficiency at  
 i) 25%, ii) 50% iii) 100% of normal load at power factor of 0.8. [5+5]

OR

7.a)

Describe the principle of operation of autotransformer, what is the saving of copper in this transformer when compared with two winding transformer?

- b) Discuss the various three phase transformer groups and their significance? [5+5]

- 8.a) Describe the constructional details of three phase slip ring induction motor.

- b) Describe the torque speed characteristics of separately excited dc motor. [5+5]

OR

- 9.a) What are the various losses occurring in the three phase induction motor in its operation?

- b) Describe briefly construction details of any three phase synchronous generator? [5+5]

- 10.a) Describe the operation of ELCB with its schematic diagram.

- b) What are the drawbacks of low power factor, describe how it is improved? [5+5]

OR

- 11.a) What is the difference between MCB and MCCB, describe their schematic diagrams?

- b) Calculate total energy consumed per day by the use of following loads:

- i) 5 number of 40W lights operated 5 hours per day

- ii) 1h.p. motor is operated 2 hours per day

- iii) 1k.W heater is operated 1 hour per day

- iv) 1 computer is used for 6 hours per day with printer about 30 minutes. [5+5]



- i) Number of 40W lights operated 5 hours per day
- ii) 1 h.p. motor is operated 2 hours per day
- iii) 1k.Wheater is operated 1 hour per day
- iv) 1 computer is used for 6 hours per day with printer about 30 minutes. [5+5]

**Code No: 151AG R18**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B.Tech I Year I Semester Examinations, July - 2021**

**BASIC ELECTRICAL ENGINEERING**

(Common to EEE, CSE, IT, CSIT, ITE, CE(SE), CSE(CS), CSE(DS), CSE(Networks))

**Time: 3 hours**


**Max. Marks: 75**

**Answer any five questions**

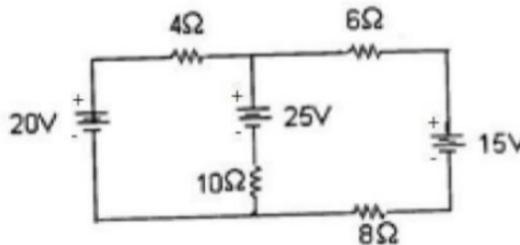**All questions carry equal marks**

---

- State and explain the Kirchhoff's laws.
- By applying Kirchhoff's laws, determine the current through all the elements in the circuit as shown in the figure 1.




[6+9]

**Figure: 1**

- State and explain Thevenin's theorem.

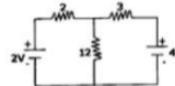- Using superposition theorem, determine the current through 3 ohm resistor shown in following figure 2 (All resistance are in ohms).



[7+8]

**Figure: 2**

- Define the following terms:

- Cycle ii) Amplitude iii) R.M.S value and iv) Average value of an alternating quantity.
- A coil having a resistance of 10 ohms and an inductance of 0.2H is connected in series with a  $100 \times 10^{-6}$  F capacitor across a 230V, 50Hz, determine i) The active and reactive components of the current and power. ii) The voltage across the coil, Draw the phasor diagram.

[6+9]

- What are the advantages of polyphase system?

- Determine the line and phase current of the load, when a delta connected balanced load with an impedance of  $(25+j15)$  ohms is connected to 230V, three phase balanced supply in positive sequence.

[6+9]

- Develop the equivalent circuit of a single phase transformer.

- A 220/440 V single phase transformer has 1000 turns on primary. The maximum flux density in the core is 1.2 Wb/m<sup>2</sup>. Calculate the number of turns on secondary, area of cross section and maximum flux in the core.

[6+9]

- Explain the different 3-phase transformers connections with neat diagram.

- The core of a 100 kVA, 11000/550V, 50 Hz, single phase core type transformer has a cross section of 20cm × 20 cm. Determine i) the number of H.V. and L.V. turns per phase and ii) the e.m.f. per turn, if the maximum core density is 1.3 tesla.

[8+7]

- Explain the speed control of 3-phase induction motor.

- A 6-pole, 100 HP, 3-phase, 440-V, 50Hz induction motor has a slip of 5% on full load. Calculate the speed of the motor?

[9+6]

- Describe the miniature circuit breaker with neat diagrams.

- Explain different types of wires used in electrical wiring.

[7+8]

