



Your roots to success...

NARSIMHA REDDY ENGINEERING COLLEGE
UGC-AUTONOMOUS INSTITUTION

An Autonomous Institute
NAAC Accreditation 'A' Grade
Accredited by NBA
Approved by AICTE, Affiliated to JNTUH

UNIT-III

DC-DC Converters


(Chopper/SMPS)

Prepared by
Ch. Prasanna.
Assistant Professor, EEE

DC-DC Converters


- Convert a fixed DC Source into a Variable DC Source
- DC equivalent to an AC transformer with variable turns ratio
- Step-up and Step-down versions
- Applications
 - Motor Control
 - Voltage Regulators

Step-down Operation

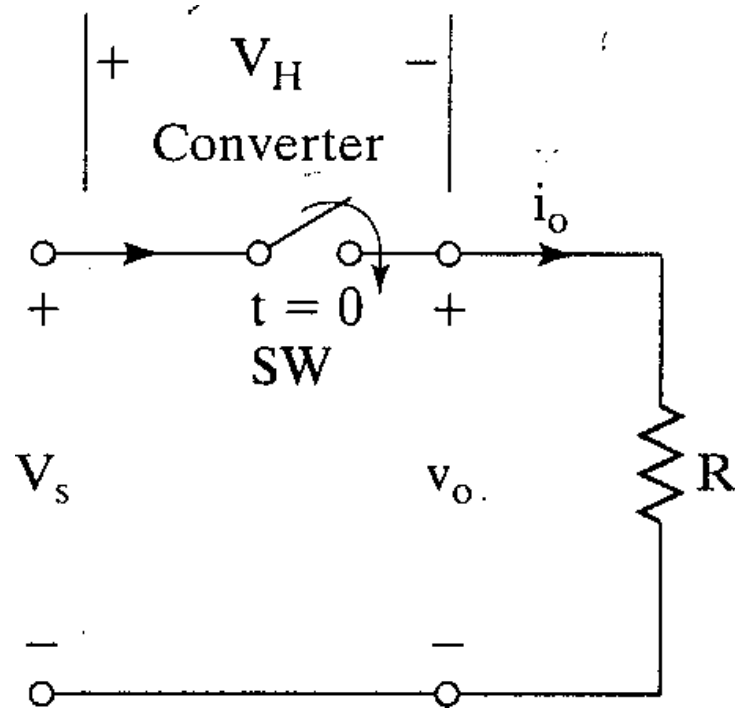


- Switch SW is known as a “Chopper”
- Use BJT, MOSFET, or IGBT
- Close for time t_1
 - V_s appears across R
- Open for time t_2
 - Voltage across $R = 0$
- Repeat
- Period $T = t_1 + t_2$

Waveforms for the Step-Down Converter

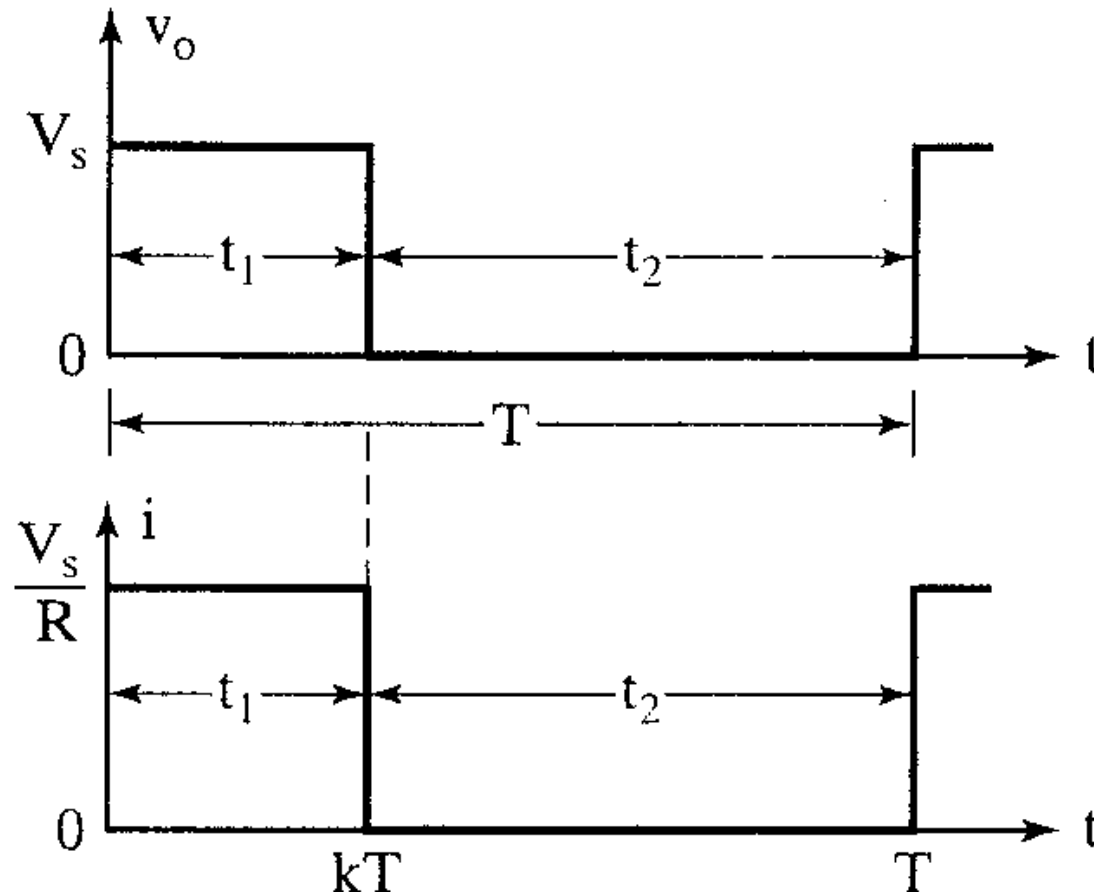

Average Value of the Output Voltage

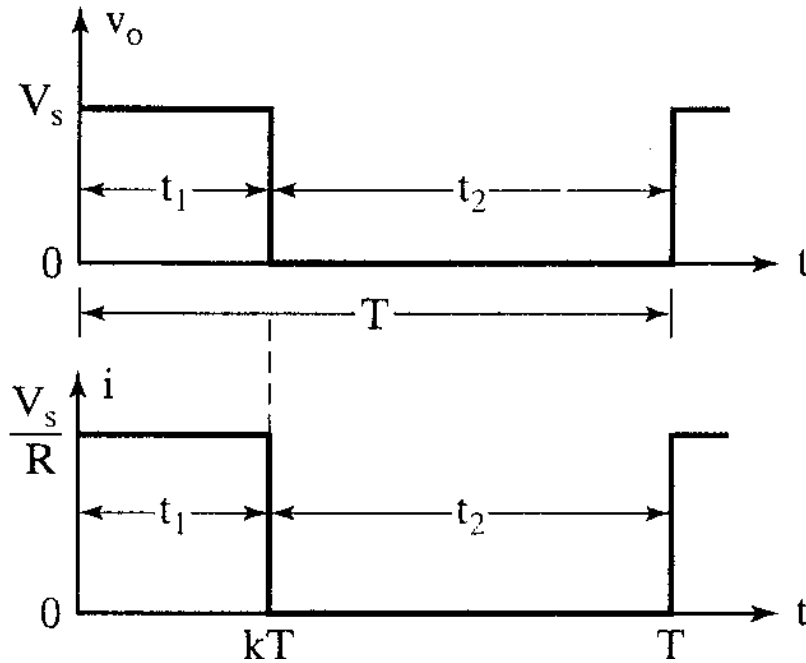

$$V_a = \frac{1}{T} \int_0^{t_1} v_o dt$$

$$V_a = \frac{1}{T} \int_0^{t_1} V_s dt$$

$$V_a = \frac{t_1}{T} V_s = f t_1 V_s$$

$$V_a = k V_s$$

Average Value of the Load Current

$$I_a = \frac{V_a}{R} = \frac{kV_s}{R}$$

$T = \textit{period}$

$k = \frac{t_1}{T} = \textit{dutycycle}$

$f = \textit{frequency}$

rms Value of the output voltage

$$V_o = \left(\frac{1}{T} \int_0^{kT} v_o^2 dt \right)^{\frac{1}{2}}$$

$$V_o = \left(\frac{1}{T} \int_0^{kT} V_s^2 dt \right)^{\frac{1}{2}}$$

$$V_o = \sqrt{k} V_s$$

If the converter is “lossless”, $P_{in} = P_{out}$

$$P_{in} = \frac{1}{T} \int_0^{kT} v_o i dt$$

$$P_{in} = \frac{1}{T} \int_0^{kT} \frac{v^2}{R} dt$$


$$P_{in} = \frac{1}{T} \frac{V_s^2}{R} kT$$

$$P_{in} = k \frac{V_s^2}{R}$$

Effective Input Resistance seen by V_S

$$R_i = \frac{V_S}{I_a} = \frac{V_S}{k \frac{V_S}{R}}$$

$$R_i = \frac{R}{k}$$

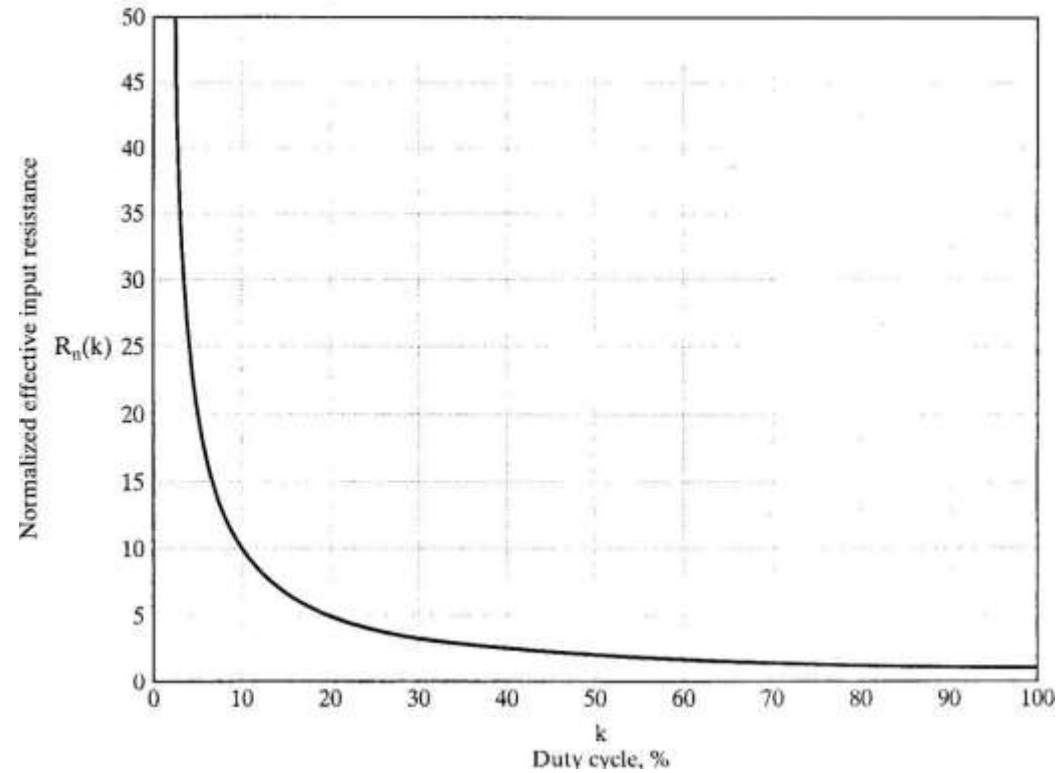


Modes of Operation


- Constant – frequency operation
 - Period T held constant, t_1 varied
 - Width of the pulse changes
 - “Pulse-width modulation”, PWM
- Variable -- frequency operation
 - Change the chopping frequency (period T)
 - Either t_1 or t_2 is kept constant
 - “Frequency modulation”

Generation of Duty Cycle

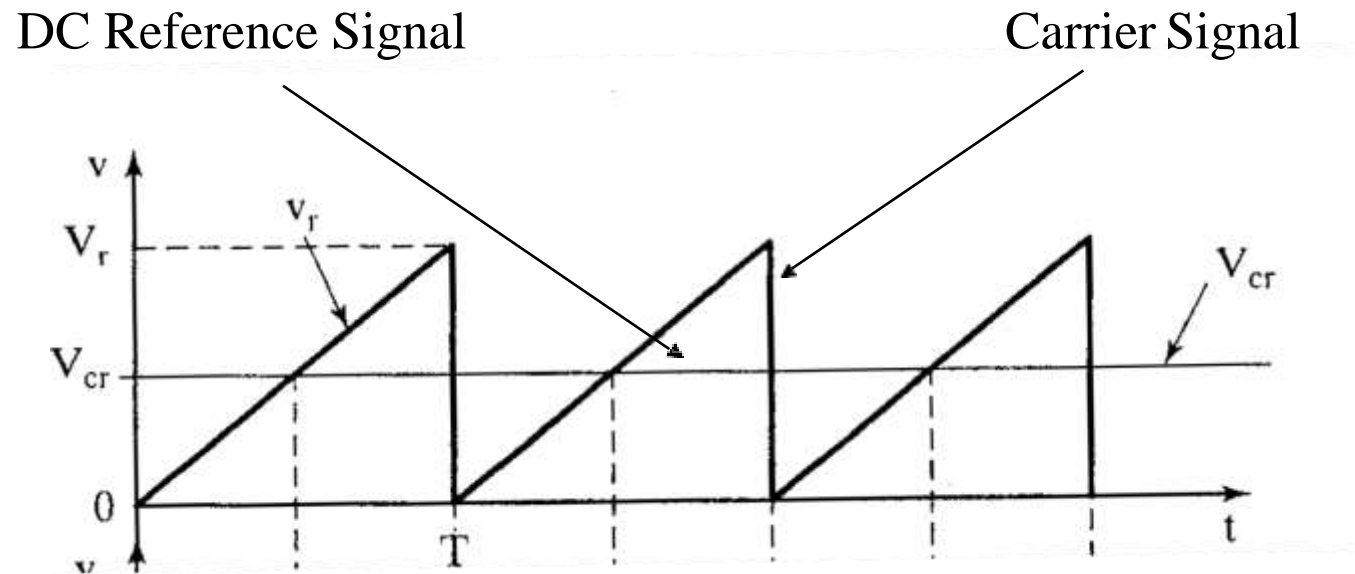- Compare a dc reference signal with a saw-tooth carrier signal



$$v_r = \frac{V_r}{T} k$$

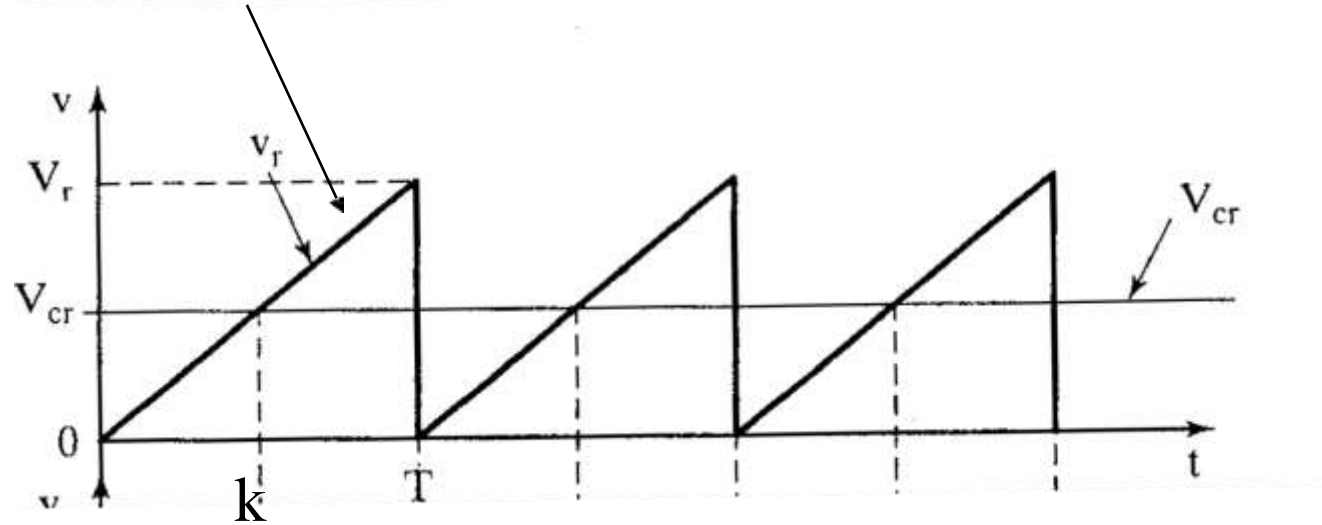


$$T \quad v_r = V_{cr} @ t = kT$$

$$V_{cr} = \frac{V_r}{T} kT$$


$$k = \frac{V_{cr}}{V_r} = M$$

To generate the gating signal

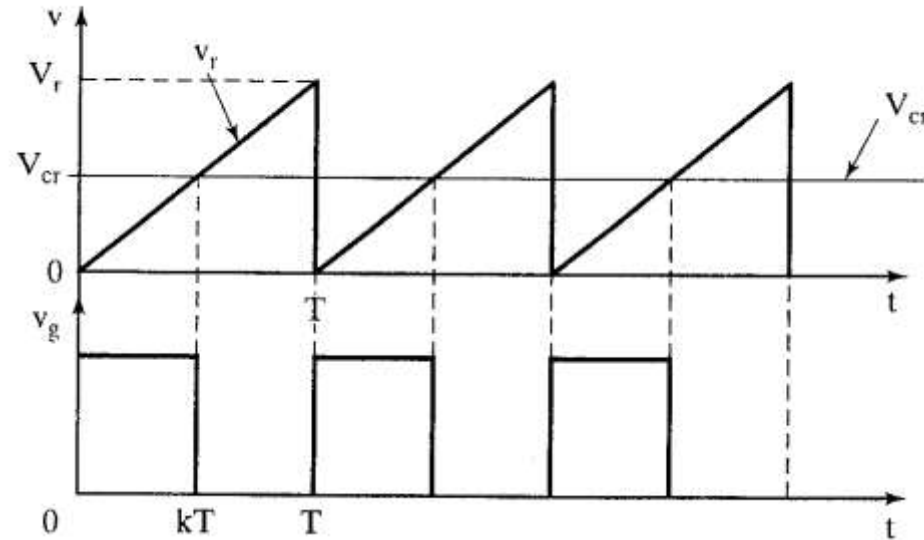


- Generate the triangular waveform of period T , v_r , and the dc carrier signal, v_{cr}
- Compare to generate the difference $v_c - v_{cr}$
- Apply to a “hard limiter” to “square off”

Step-Down Converter with RL Load

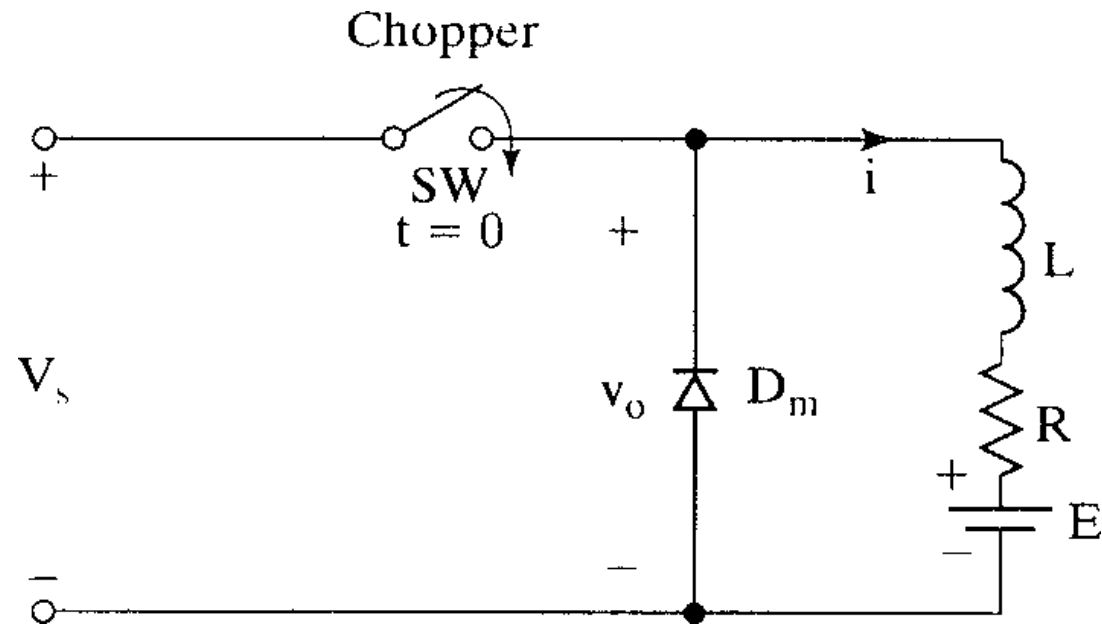

Mode 1: Switch Closed

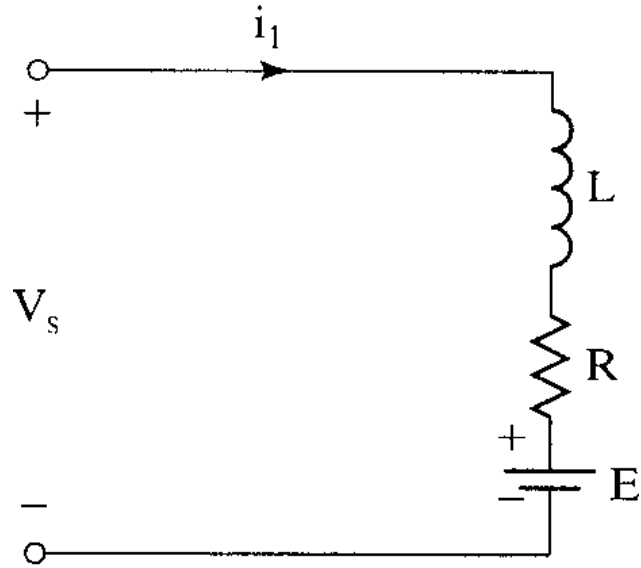

$$V_s = Ri_1 + L \frac{di_1}{dt} + E$$

$$i_1(t) \Big|_{(t=0)} = I_1$$


Mode 1

$$i_1(t) = I_1 e^{-\frac{R}{L}t} + \frac{V_s - E}{R} \left(1 - e^{-\frac{R}{L}t} \right) \quad t \leq t_1(kT)$$

$$t = t_1 = kT$$

$$i_1(kT) = I_2$$

Mode 2: Switch Open

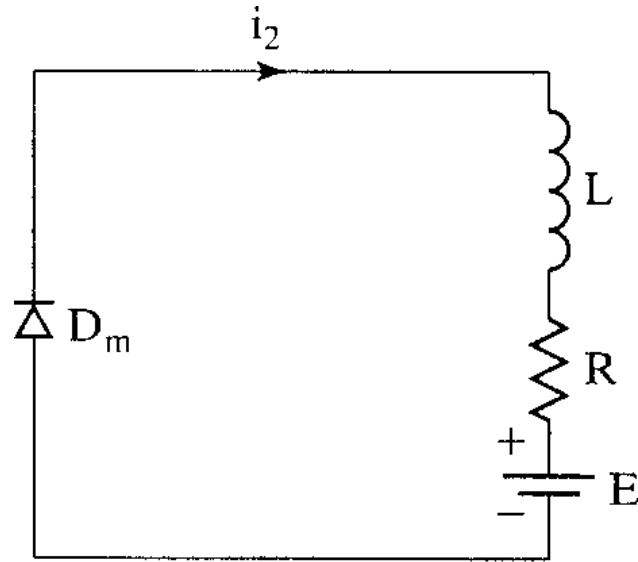

Mode 2

$$0 = Ri_2 + L \frac{di_2}{dt} + E$$

$$i_2(t = 0) = I_2$$


$$i_2(t) = I_2 e^{-\frac{Rt}{L}} - \frac{E}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$0 \leq t \leq t_2 = (1 - k)T$$

$$@t = t_2 = (1 - K)T$$

$$i_2(t) = I_2 = I_3 = I_1$$

Current for “Continuous” Mode

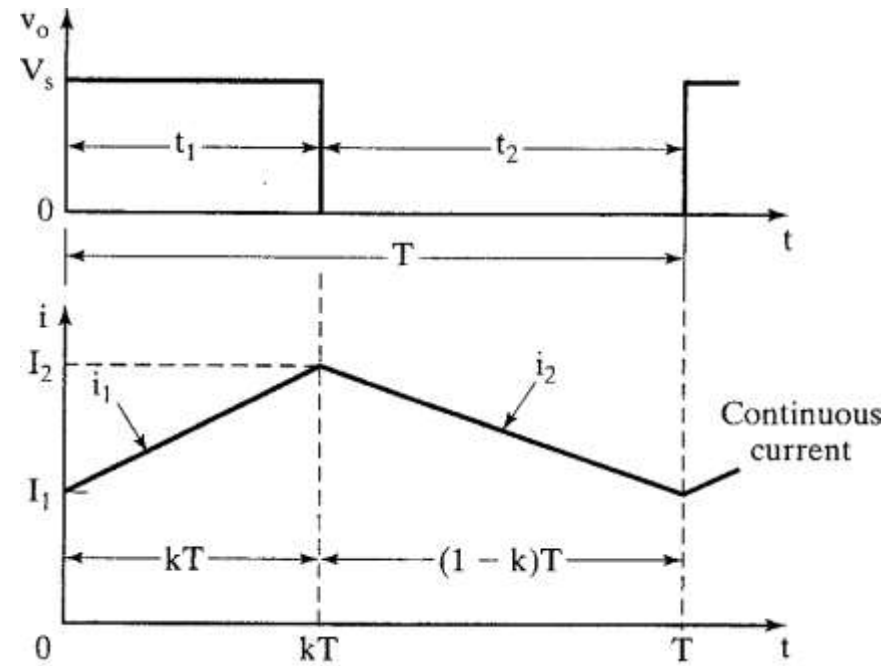

$$I_1 = \frac{V_s}{R} \left(\frac{e^{kz} - 1}{e^z - 1} \right) - \frac{E}{R}$$

$$I_2 = \frac{V_s}{R} \left(\frac{e^{-kz} - 1}{e^z - 1} \right) - \frac{E}{R}$$

$$z = \frac{TR}{L}$$

$$\Delta I = \frac{V_s}{R} \left[\frac{1 - e^{-kz} + e^{-z} - e^{-(1-k)z}}{1 - e^{-z}} \right]$$

$$\Delta I_{\max} \cong \frac{V_s}{4fL}$$

For Continuous Current

$$I_1 \geq 0$$


$$\left[\frac{e^{kz} - 1}{e^z - 1} - \frac{E}{V_s} \right] \geq 0$$

Define the load emf ratio


$$x = \frac{E}{V_s}$$

$$x = \frac{E}{V_s} \leq \frac{e^{kz} - 1}{e^z - 1}$$


Boost converter operation

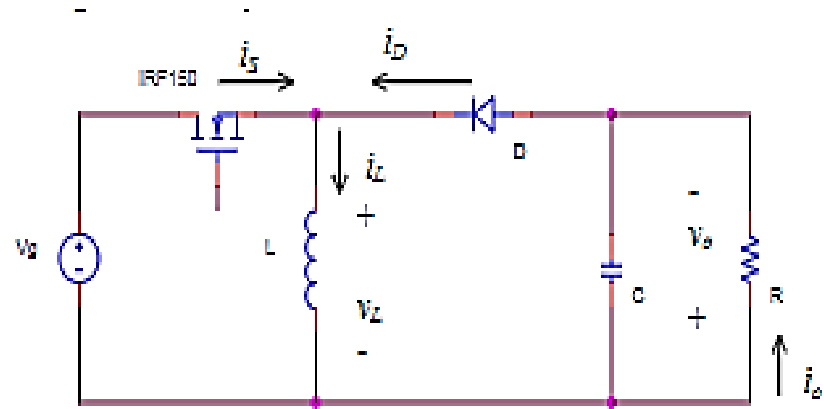


(a)

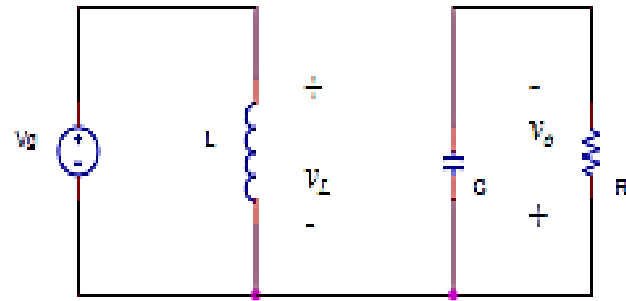


(b)

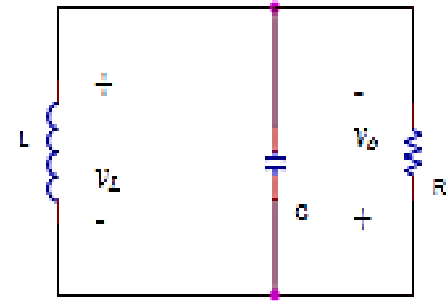


(c)

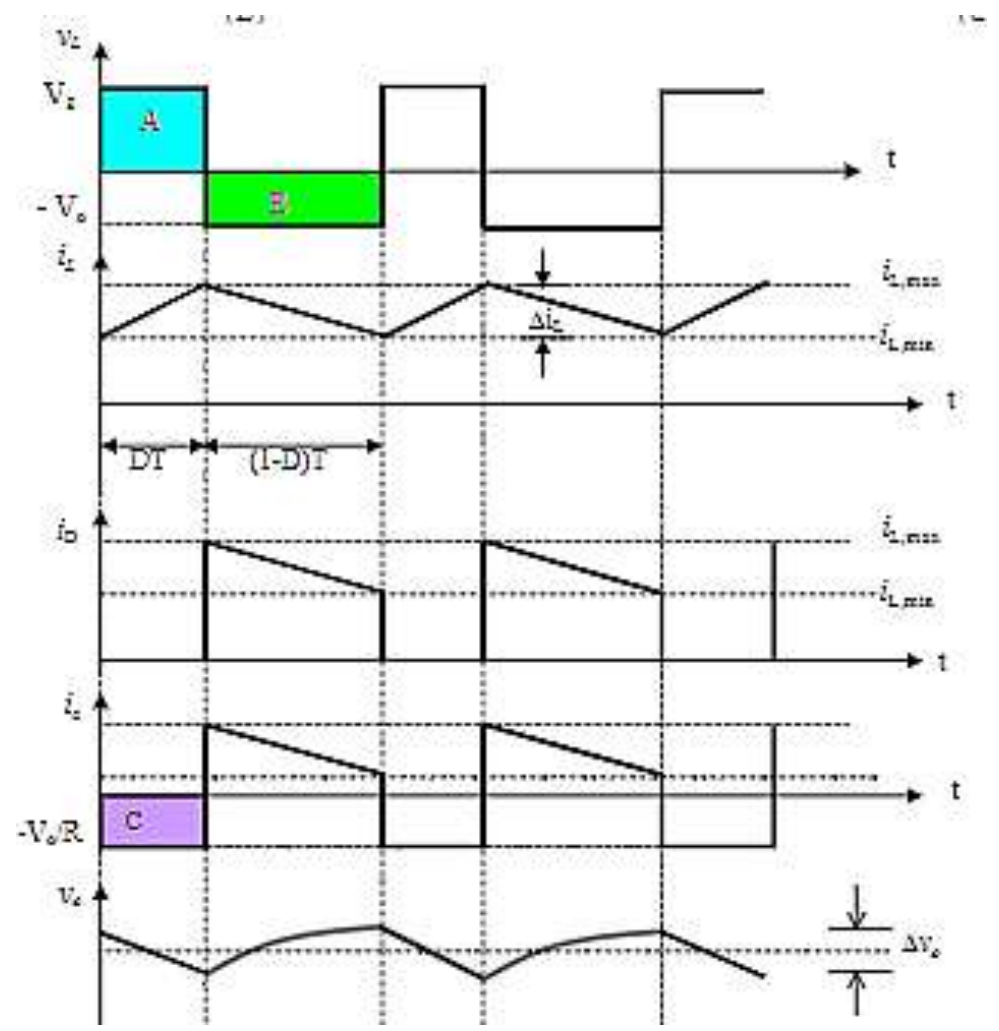


Step Up/ Step Down Chopper

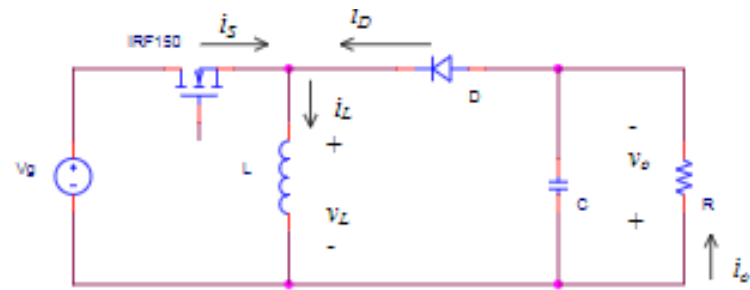

(a)

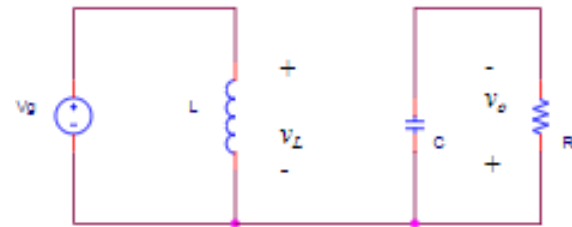

(b)

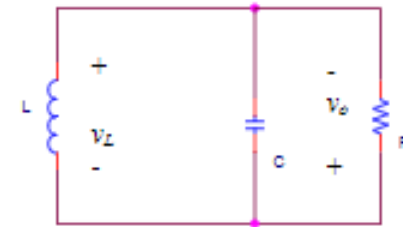

(c)

Step Down Chopper

