



Your roots to success...

**NARSIMHA REDDY ENGINEERING COLLEGE**  
**UGC-AUTONOMOUS INSTITUTION**

An Autonomous Institute  
NAAC Accreditation 'A' Grade  
Accredited by NBA  
Approved by AICTE, Affiliated to JNTUH


# **UNIT-V**

## **AC-AC Converters**

Prepared by  
Ch. Prasanna.  
Assistant Professor, EEE
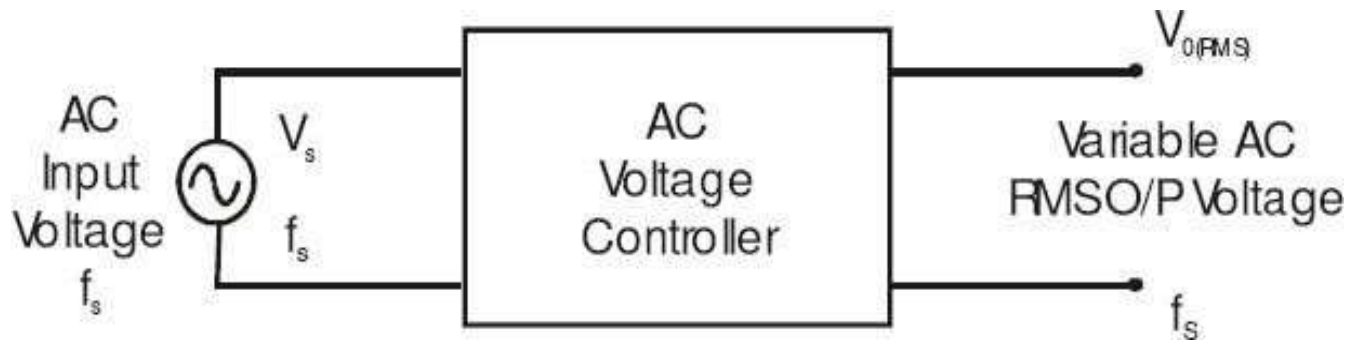
# Ac Voltage controller circuits (RMS voltage controllers)

An ac voltage controller is a type of thyristor power converter which is used to convert a fixed voltage, fixed frequency ac input supply to obtain a variable voltage ac output



# Applications Of Ac Voltage Controllers

- Lighting / Illumination control in ac power circuits.
- Induction heating.
- Industrial heating & Domestic heating.
- Transformer tap changing (on load transformer tap changing).
- Speed control of induction motors C magnet controls.


# Type Of Ac Voltage Controllers

- Single phase half wave ac voltage controller (Uni-directional controller).
- Single phase full wave ac voltage controller (Bi-directional controller).
- Three phase half wave ac voltage controller (Uni-directional controller).
- Three phase full wave ac voltage controller (Bi-directional Controller)


# A.C voltage control technique

- On-Off control.
- Phase control.

# Principle of ON-OFF Control Technique

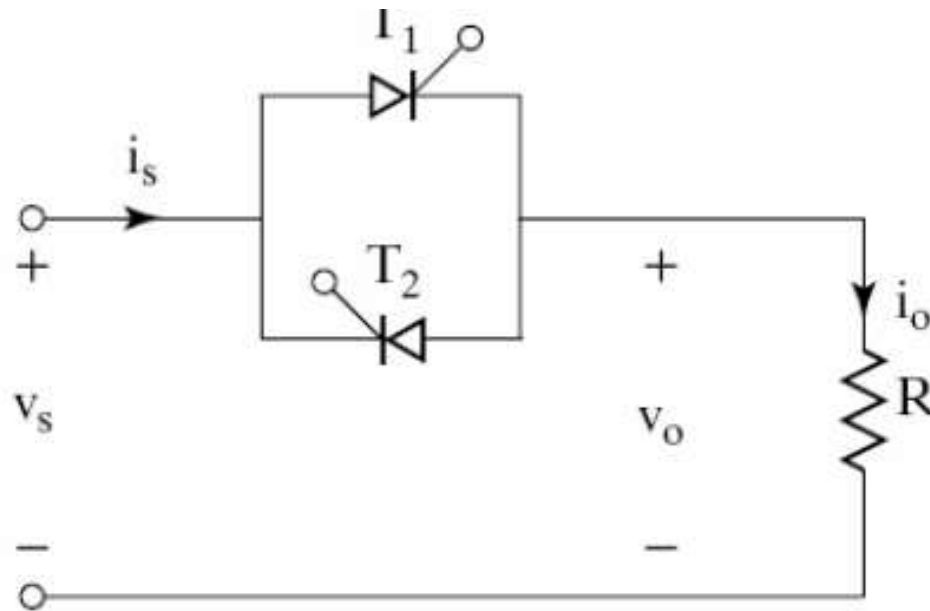

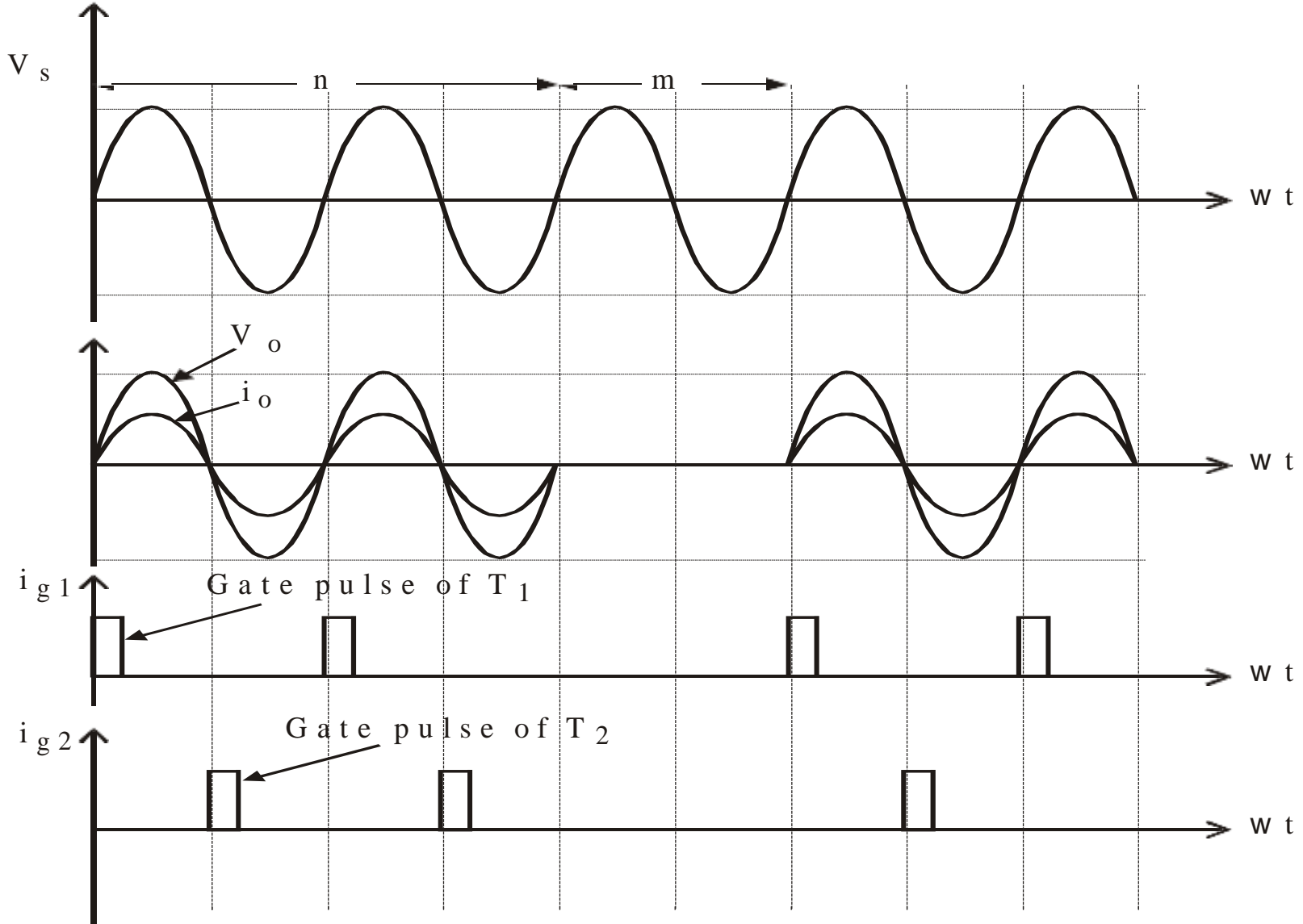**Single phase full wave AC voltage controller circuit**



For a sine wave i/p ac supply

$$v_s = V_m \sin \omega t = \sqrt{2}V_s \sin \omega t$$

$$V_s = \frac{V_m}{\sqrt{2}} = \text{RMS value of i/p ac supply}$$

$$t_{ON} = n \times T, \quad t_{OFF} = m \times T$$

$n$  = no. of i/p cycles during on time  $t_{ON}$

$m$  = no. of i/p cycles during off time  $t_{OFF}$

$$T = \frac{1}{f} = \text{input cycle time (time period)}$$

$f$  = input supply frequency.

$$t_{ON} = \text{controller on time} = n \times T$$

$$t_{OFF} = \text{controller off time} = m \times T$$

$$T_o = \text{Output time period}$$

$$= (t_{ON} + t_{OFF}) = (nT + mT)$$

For on-off control method

$$V_{O(RMS)} = V_{i(RMS)} \sqrt{\frac{t_{ON}}{T_o}} = V_S \sqrt{\frac{t_{ON}}{T_o}}$$

# Expression For The RMS Value Of Output Voltage, For ON-OFF Control Method

$$V_{O(RMS)} = \sqrt{\frac{1}{\omega T_o} \int_{\omega t=0}^{\omega t_{ON}} V_m^2 \sin^2 \omega t \cdot d(\omega t)}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{\omega T_o} \int_0^{\omega t_{ON}} \sin^2 \omega t \cdot d(\omega t)}$$

Substituting for  $\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{\omega T_o} \int_0^{\omega t_{ON}} \left[ \frac{1 - \cos 2\omega t}{2} \right] d(\omega t)}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\omega T_o} \left[ \int_0^{\omega t_{ON}} d(\omega t) - \int_0^{\omega t_{ON}} \text{Cos}2\omega t.d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\omega T_o} \left[ \frac{(\omega t)}{0} \Big|_0^{\omega t_{ON}} - \frac{\text{Sin}2\omega t}{2} \Big|_0^{\omega t_{ON}} \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\omega T_o} \left[ (\omega t_{ON} - 0) - \frac{\text{sin}2\omega t_{ON} - \text{sin}0}{2} \right]}$$

Here in this case,

$t_{ON}$  = An integral number of  
input cycles; Hence

$$t_{ON} = T, 2T, 3T, 4T, 5T, \dots \quad \&$$

$$\omega t_{ON} = 2\pi, 4\pi, 6\pi, 8\pi, 10\pi, \dots$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2 \omega t_{ON}}{2 \omega T_o}} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{t_{ON}}{T_o}}$$

$$V_{O(RMS)} = V_{i(RMS)} \sqrt{\frac{t_{ON}}{T_o}} = V_S \sqrt{\frac{t_{ON}}{T_o}}$$

Where  $V_{i(RMS)} = \frac{V_m}{\sqrt{2}} = V_S$

$$\begin{aligned}\frac{t_{ON}}{T_O} &= \frac{t_{ON}}{t_{ON} + t_{OFF}} \\ &= \frac{nT}{nT + mT} = \frac{n}{(n + m)} = k\end{aligned}$$

$$V_{O(RMS)} = V_S \sqrt{\frac{n}{(m + n)}} = V_S \sqrt{k}$$

# RMS Out put voltage

$$V_{O(RMS)} = \left[ \frac{n}{2\pi(n+m)} \int_0^{2\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{1/2}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{n}{(m+n)}} = V_{i(RMS)} \sqrt{k} = V_S \sqrt{k}$$

$$V_{O(RMS)} = V_{i(RMS)} \sqrt{k} = V_S \sqrt{k}$$

# Duty cycle

$$k = \frac{t_{ON}}{T_o} = \frac{t_{ON}}{(t_{ON} + t_{OFF})} = \frac{nT}{(m+n)T}$$

$$k = \frac{n}{(m+n)}$$

## RMS Load Current

$$I_{O(RMS)} = \frac{V_{O(RMS)}}{Z} = \frac{V_{O(RMS)}}{R_L}$$

## Output AC (Load) Power

$$P_O = I_{O(RMS)}^2 \times R_L$$

# Input Power factor

$$PF = \frac{P_o}{VA} = \frac{\text{output load power}}{\text{input supply volt amperes}} = \frac{P_o}{V_s I_s}$$

$$PF = \frac{I_{O(RMS)}^2 \times R_L}{V_{i(RMS)} \times I_{in(RMS)}}$$

$$I_s = I_{in(RMS)} = \text{RMS input supply current.}$$


$$= \text{same as RMS load current } I_{O(RMS)}$$

$$\begin{aligned}
 PF &= \frac{I_{O(RMS)}^2 \times R_L}{V_{i(RMS)} \times I_{in(RMS)}} = \frac{V_{O(RMS)}}{V_{i(RMS)}} \\
 &= \frac{V_{i(RMS)} \sqrt{k}}{V_{i(RMS)}} = \sqrt{k}
 \end{aligned}$$

$$PF = \sqrt{k} = \sqrt{\frac{n}{m+n}}$$


# The Average Current Of Thyristor

Waveform of Thyristor Current

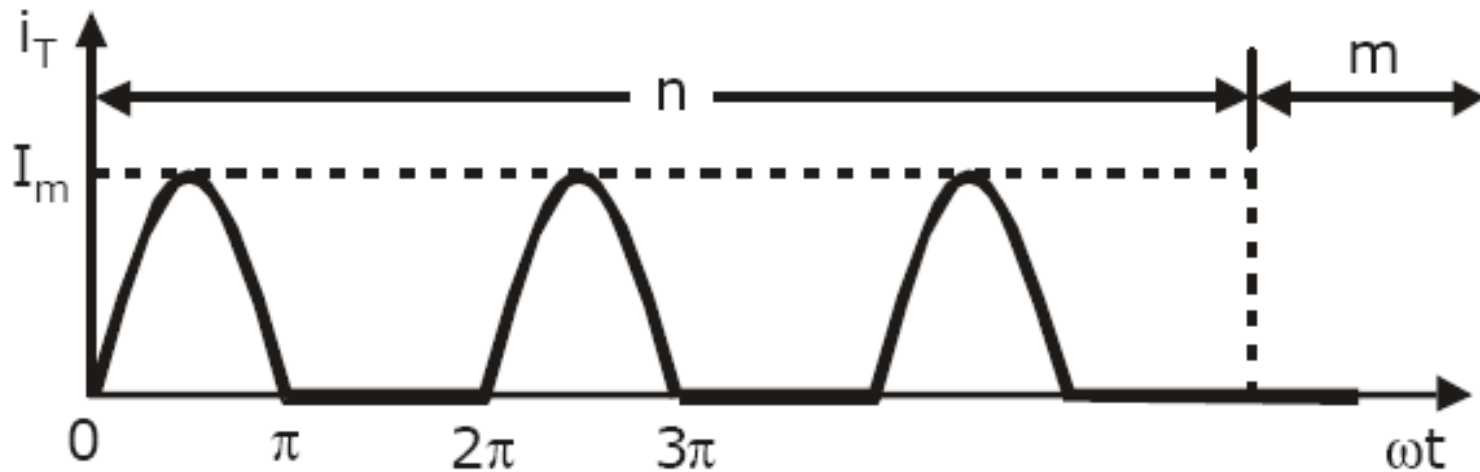

$$I_m = \frac{V_m}{R_L} = \text{max. or peak thyristor current}$$

# Waveform of Thyristor current

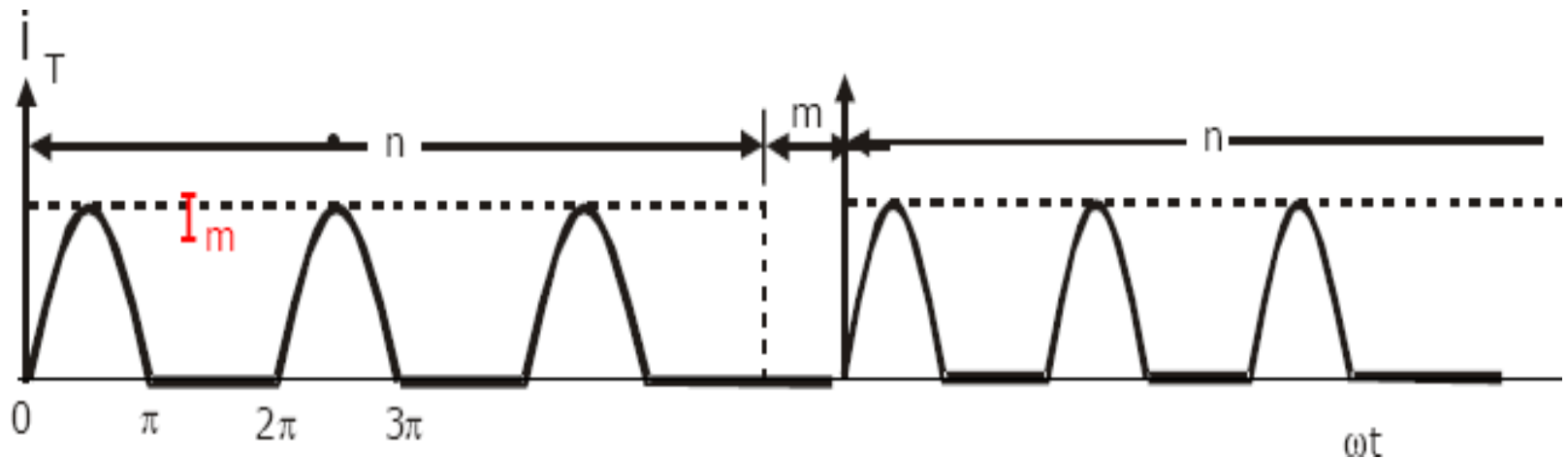

$$I_{T(Avg)} = \frac{n}{2\pi(m+n)} \int_0^{\pi} I_m \sin \omega t \cdot d(\omega t)$$

$$I_{T(Avg)} = \left( \frac{I_m}{\pi} \right) \frac{n}{(n+m)}$$

$$I_{T(Avg)} = \left( \frac{I_m}{\pi} \right) k$$

# RMS Thyristor Current


$$I_{T(RMS)} = \left[ \frac{n}{2\pi(n+m)} \int_0^{\pi} I_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{1/2}$$

$$I_{T(RMS)} = \frac{I_m}{2} \sqrt{\frac{n}{(m+n)}} = \frac{I_m}{2} \sqrt{k}$$


$$I_{T(RMS)} = \frac{I_m}{2} \sqrt{k}$$

Principle Of AC Phase Control  
And  
Operation of single Phase half-Wave  
A.C Phase controller

# Principle Of AC Phase Control

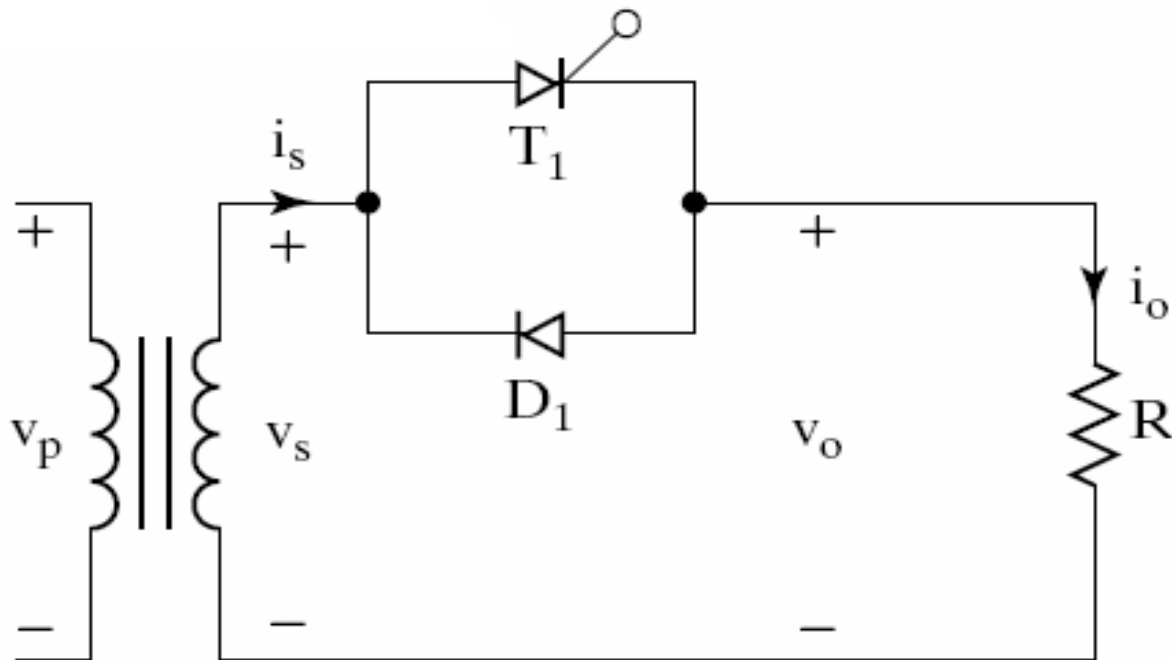

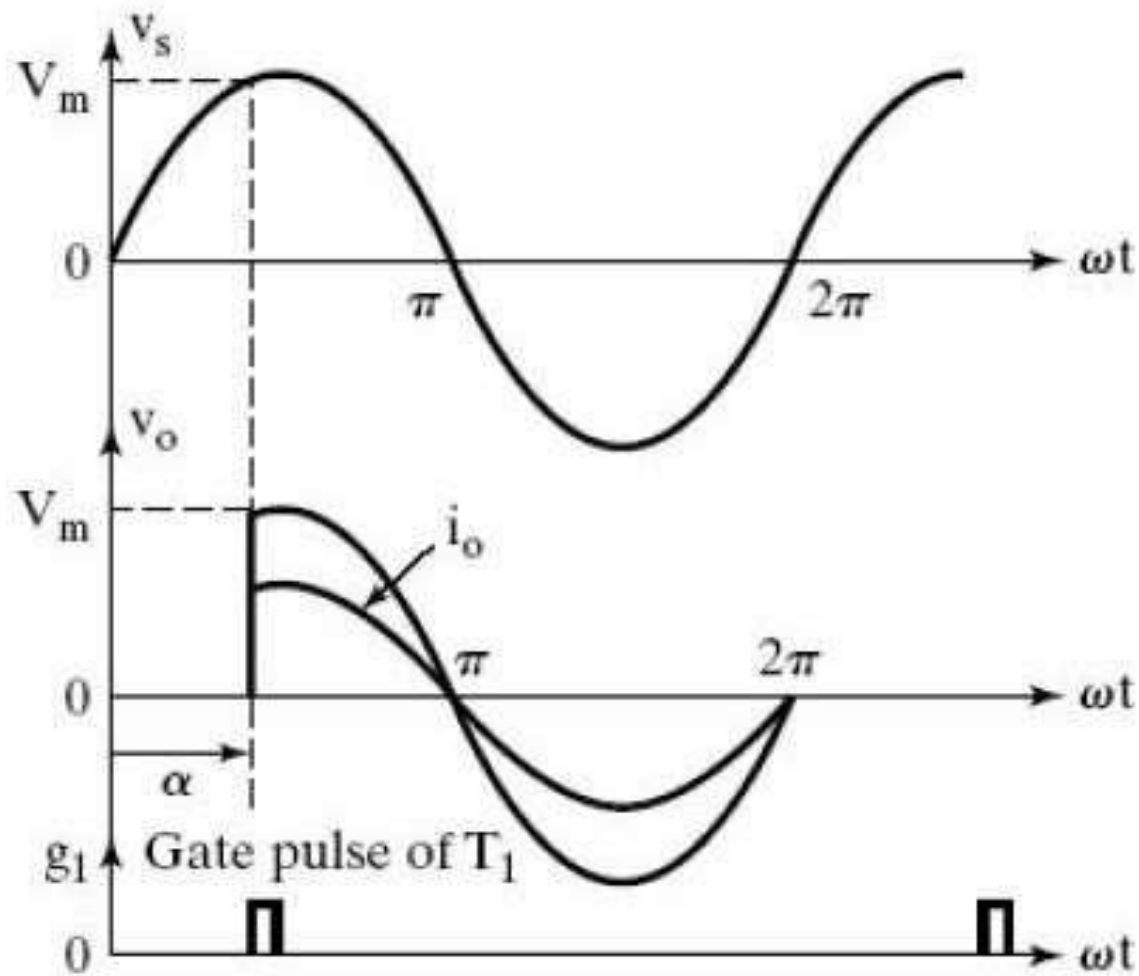**Single phase Half-wave AC phase controller  
(Unidirectional Controller)**



# Equations

- **Input AC Supply Voltage**

$$v_s = V_m \sin \omega t$$

$$V_S = V_{in(RMS)} = \frac{V_m}{\sqrt{2}} = \text{RMS value of}$$

input supply voltage

# Output Load Voltage

$$v_o = v_L = 0;$$

for  $\omega t = 0$  to  $\alpha$

$$v_o = v_L = V_m \sin \omega t;$$

for  $\omega t = \alpha$  to  $2\pi$

# Out Put Load Current

$$i_o = i_L = \frac{v_o}{R_L} = \frac{V_m \sin \omega t}{R_L} = I_m \sin \omega t ;$$

for  $\omega t = \alpha$  to  $2\pi$

$$i_o = i_L = 0;$$

for  $\omega t = 0$  to  $\alpha$

# Expression For RMS Out put Load Voltage

$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[ \int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t .d (\omega t) \right]}$$
$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ \int_{\alpha}^{2\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) .d (\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{4\pi} \left[ \int_{\alpha}^{2\pi} (1 - \cos 2\omega t) \cdot d(\omega t) \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[ \int_{\alpha}^{2\pi} d(\omega t) - \int_{\alpha}^{2\pi} \cos 2\omega t \cdot d\omega t \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[ \left( \omega t \right) \Big|_{\alpha}^{2\pi} - \left( \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{2\pi} \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(2\pi - \alpha) - \left(\frac{\sin 2\omega t}{2}\right) / \alpha^{2\pi}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(2\pi - \alpha) - \left\{ \frac{\sin 4\pi}{2} - \frac{\sin 2\alpha}{2} \right\}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{(2\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}\sqrt{2\pi}} \sqrt{(2\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[ (2\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$


$$V_{O(RMS)} = V_{i(RMS)} \sqrt{\frac{1}{2\pi} \left[ (2\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{O(RMS)} = V_S \sqrt{\frac{1}{2\pi} \left[ (2\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

where  $V_{i(RMS)} = V_S = \frac{V_m}{\sqrt{2}} =$

RMS value of input supply voltage

# Control Characteristics

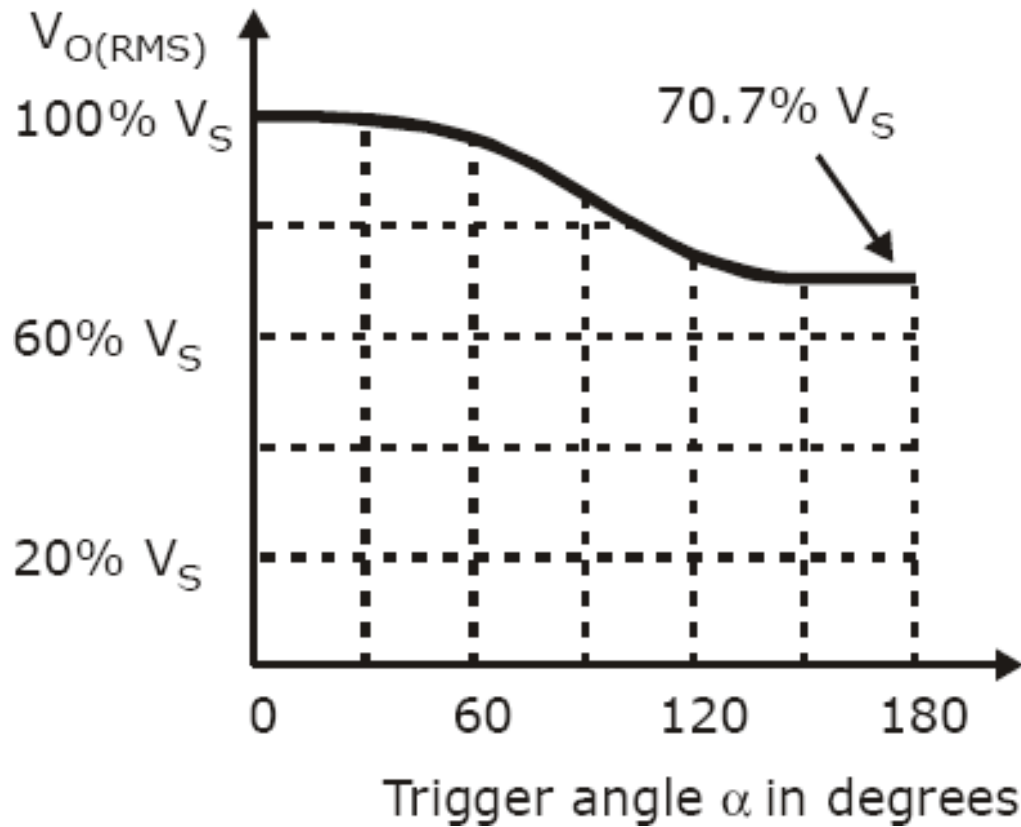

# Average Value of Out put Voltage

$$V_{O(dc)} = \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m \sin \omega t . d (\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \int_{\alpha}^{2\pi} \sin \omega t . d (\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_{\alpha}^{2\pi} \right]$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [-\cos 2\pi + \cos \alpha] ; \cos 2\pi = 1$$

$$V_{dc} = \frac{V_m}{2\pi} [\cos \alpha - 1] ; V_m = \sqrt{2}V_s$$

Hence,

$$V_{dc} = \frac{\sqrt{2}V_s}{2\pi} (\cos \alpha - 1)$$

When  $\alpha$  is varied from 0 to  $\pi$


$$V_{dc} \text{ varies from } 0 \text{ to } \frac{-V_m}{\pi}$$

# Disadvantages

- Output load voltage has a DC component as the two halves are not symmetrical with respect to '0' level.
- Limited range of RMS output voltage control from 100% of  $V_S$  to 70.7% of  $V_S$ , when we vary the trigger angle from zero to 180 degrees.


Single Phase Full Wave Ac Voltage  
Controller (Bidirectional Controller)  
With R-Load

# Single Phase Full Wave Ac Voltage Controller With R-Load

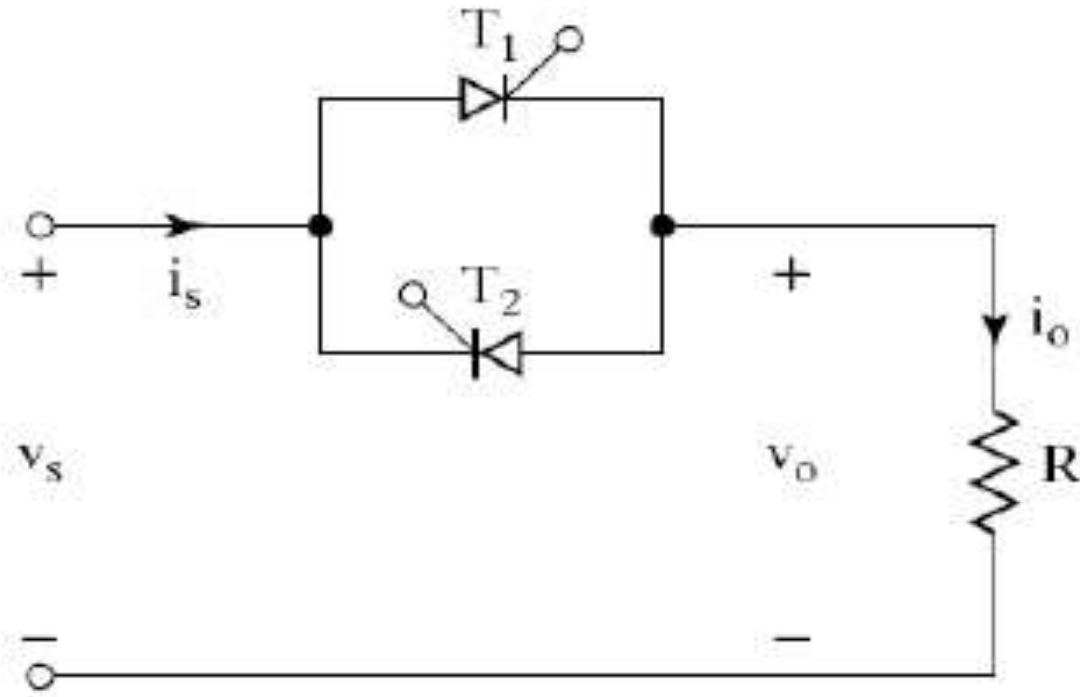

**Fig.: Single phase full wave ac voltage controller (Bi-directional Controller) using SCR**
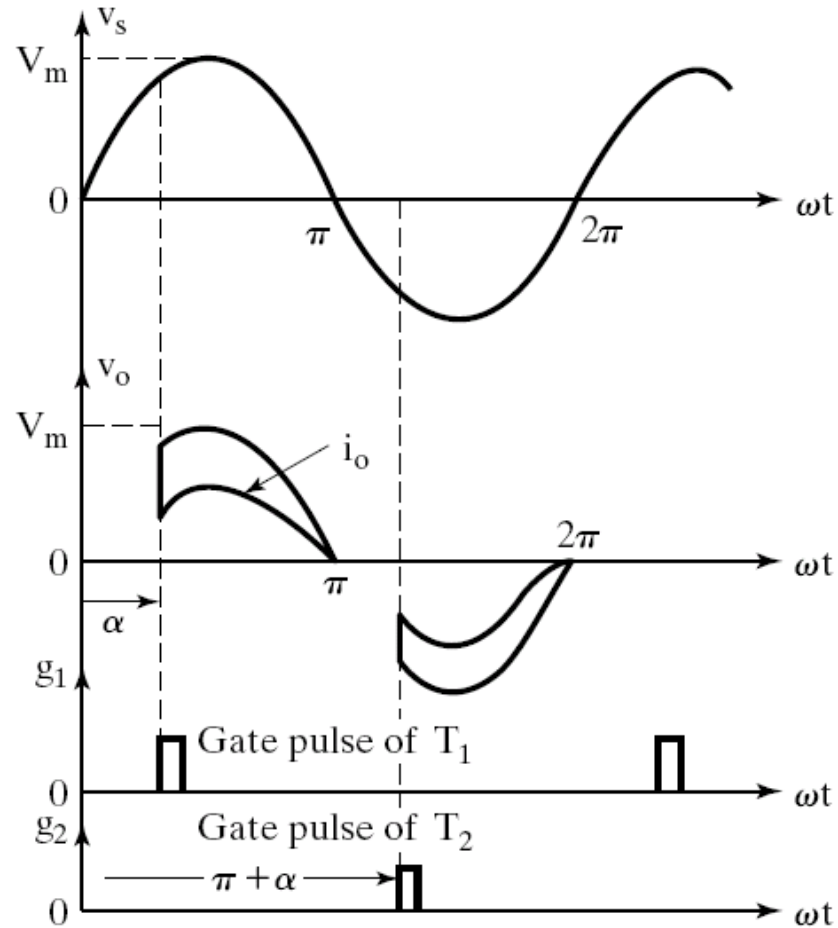
# Waveforms of single phase full wave ac voltage controller



# Expression for RMS output voltage

$$V_{L(RMS)}^2 = \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t$$

$$V_{L(RMS)}^2 = \frac{1}{2\pi} \int_0^{2\pi} v_L^2 \cdot d(\omega t)$$

$$V_{L(RMS)}^2 = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t) + \int_{\pi + \alpha}^{2\pi} (V_m \sin \omega t)^2 d(\omega t) \right]$$

Contd...

$$= \frac{1}{2\pi} \left[ V_m^2 \int_{\alpha}^{\pi} \sin^2 \omega t \cdot d(\omega t) + V_m^2 \int_{\pi+\alpha}^{2\pi} \sin^2 \omega t \cdot d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[ V_m^2 \int_{\alpha}^{\pi} \sin^2 \omega t \cdot d(\omega t) + V_m^2 \int_{\pi+\alpha}^{2\pi} \sin^2 \omega t \cdot d(\omega t) \right]$$

$$= \frac{V_m^2}{2\pi} \left[ \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) + \int_{\pi+\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right]$$

$$= \frac{V_m^2}{2\pi \times 2} \left[ \int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t \cdot d(\omega t) + \int_{\pi+\alpha}^{2\pi} d(\omega t) - \int_{\pi+\alpha}^{2\pi} \cos 2\omega t \cdot d(\omega t) \right]$$

$$= \frac{V_m^2}{4\pi} \left[ \left( \omega t \right) \Big|_{\alpha}^{\pi} + \left( \omega t \right) \Big|_{\pi+\alpha}^{2\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\pi+\alpha}^{2\pi} \right]$$

$$= \frac{V_m^2}{4\pi} \left[ (\pi - \alpha) + (\pi - \alpha) - \frac{1}{2} (\sin 2\pi - \sin 2\alpha) - \frac{1}{2} (\sin 4\pi - \sin 2(\pi + \alpha)) \right]$$

$$= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) - \frac{1}{2} (0 - \sin 2\alpha) - \frac{1}{2} (0 - \sin 2(\pi + \alpha)) \right]$$

$$= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin 2(\pi + \alpha)}{2} \right]$$

$$= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin(2\pi + 2\alpha)}{2} \right]$$

$$= \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{1}{2}(\sin 2\pi \cos 2\alpha + \cos 2\pi \sin 2\alpha) \right]$$

$$\sin 2\pi = 0 \quad \& \quad \cos 2\pi = 1$$

Therefore,

$$V_{L(RMS)}^2 = \frac{V_m^2}{4\pi} \left[ 2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin 2\alpha}{2} \right]$$

$$V_{L(RMS)}^2 = \frac{V_m^2}{4\pi} \left[ (2\pi - 2\alpha) + \sin 2\alpha \right]$$

- Taking the square root, we get

$$V_{L(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[ (2\pi - 2\alpha) + \sin 2\alpha \right]}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}\sqrt{2\pi}} \sqrt{\left[ (2\pi - 2\alpha) + \sin 2\alpha \right]}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[ (2\pi - 2\alpha) + \sin 2\alpha \right]}$$

$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[ 2 \left\{ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right\} \right]}$$


$$V_{L(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{L(RMS)} = V_{i(RMS)} \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$


$$V_{L(RMS)} = V_S \sqrt{\frac{1}{\pi} \left[ (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

Single Phase Full Wave Ac Voltage  
Controller (Bidirectional Controller)  
With R-L Load

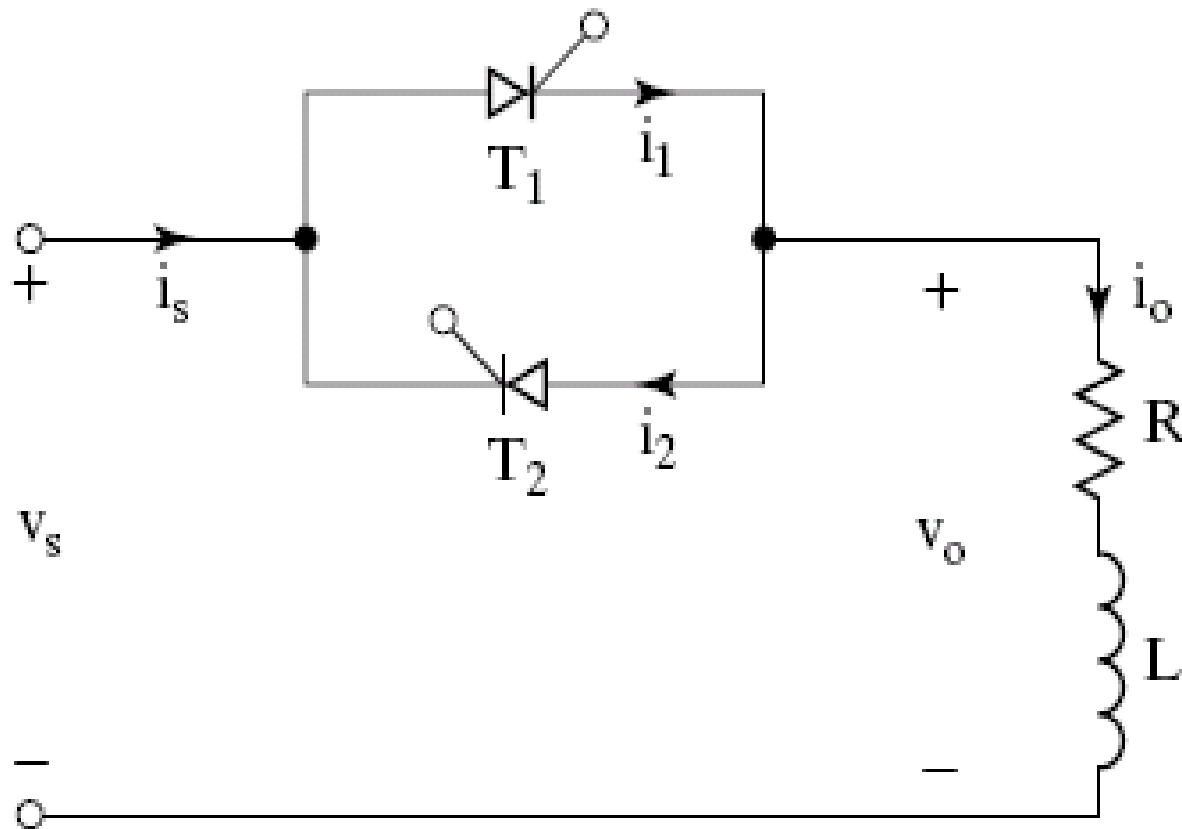
# Single Phase Full Wave Ac Voltage Controller (Bidirectional Controller) With R-L Load


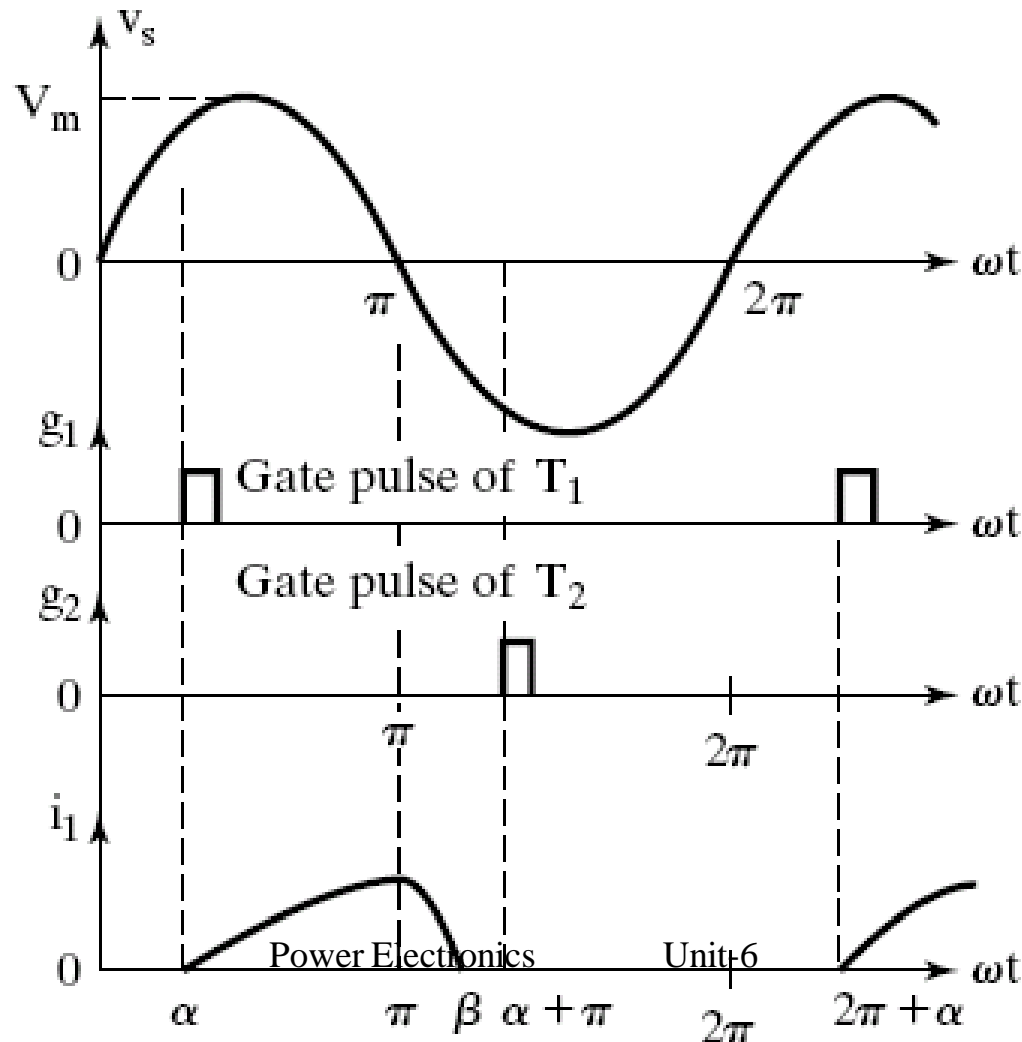
# Input supply voltage & Thyristor current waveforms




# Gating Signals

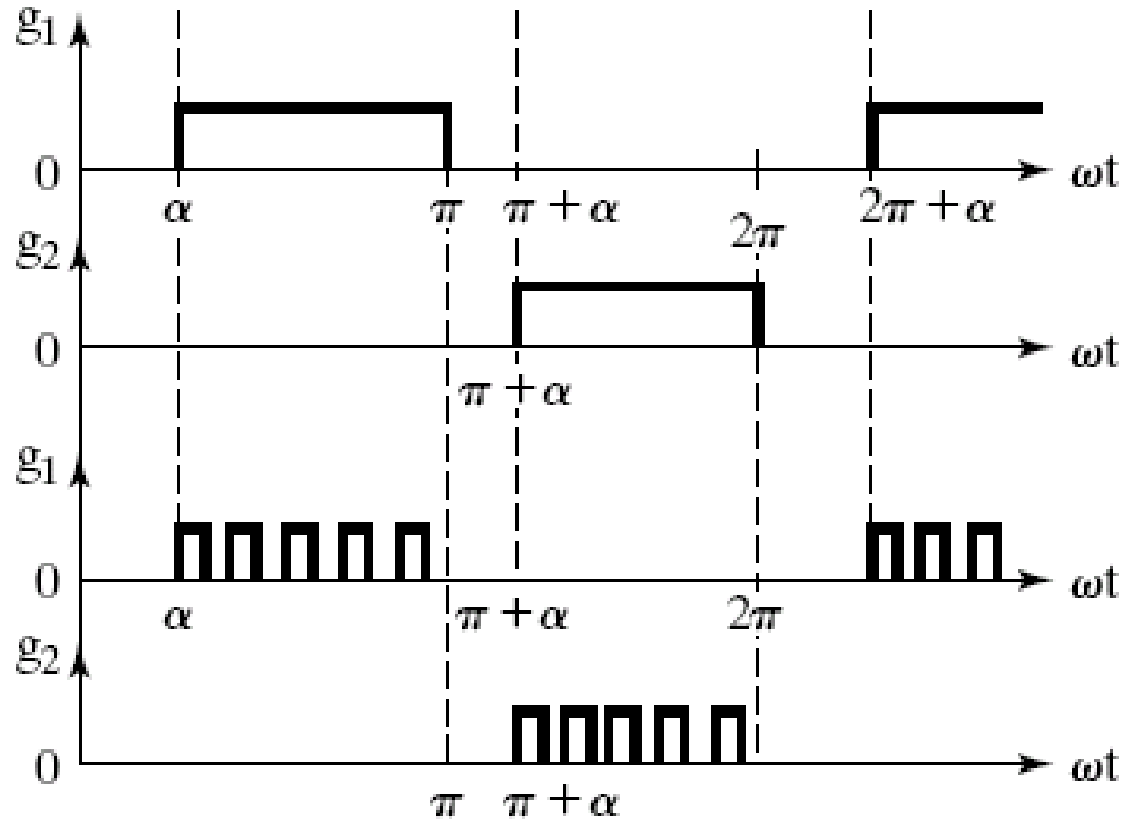

# Waveforms For RL load for for Discontinuous Conduction

$$\alpha > \phi \text{ and}$$

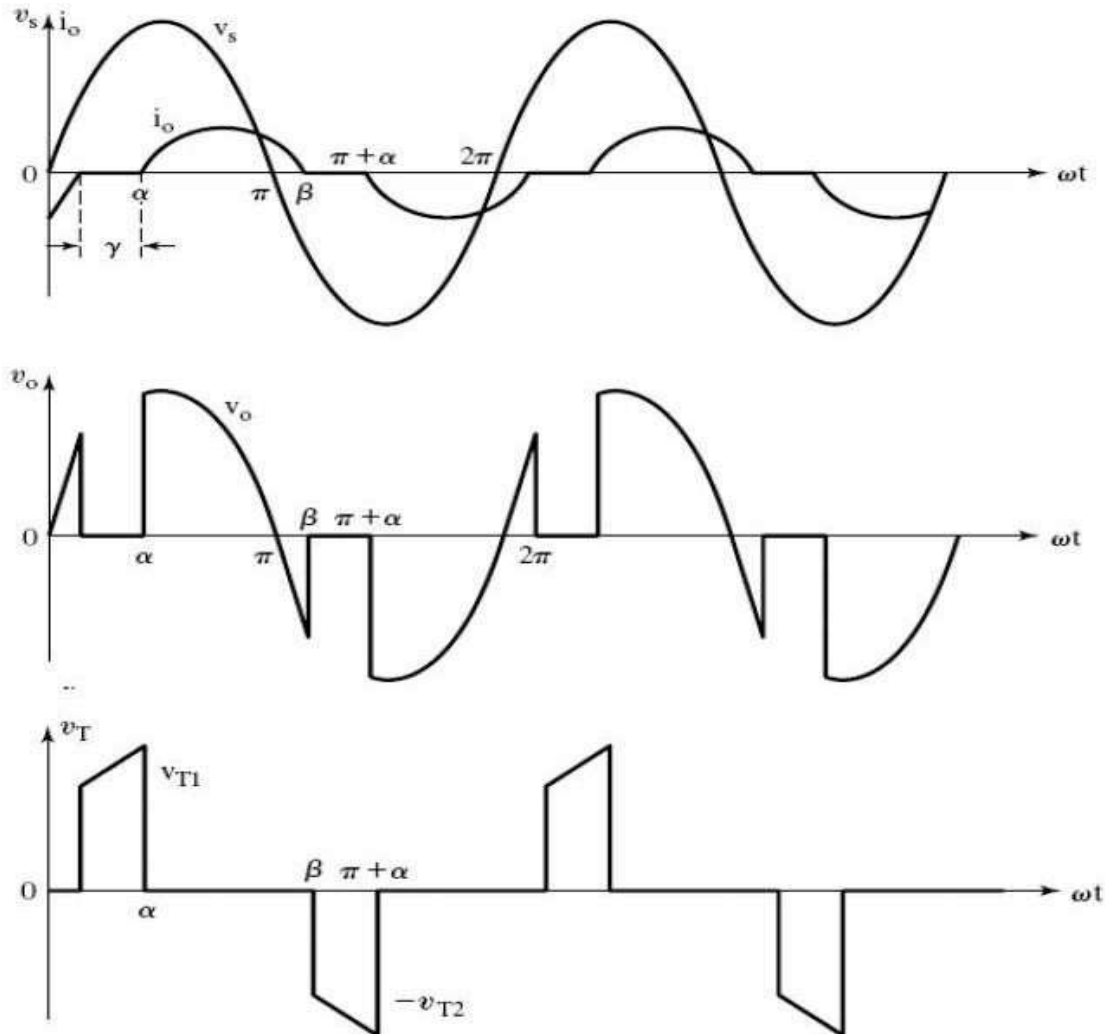

Expression for the inductive load current of a single phase full wave ac voltage controller with RL load

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right]$$


Where  $Z = \sqrt{R^2 + (\omega L)^2}$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

= Load impedance angle (power factor angle of load).

# Output voltage and output current waveforms for a single phase full wave ac voltage controller with RL load for $\alpha \leq \phi$

$\alpha \leq \phi$

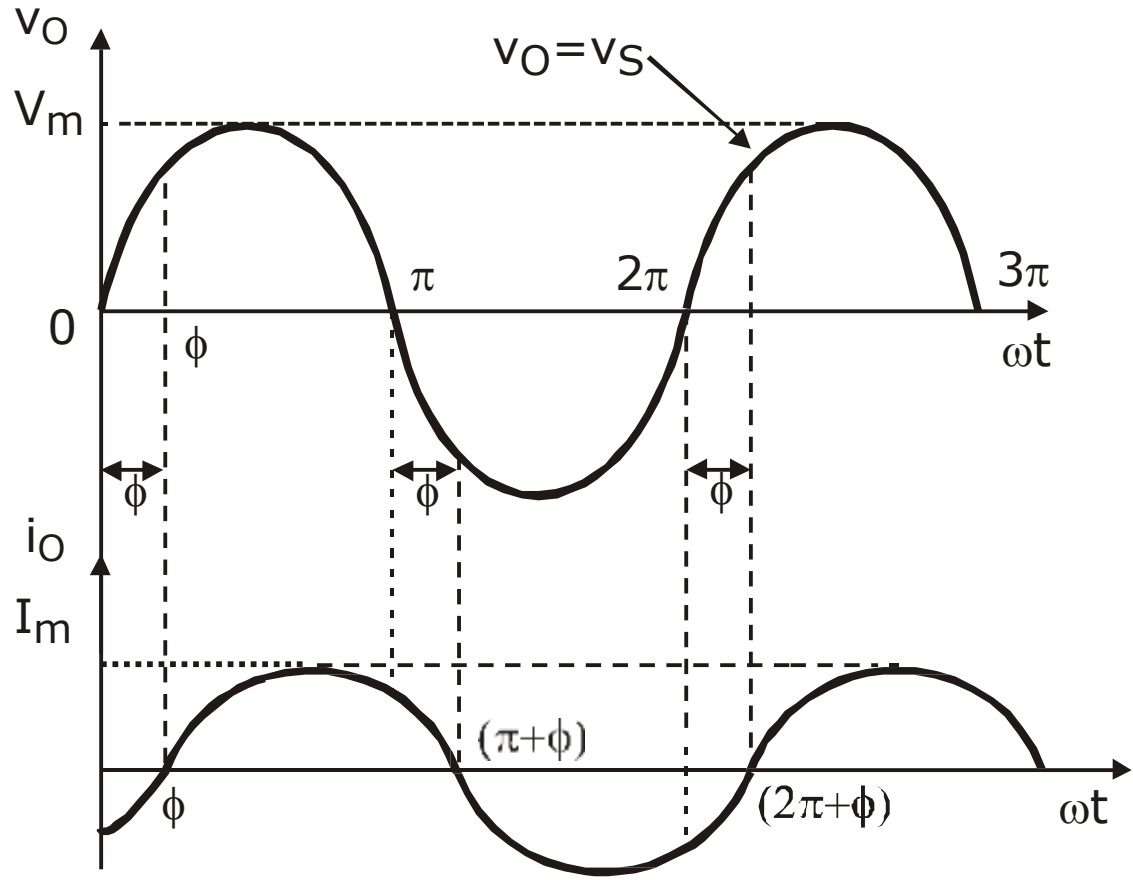

# TRIAC and Its Modes of Operation

# TRIAC

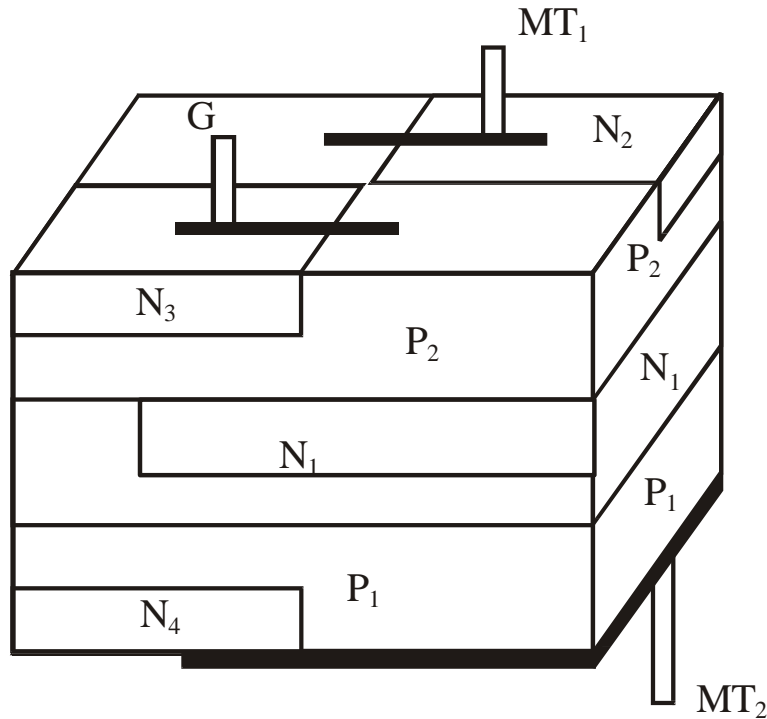


Fig.1 : Triac Structure  
Symbol


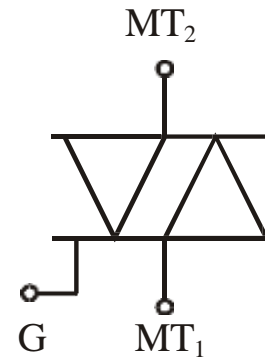


Fig. 2 : Triac
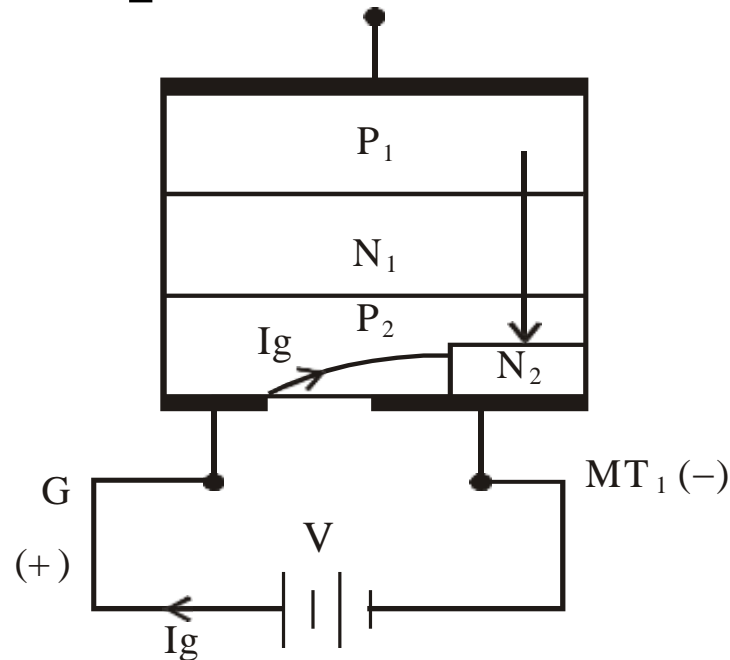
# TRIGGERING MODES OF TRIAC


- **MODE 1 : MT1 positive, Positive gate current ( I<sup>+</sup> mode of operation )**



- When  $V_{GT}$  and gate current are positive with respect to MT1, the gate current flows through P2-N2 junction
- The junction P1-N1 and P2-N2 are forward biased but junction N1-P2 is reverse biased.
- When sufficient number of charge carriers are injected in P2 layer by the gate current the junction N1-P2 breakdown and triac starts conducting through P1N1P2N2 layers.
- Once triac starts conducting the current increases and its V-I characteristics is similar to that of thyristor. Triac in this mode operates in the first-quadrant.
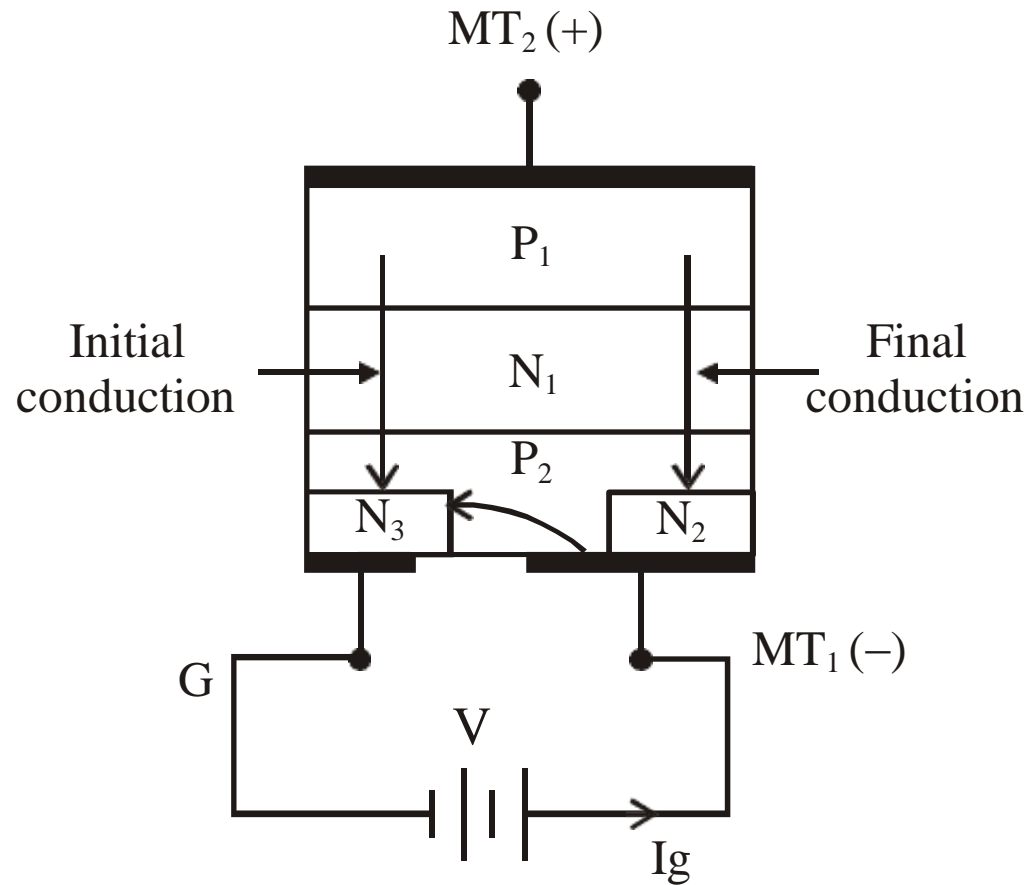
# MODE 2

- **MT2 positive, Negative gate current**  
(I- mode of operation)




- When MT2 is positive and gate G is negative with respect to MT1 the gate current flows through P2-N3 junction
- The junction P1-N1 and P2-N3 are forward biased but junction N1-P2 is reverse biased. Hence, the triac initially starts conducting through P1N1P2N3 layers.
- As a result the potential of layer between P2-N3 rises towards the potential of MT2.
- Thus, a potential gradient exists across the layer P2 with left hand region at a higher potential than the right hand region.

- This results in a current flow in P2 layer from left to right, forward biasing the P2N2 junction. Now the right hand portion P1-N1 - P2-N2 starts conducting.
- The device operates in first quadrant. When compared to Mode 1, triac with MT2 positive and negative gate current is less sensitive and therefore requires higher gate current for triggering.
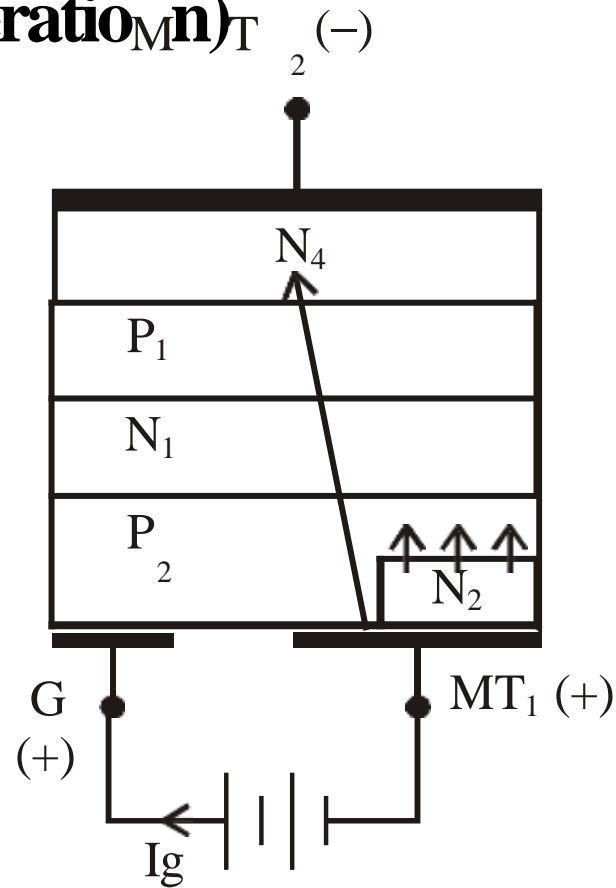
# MODE 3


- **MT2 negative, Positive gate current**  
**(III<sup>+</sup> mode of operation)**



- When MT2 is negative and gate is positive with respect to MT1 junction P2N2 is forward biased and junction P1-N1 is reverse biased.
- N2 layer injects electrons into P2 layer as shown by arrows in figure below.
- This causes an increase in current flow through junction P2-N1. Resulting in breakdown of reverse biased junction N1-P1.
- Now the device conducts through layers P2N1P1N4 and the current starts increasing, which is limited by an external load.
- The device operates in third quadrant in this mode. Triac in this mode is less sensitive and requires higher gate current for triggering.
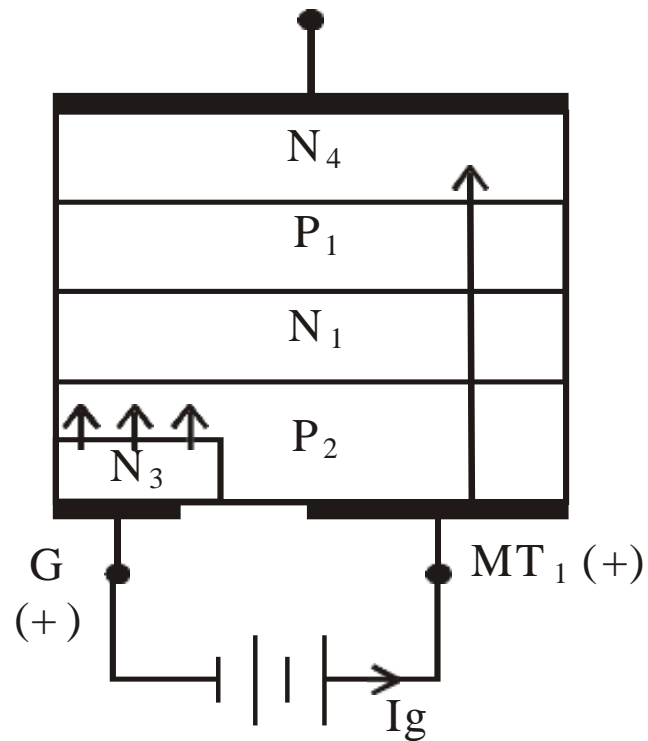
# MODE 4


- **MT2 negative, Negative gate current**  
(III<sup>+</sup> mode of operation)  
MT<sub>2</sub>(-)




- In this mode both MT2 and gate G are negative with respect to MT1, the gate current flows through P2N3 junction as shown.
- Layer N3 injects electrons as shown by arrows into P2 layer. This results in increase in current flow across P1N1 and the device will turn ON due to increased current in layer N1.
- The current flows through layers P2N1P1N4. Triac is more sensitive in this mode compared to turn ON with positive gate current. (Mode 3).

- Triac sensitivity is greatest in the first quadrant when turned ON with positive gate current and also in third quadrant when turned ON with negative gate current. when  $V_{AK}$  is positive with respect to  $V_{AK}$  it is recommended to turn on the triac by a positive gate current.
- When  $V_{AK}$  is negative with respect to  $V_{AK}$  it is recommended to turn on the triac by negative gate current. Therefore Mode 1 and Mode 4 are the preferred modes of operation of a triac (mode 1 and mode 4 of operation are normally used).

# Triac characteristics

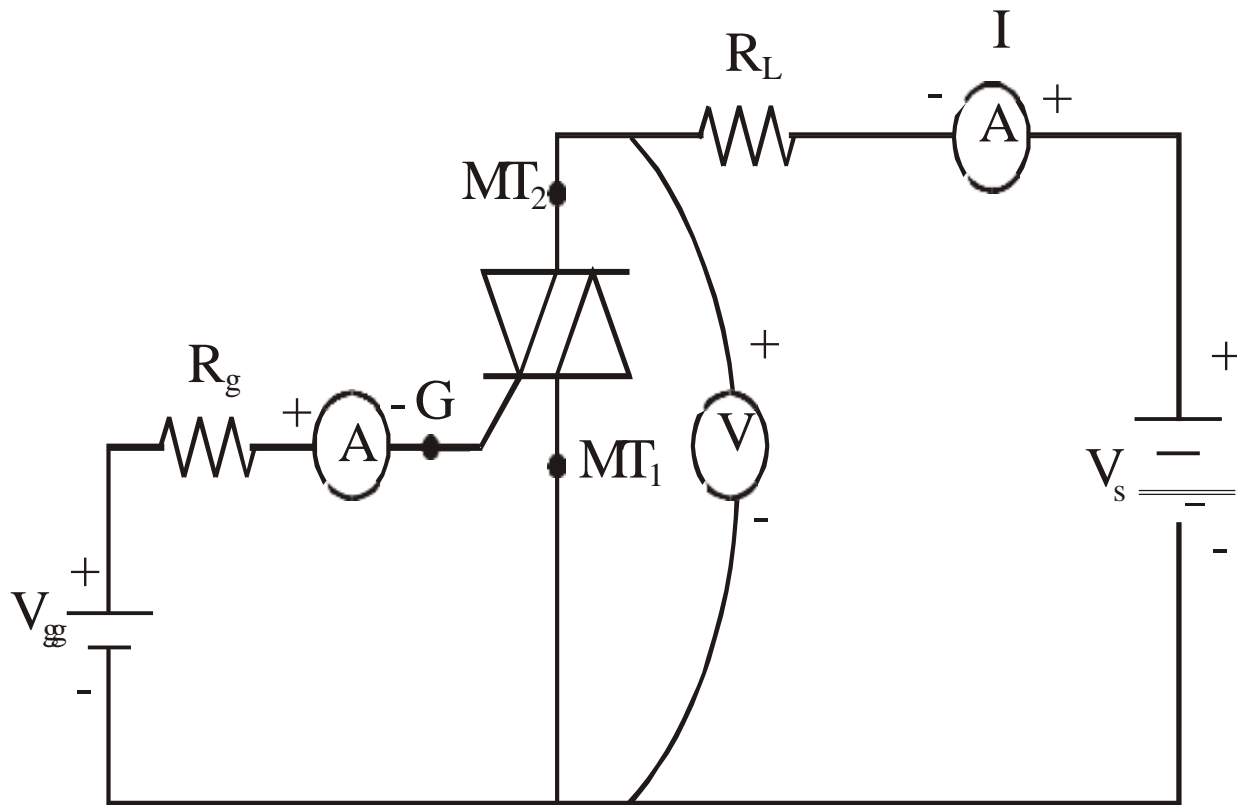


# V-I Characteristics of a triac

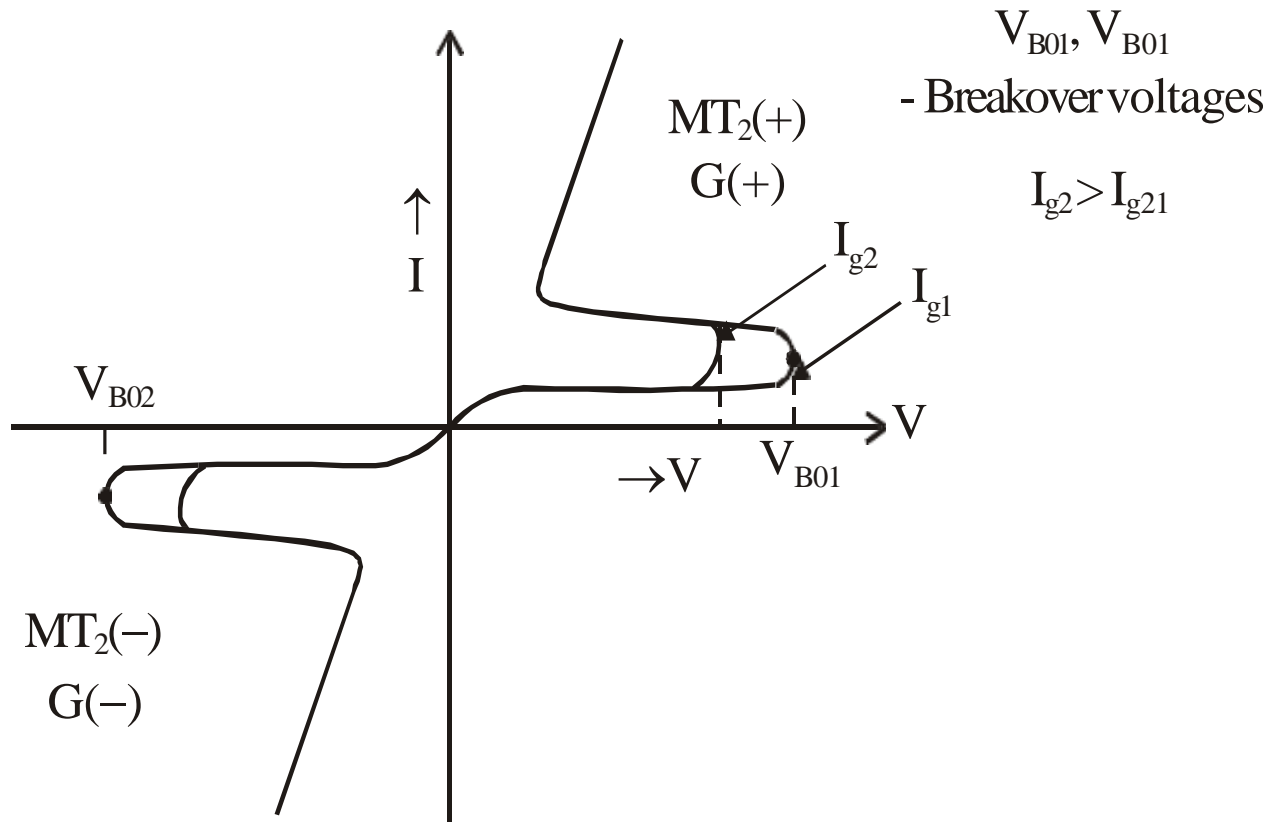


**Single phase full wave ac  
voltage controller  
(Bi-directional Controller) using  
TRIAC**

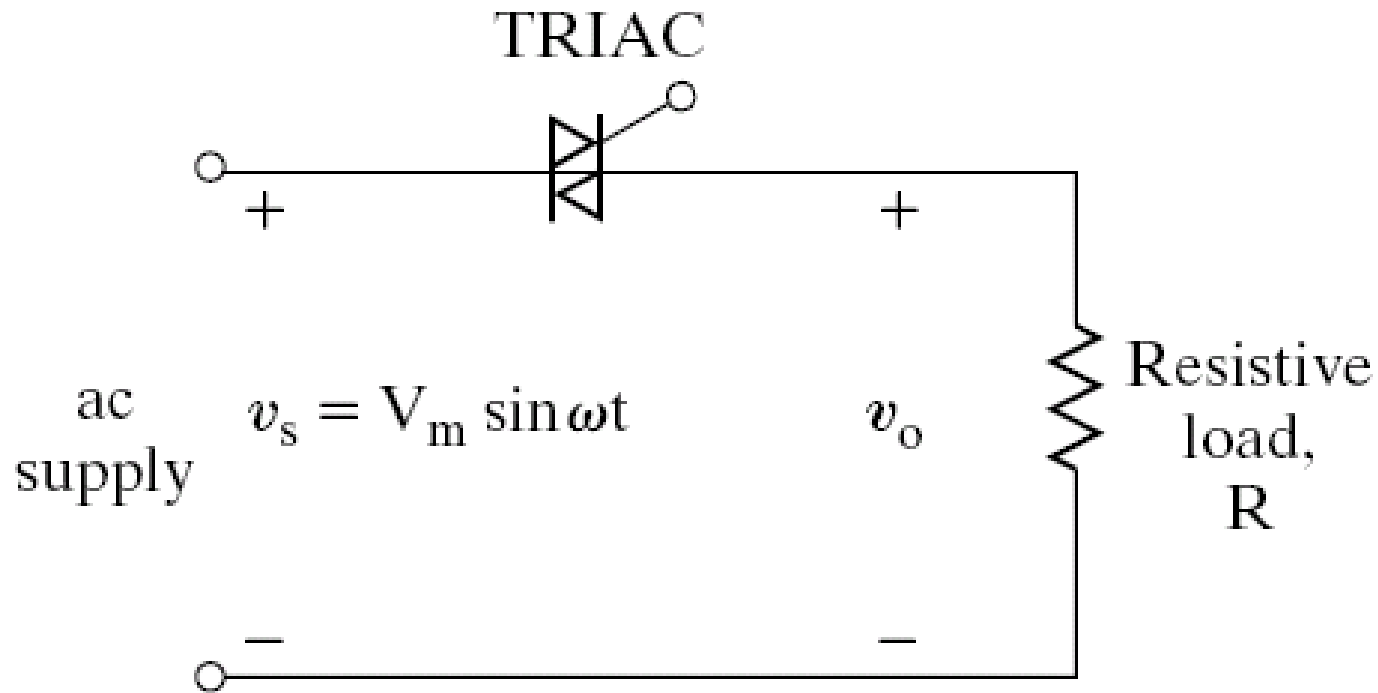
# Single phase full wave ac voltage controller (Bi-directional Controller) using TRIAC




# Waveforms of single phase full wa ller

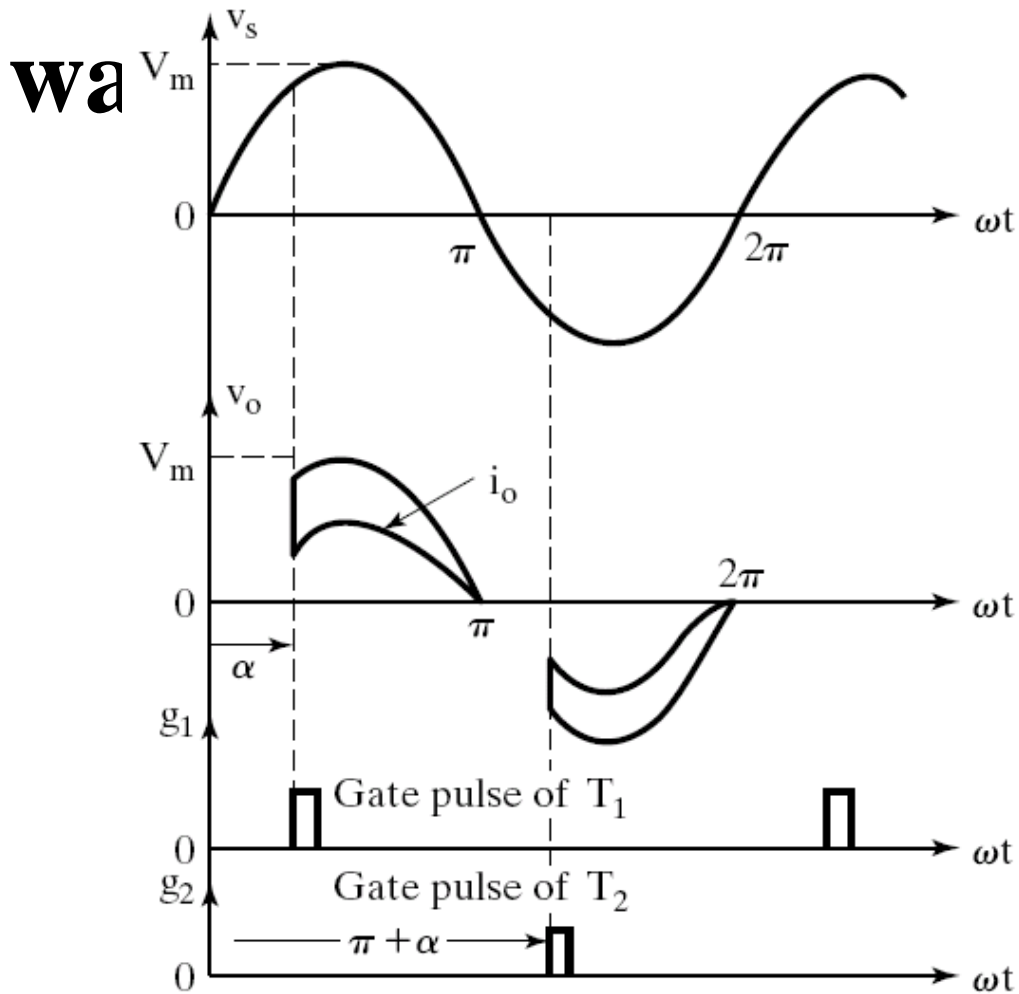
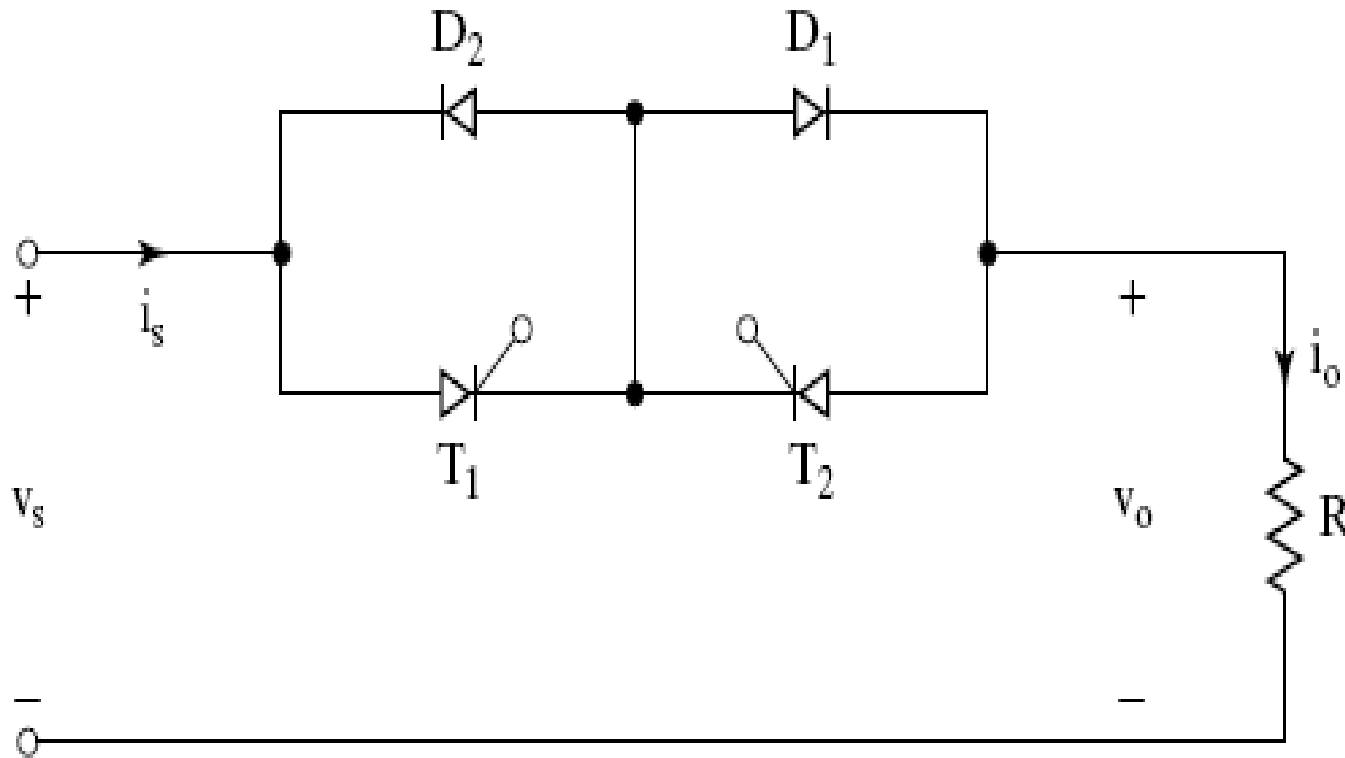
# Single phase full wave ac controller with common cathode (Bidirectional controller in common cathode configuration)


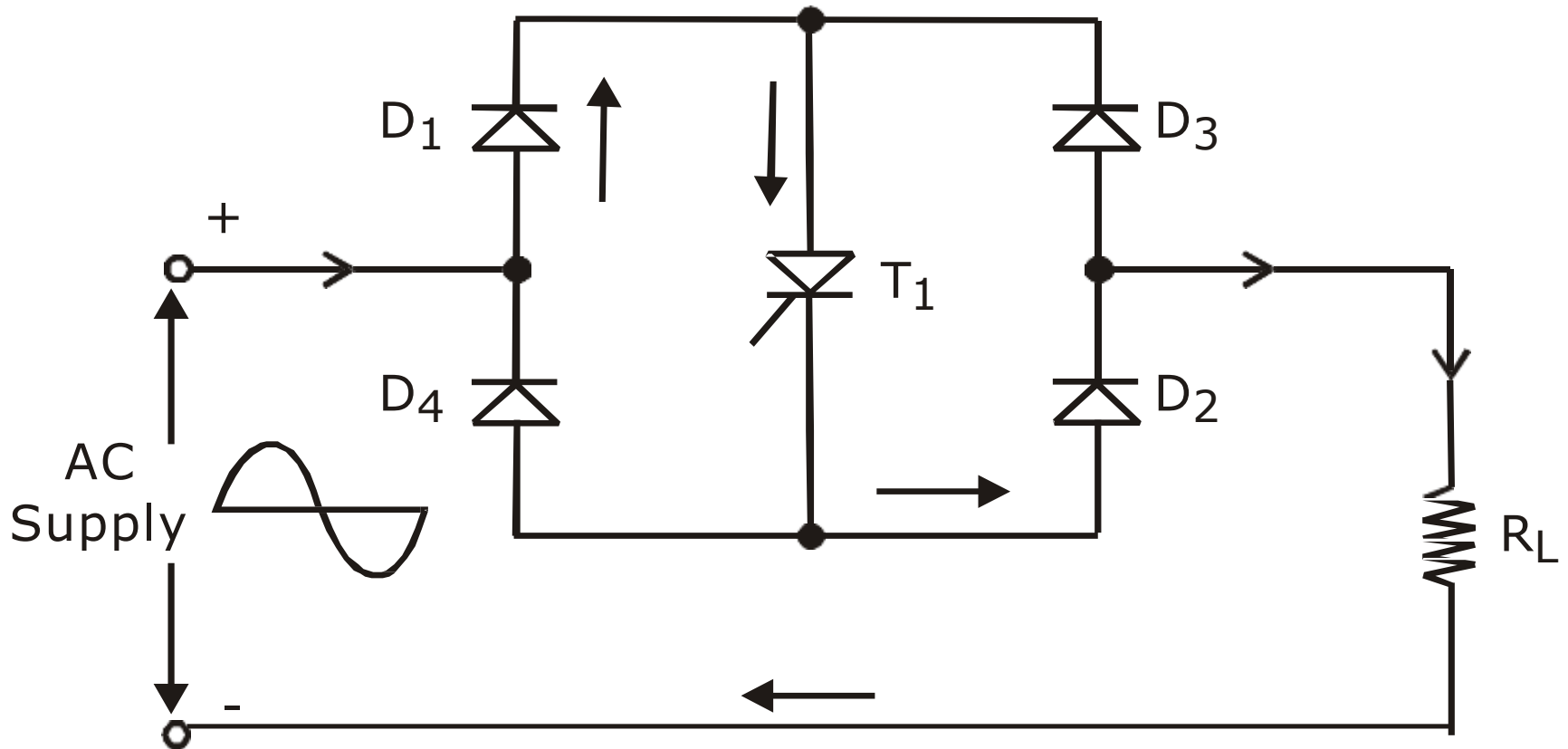
# Single Phase Full Wave Ac Voltage Controller Using A Single Thyristor




# CYCLOCONVERTER

# CYCLOCONVERTER


- A device which converts input power at one frequency to the out put power at different frequency with one stage conversion is called a cycloconverter.
- A cycloconverter requires one stage frequency conversion.
- Cycloconverter of two types
  - (i) Step-Up Cycloconverter (  $f_o > s$  )
  - (ii) step-Down Cycloconverter (  $f_o < fs$  )

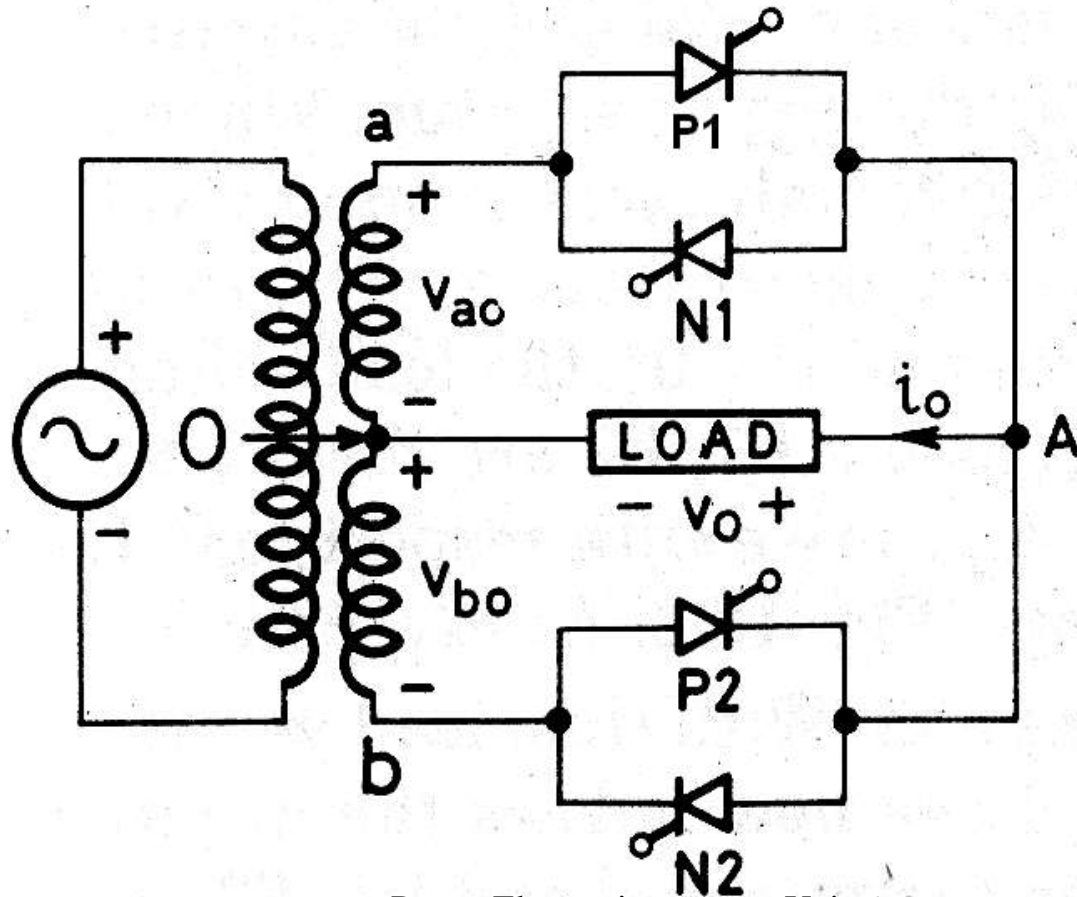
# Single phase to single phase Mid point type step-up Cycloconverter with R load




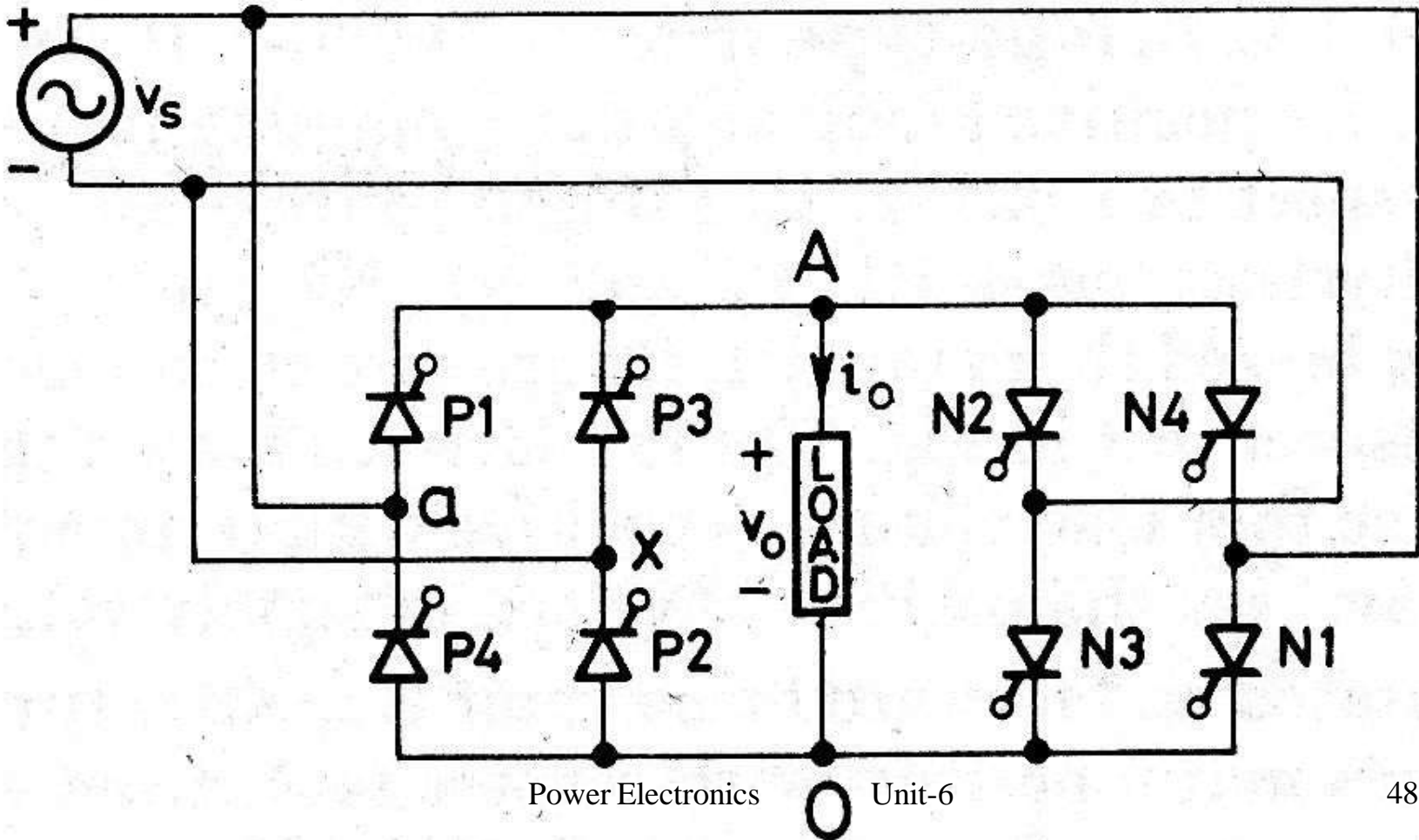
# Single phase to single phase Bridge type step-up Cycloconverter with R load



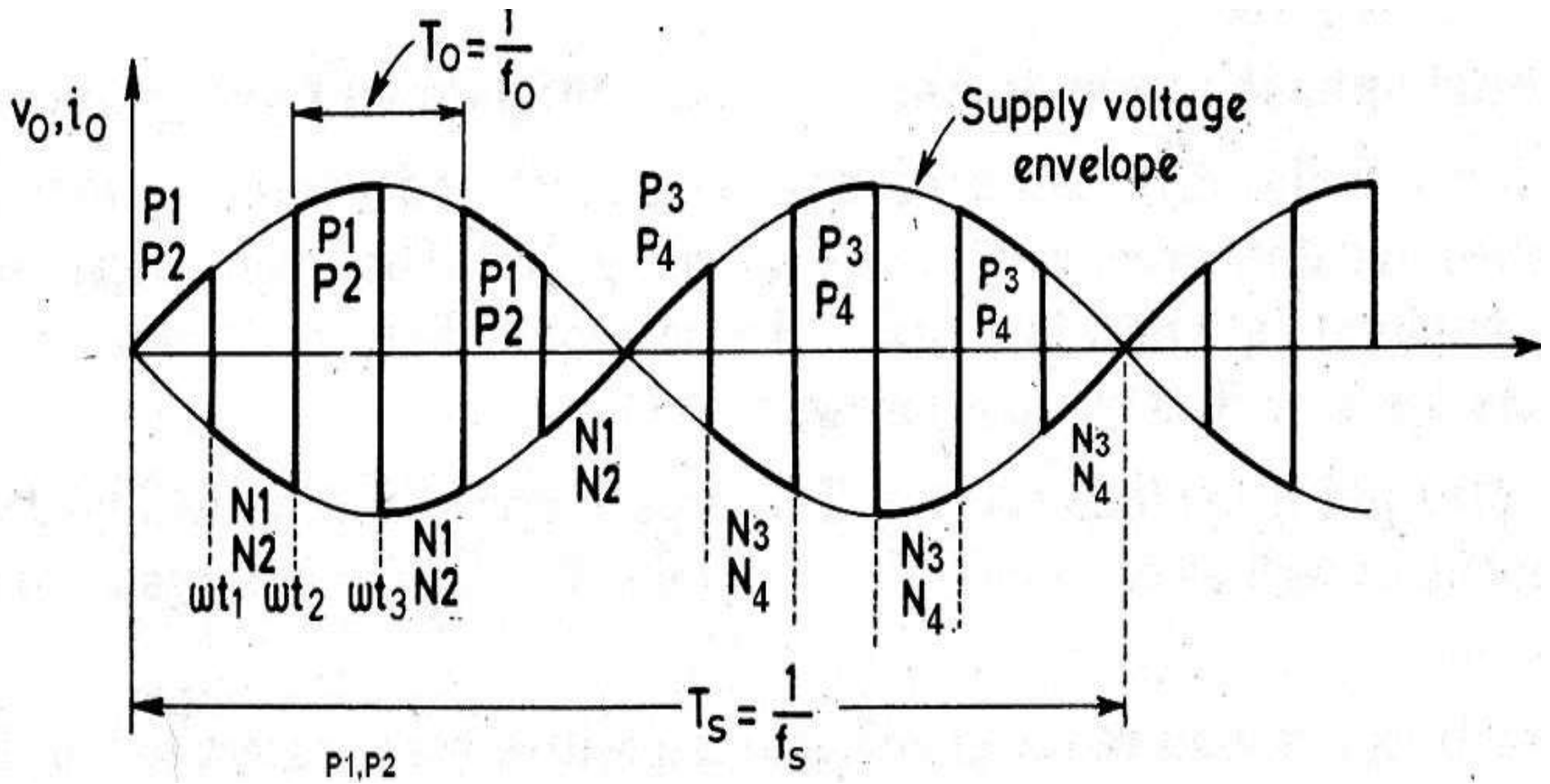



# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform


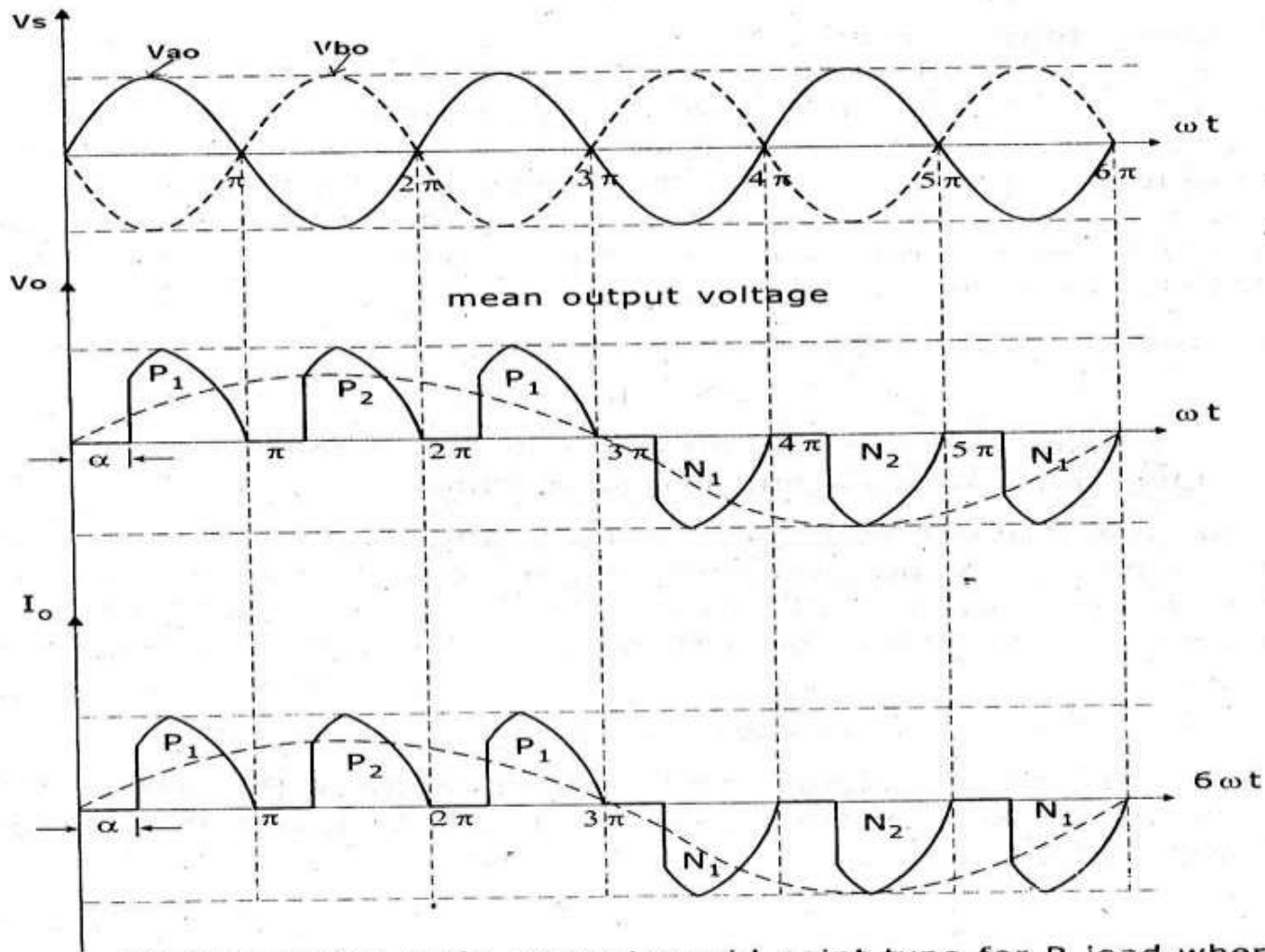


Fig. Step down cyclo converter-mid point type for R load where  $\alpha$  is firing angle

# 1- $\phi$ to 1- $\phi$ Bridge type Cyclo-converter with R and R-L load
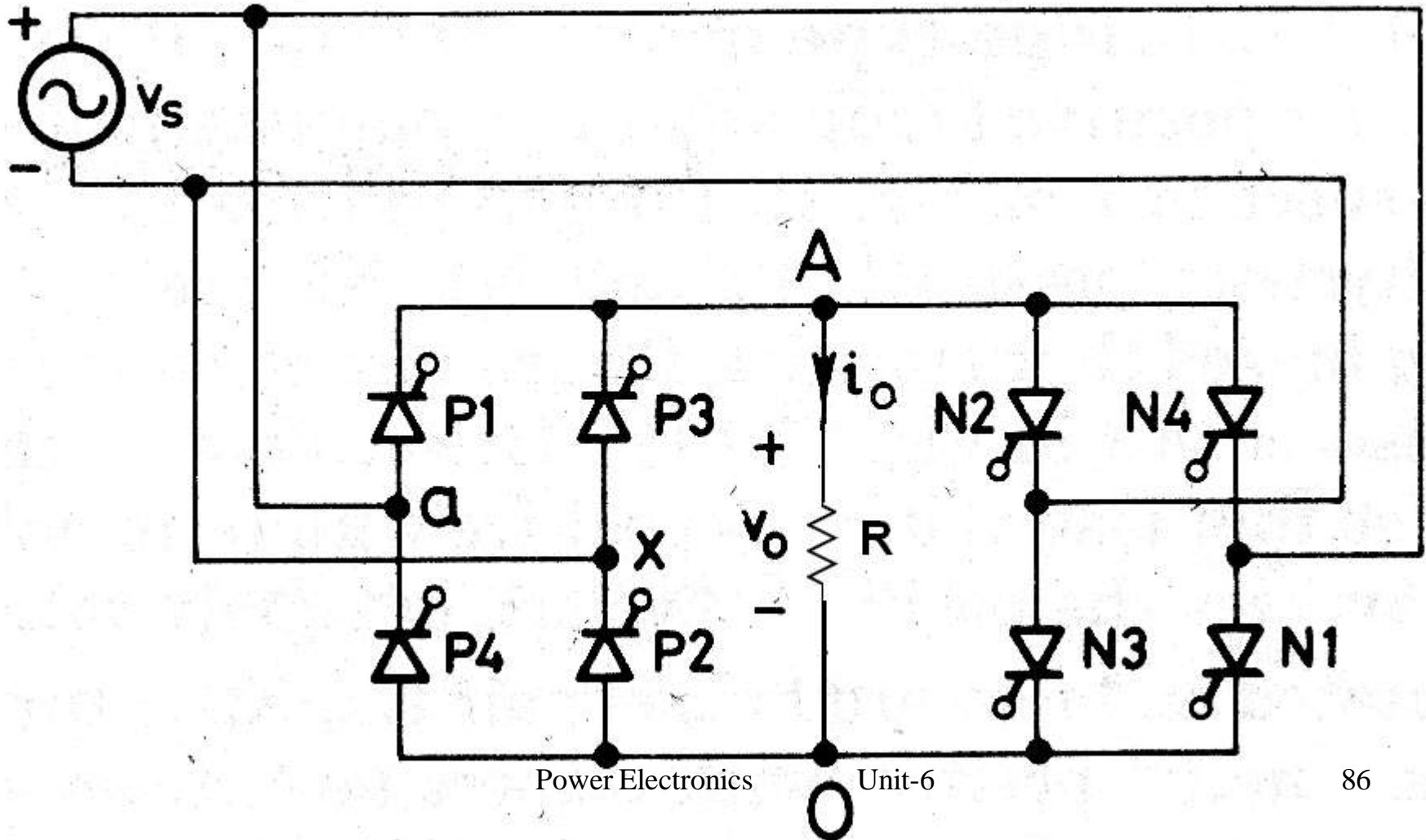
# 1- $\phi$ to 1- $\phi$ Bridge type step-Down Cycloconverter with R load



# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform



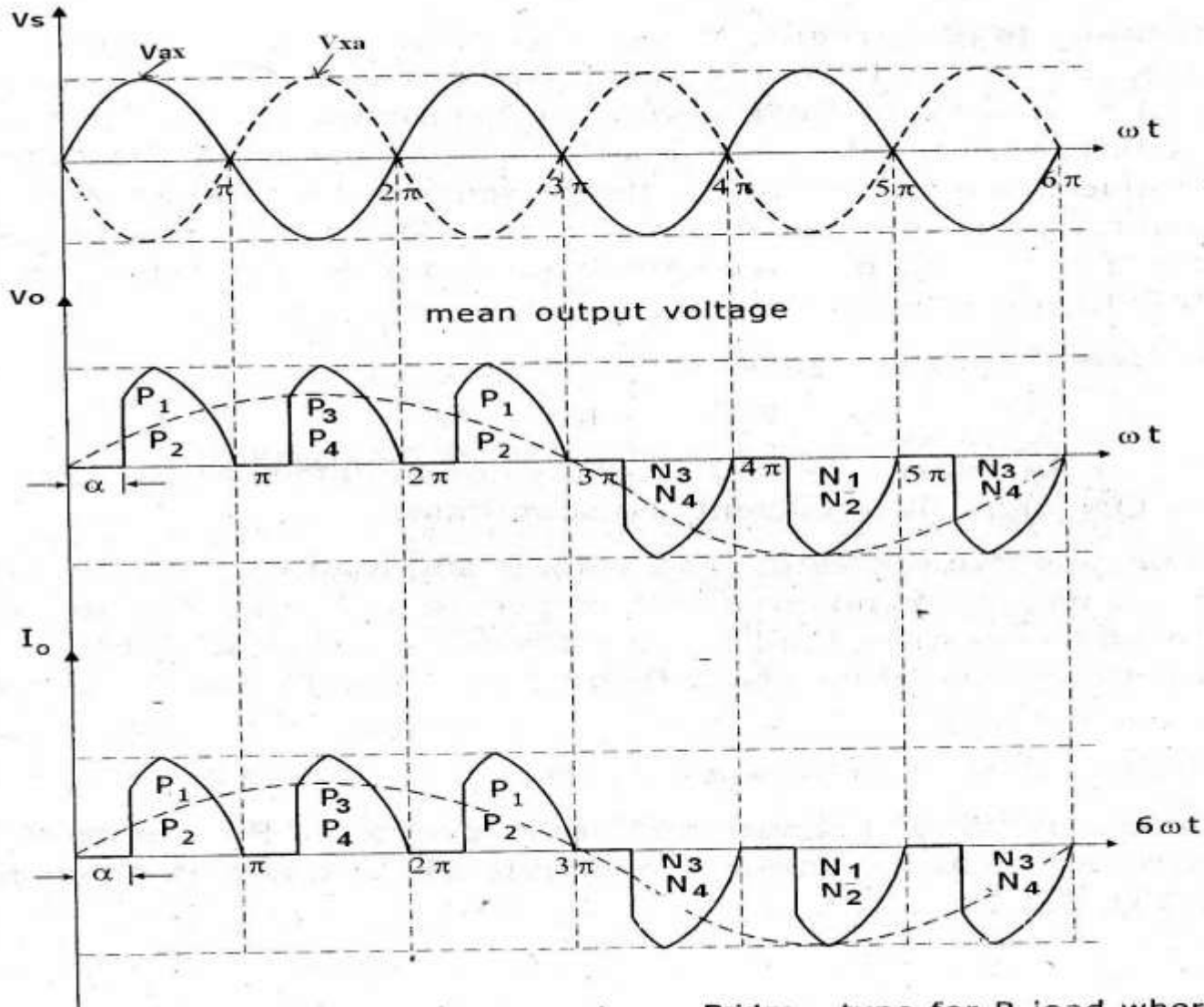


Fig. Step down cyclo converter- Bridge type for R load where  $\alpha$  is firing angle

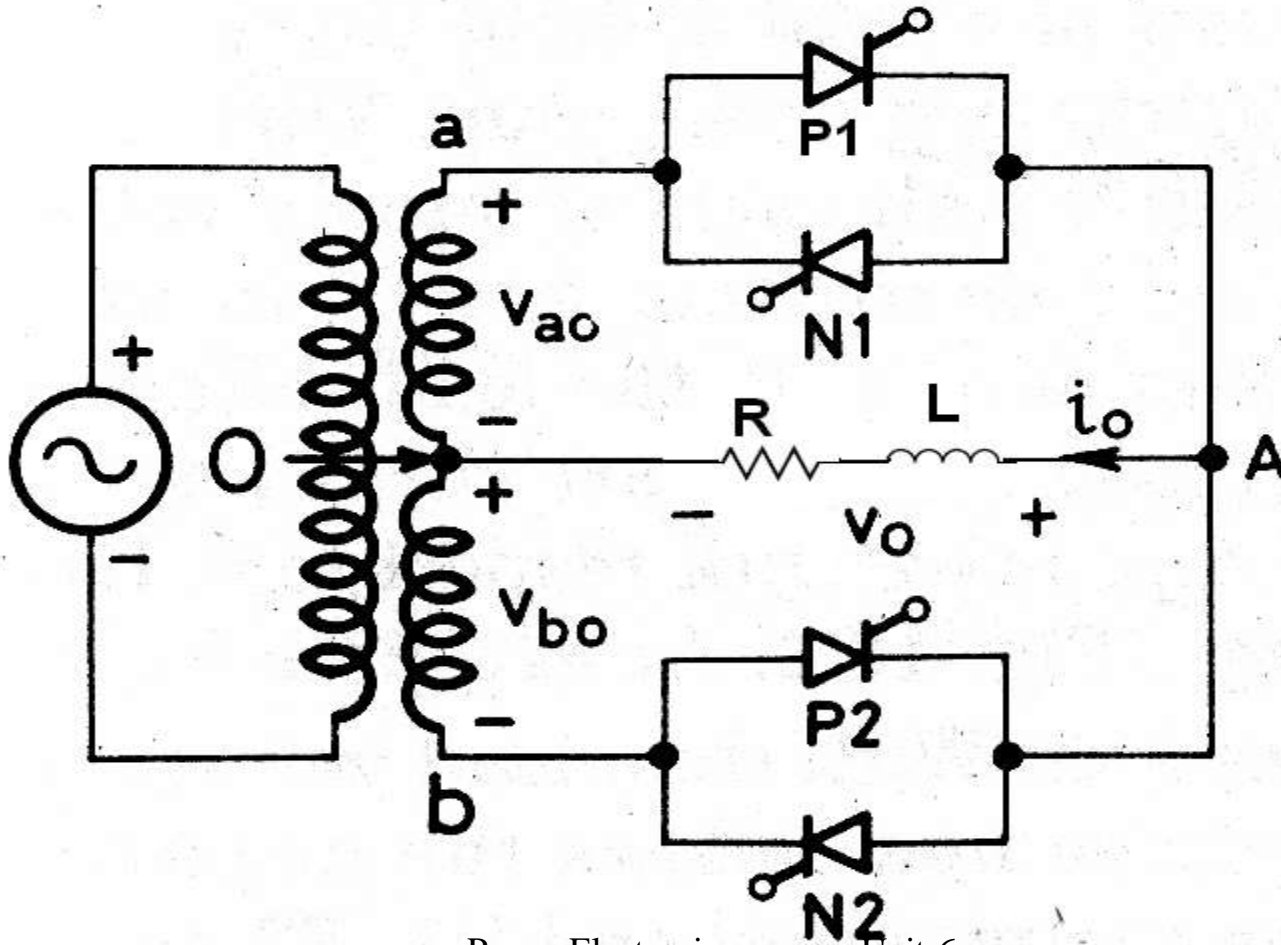
# 1- $\phi$ to 1- $\phi$ Midpoint type step-Down Cycloconverter with R-L load



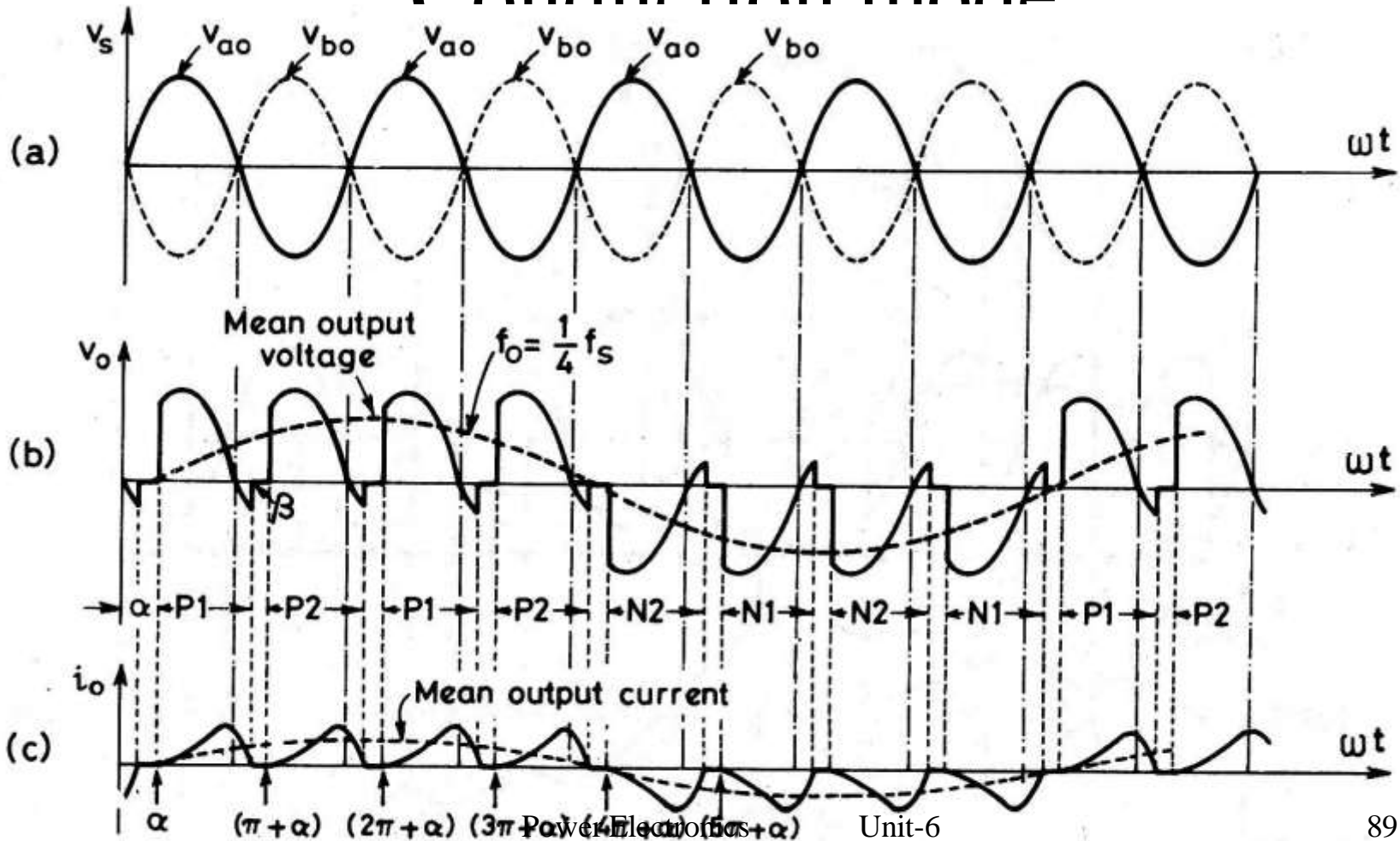
# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform for Discontinuous Conduction mode



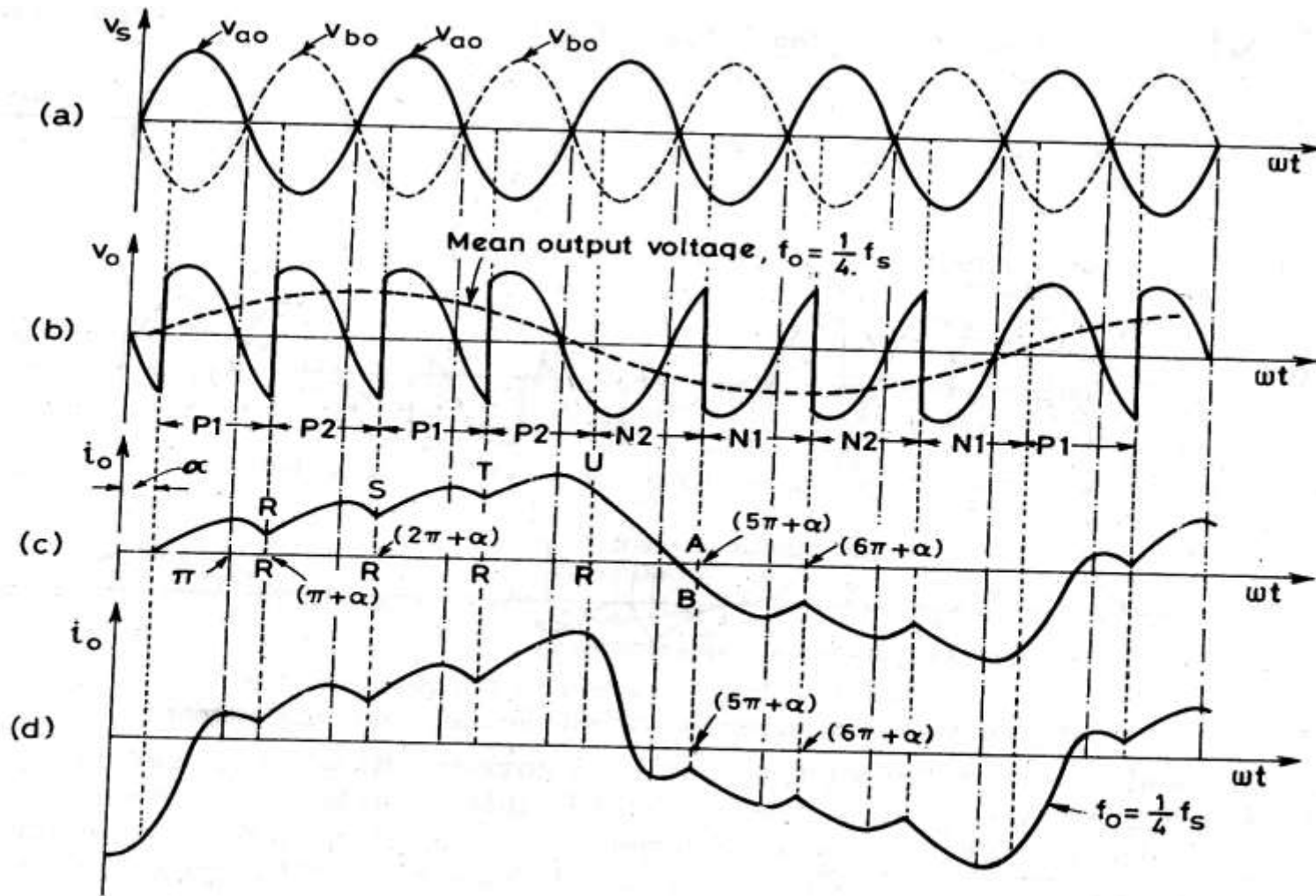
# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform for Continuous Conduction mode


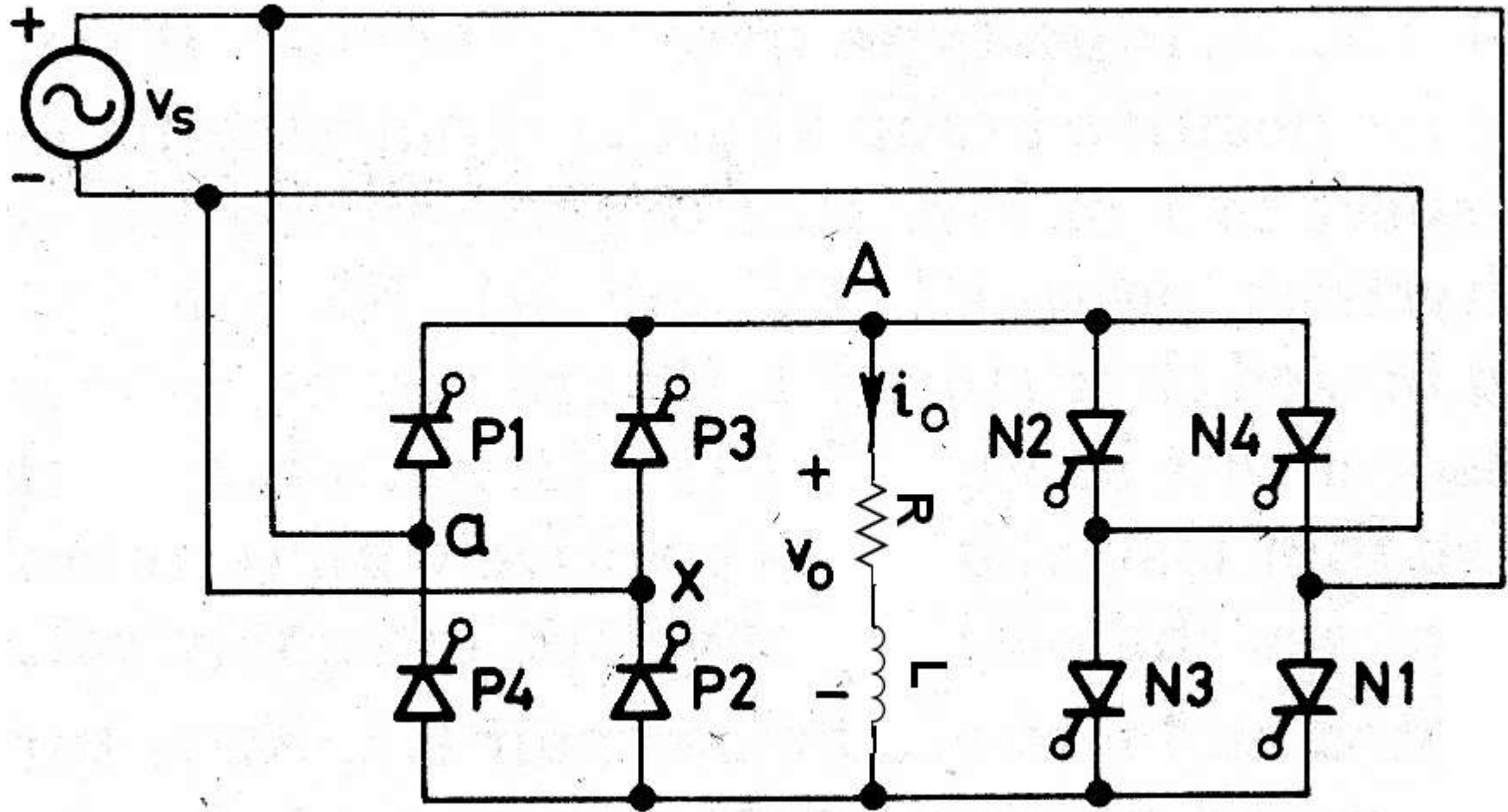
# 1- $\phi$ to 1- $\phi$ Bridge-type step-Down Cycloconverter with R-L load


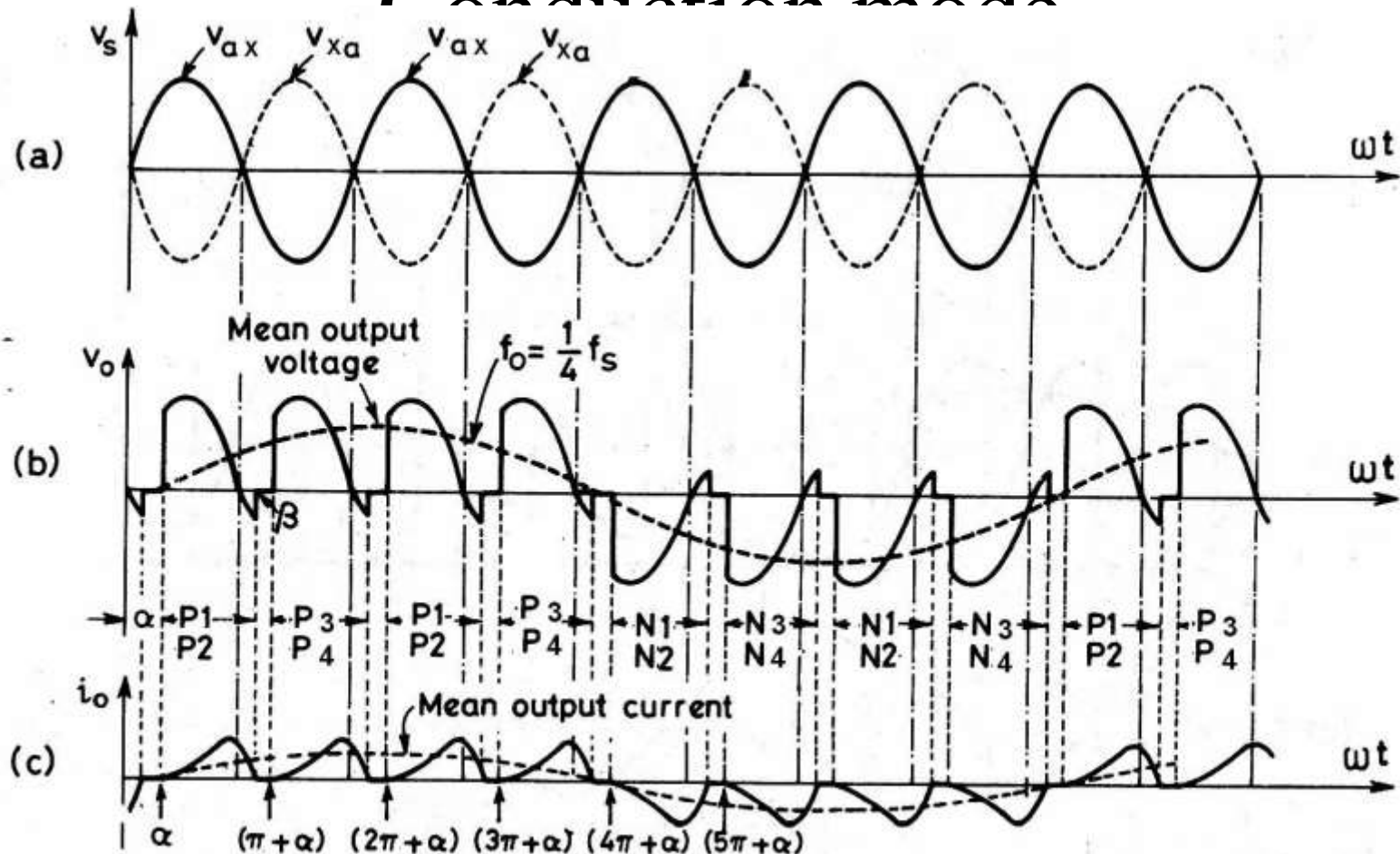
# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform for Discontinuous Conduction mode



# Output voltage ( $V_o$ ) and current ( $I_o$ ) waveform for Continuous Conduction mode

