

Classification of Amplifiers

Type of Signal	Based on No.of Stages	Type of Configuration	Classification based on conduction angle	Frequency of Operation
Small Signal	Single Stage	Common Emitter	Class A Amplifier	Direct Current (DC)
Large Signal	Multistage	Common Base	Class B Amplifier	Audio Frequencies (AF)
		Common Collector	Class AB Amplifier	Radio Frequencies (RF)
			Class C Amplifier	VHF, UHF and SHF Frequencies

Different Regions Of Operation

Region of Operation	Emitter Base Junction	Collector Base Junction
Cut off	Reverse biased	Reverse biased
Active	Forward biased	Reverse biased
Saturation	Forward biased	Forward biased

Transistor Voltage specifications For Various Operating Regions

Transistor	$V_{CE} \text{ (sat)}$	$V_{BE} \text{ (sat)}$	$V_{BE} \text{ (active)}$	$V_{BE} \text{ (cut-in)}$	$V_{BE} \text{ (cut-off)}$
Si	0.2 V	0.8 V	0.7 V	0.5 V	0 V
Ge	0.1 V	0.3 V	0.2 V	0.1 V	- 0.1 V


Condition for Active & Saturation Regions

For saturation :


$$I_B > \frac{I_C}{\beta_{dc}}$$

For active region :


$$V_{CE} > V_{CE \text{ (sat)}}$$

 

 Operating point near saturation region gives clipping at the positive peaks




 Operating point near cut-off region gives clipping at the negative peaks




Operating point at the centre of active region is most suitable

Transistor Biasing

 


Fixed bias circuit

 


Voltage divider bias circuit


CE, CC, & CB Amplifiers

 

 Practical common emitter amplifier circuit



Common collector circuit

 

Common base circuit

H-Parameters Representation Of An Amplifier



$$V_i = h_{11} I_i + h_{12} V_o$$

$$I_o = h_{21} I_i + h_{22} V_o$$

Definitions of h-parameter

The parameters in the above equation are defined as follows :

$$h_{11} = \left. \frac{V_i}{I_i} \right|_{V_o=0} = \text{Input resistance with output short-circuited, in ohms.}$$

$$h_{12} = \left. \frac{V_i}{V_o} \right|_{I_i=0} = \text{Fraction of output voltage at input with input open circuited.}$$

This parameter is ratio of similar quantities, hence unitless

$$h_{21} = \left. \frac{I_o}{I_i} \right|_{V_o=0} = \text{Forward current transfer ratio or current gain with output short circuited.}$$

This parameter is a ratio of similar quantities, hence unitless.

$$h_{22} = \left. \frac{I_o}{V_o} \right|_{I_i=0} = \text{Output admittance with input open-circuited, in mhos.}$$

a) With output short circuited :



$h_{11} = h_i$: Input resistance

$h_{21} = h_f$: Short circuit current gain

b) With input open circuited :

$h_{12} = h_r$: Reverse voltage transfer ratio



$h_{22} = h_o$: Output admittance

  

CE

$$V_b = h_{ie} I_b + h_{re} V_c$$



$$I_c = h_{fe} I_b + h_{oe} V_c$$

  

CC

$$V_b = h_{ic} I_b + h_{rc} V_e$$

$$I_e = h_{fc} I_b + h_{oc} V_e$$

  


CB

$$V_e = h_{ib} I_e + h_{rb} V_c$$


$$I_c = h_{fb} I_e + h_{ob} V_c$$

Transistor configurations and their hybrid models

 Small Signal Analysis Of A Junction Transistor



Basic transistor amplifier

 

Transistor amplifier in its h-parameter model

small-signal analysis of a transistor amplifier

$$A_i = -\frac{h_f}{1 + h_o R_L}$$

$$A_{is} = \frac{A_i R_s}{Z_i + R_s}$$

$$Z_i = h_i + h_r A_i R_L = h_i - \frac{h_f h_r}{h_o + Y_L}$$

$$A_v = \frac{A_i R_L}{Z_i}$$

$$A_{vs} = \frac{A_v R_i}{Z_i + R_s} = \frac{A_i R_L}{Z_i + R_s} = \frac{A_{is} R_L}{R_s}$$

$$Y_o = h_o - \frac{h_f h_r}{h_i + R_s} = \frac{1}{Z_o}$$


$$A_p = A_v A_i = A_i^2 \frac{R_L}{Z_i}$$

Guidelines for Analysis of a Transistor Circuit

 
1. Draw the actual circuit diagram.
2. Replace coupling capacitors and emitter bypass capacitor by short circuit.
3. Replace dc source by a short circuit. In other words, short V_{CC} and ground lines.
4. Mark the points B(base), C(collector), E(emitter) on the circuit diagram and locate these points as the start of the equivalent circuit.
5. Replace the transistor by its h-parameter model.

Design Problem

➡ Consider a single stage CE amplifier with $R_s = 1 \text{ k}\Omega$, $R_1 = 50 \text{ K}$, $R_2 = 2 \text{ K}$, $R_C = 1 \text{ K}$, $R_L = 1.2 \text{ K}$, $h_{fe} = 50$, $h_{ie} = 1.1 \text{ K}$, $h_{oe} = 25 \text{ }\mu\text{A/V}$ and $h_{re} = 2.5 \times 10^{-4}$, as shown in Fig.



Approximate H-Model For CE Amplifier

 

Approximate CE model

Current Gain $A_i \approx -h_{fe}$


Input Impedance $R_i \approx h_{ie}$

Voltage Gain : $A_v = \frac{A_i R_L}{R_i} = \frac{A_i R_L}{h_{ie}}$

Output Impedance $Y_o = 0$
 $R_o = \frac{1}{Y_o} = \infty$

$R'_o = R_o \parallel R_L = \infty \parallel R_L = R_L$

Approximate H-Model For CC Amplifier

 

Simplified CC model

Current gain $A_i = \frac{I_o}{I_b} = \frac{-I_e}{I_b} = 1 + h_{fe}$


Input resistance : $R_i = \frac{V_b}{I_b} = h_{ie} + (1 + h_{fe}) R_L$

Voltage gain (A_v) $A_v = \frac{(1 + h_{fe}) R_L}{h_{ie} + (1 + h_{fe}) R_L} \cong 1$

Output resistance R_o $R_o = \frac{V_o}{I_e} = \frac{R_s + h_{ie}}{1 + h_{fe}}$

$R'_o = R_o \parallel R_L = \infty \parallel R_L = R_L$

Approximate H-Model For CB Amplifier

 

Simplified CB model

Current gain $A_i = \frac{h_{fe}}{1 + h_{fe}}$

Input resistance (R_i) $R_i = \frac{h_{ie}}{1 + h_{fe}}$

Voltage gain (A_v) $A_v = \frac{\frac{h_{fe}}{1 + h_{fe}} \times R_L}{\frac{h_{ie}}{1 + h_{fe}}} = \frac{h_{fe} R_L}{h_{ie}}$

Output resistance (R_o) $R_o = \left. \frac{V_o}{I_c} \right|_{V_s=0}$


$R'_o = R_o \parallel R_L = \infty \parallel R_L = R_L$

Design Problem

For the circuit shown in Fig. estimate A_p , A_v , R_i and R_o using reasonable approximations. The *h-parameters* for the transistor are given as

$$h_{fe} = 100 \quad h_{ie} = 2000 \, \Omega \quad h_{re} \text{ is negligible} \quad \text{and} \quad h_{oe} = 10^{-5} \text{ mhos}(\Omega).$$


$$I_b = 100 \, \mu\text{A}.$$

 

CE Amplifier Circuit


Miller's Theorem

 Millers theorem is used to simplify the analysis of a circuit whenever there is a feedback connection in the circuit



(a)


$$Z_1 = \frac{Z}{1-K}$$

 


(b)

$$Z_2 = \frac{Z \cdot K}{K-1}$$

 Analysis of Common Emitter Amplifier with Collector to Base Bias




AC equivalent circuit

 

Design Problems

 - ➡ The Fig. shows common emitter amplifier with collector to base bias. Calculate R_i , R_o , A_v , A_{vs} , A_i . The transistor parameters are $h_{ie} = 1.1 \text{ K}$, $h_{fe} = 50$, $h_{oe} = 25 \times 10^{-6} \text{ A/V}$, $h_{re} = 2.5 \times 10^{-4}$.




Design Problems

➡ For a Common Emitter Configuration, what is the maximum value of R_L for which R_1 differs by not more than 10% of its value at $R_2 = 0$?


$$\begin{array}{ll} h_{ie} = 1100\Omega ; & h_{fe} = 50 \\ h_{re} = 2.50 \times 10^{-4} ; & h_{oe} = 25\mu A/v \end{array}$$

 Analysis Of CE Amplifier With Unbypassed R_E




- ❖ R_E is added to stabilize the gain of the amplifier
- ❖ R_E acts as a feedback resistor
- ❖ The overall gain will reduce with unbypassed R_E

 
AC Equivalent Circuit For CE Amplifier with Unbypassed R_E



 AC Equivalent Circuit For CE Amplifier with R_E Splitted using dual of Miller's Theorem




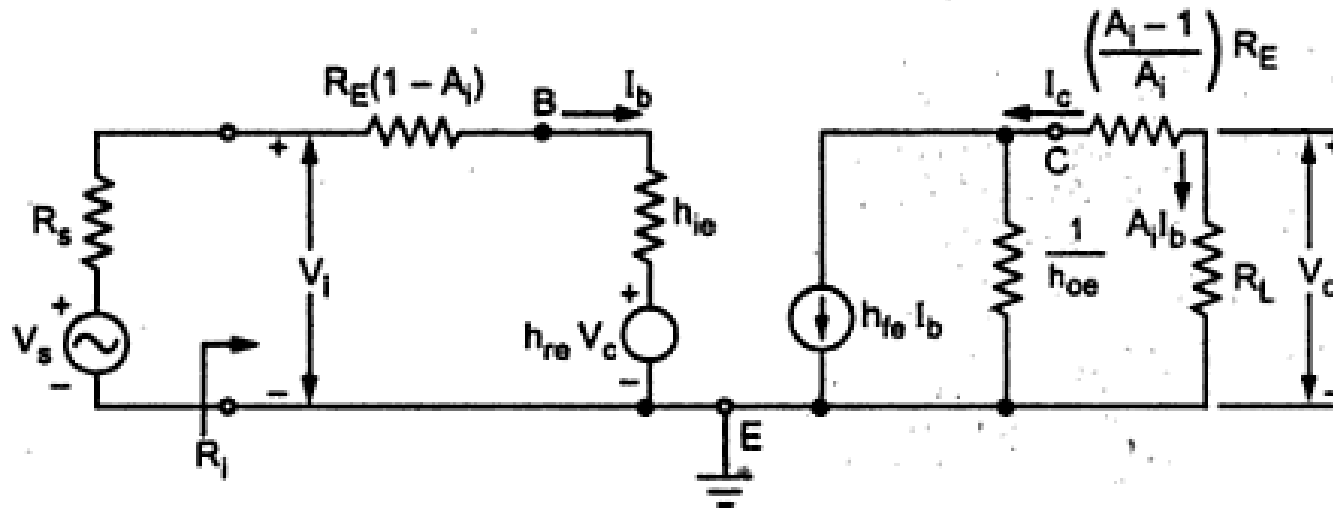h-Parameter Equivalent Circuit (Exact Analysis)



$$A_i = \frac{-h_{fe}}{1 + h_{oe} R'_L} = \frac{-h_{fe}}{1 + h_{oe} \left(R_L + \frac{A_i - 1}{A_i} R_E \right)}$$

 h-Parameter Equivalent Circuit (Approximate Analysis)



Approximate model for CE amplifier with R_E

$$\text{Current gain } A_i = \frac{-I_c}{I_b} = \frac{-h_{fe}I_b}{I_b} = -h_{fe}$$

$$\text{Input resistance } R_i = \frac{V_i}{I_b} = h_{ie} + (1 + h_{fe}) R_E$$


$$\text{Voltage gain } A_v = \frac{A_i R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1 + h_{fe}) R_E}$$

$$\text{Output resistance } R_o = \left. \frac{V_o}{I_o} \right|_{V_s=0}$$

$$R'_o = R_o \parallel R_L = \infty \parallel R_L = R_L$$

Design Problems

 ➡ **Example** Fig. shows a single stage CE amplifier with unbypassed emitter resistance find current gain, input resistance, voltage gain and output resistance. Use typical values of h -parameter




MULTISTAGE AMPLIFIERS


Need For Cascading

- When the amplification of a single stage amplifier is not sufficient, or,
- When the input or output impedance is not of the correct magnitude, for a particular application two or more amplifier stages are connected, in cascade. Such amplifier, with two or more stages is also known as multistage amplifier.

 Block diagram of 2-Stage Cascade Amplifier



Gain of 2-Stage Cascade Amplifier

 

$$G_1 = \frac{P_2}{P_1}; \quad G_2 = \frac{P_3}{P_2}$$

Overall gain

$$G = \frac{P_3}{P_1}$$

$$= \frac{P_2}{P_1} \cdot \frac{P_3}{P_2}$$

$$G = G_1 G_2$$

Decibel Voltage Gain

Cascaded Stages

 


Fig. 2.23 Cascaded stages


$$A = A_1 \times A_2$$

$$A_1 = A_1' + A_2' \text{ (in decibels)}$$

Methods of Inter Stage Coupling


In multistage amplifier, the output signal of preceding stage is to be coupled to the input **circuit** of succeeding stage. For this interstage coupling, different types of coupling elements can be employed. These are :

 
1. RC coupling
2. Transformer coupling
3. Direct coupling



Two stage RC coupled amplifier using transistors

 
Two stage transformer coupled amplifier using transistors



 

Two stage directly coupled amplifier using transistors

 
Frequency Response of 2-Stage RC Coupled Amplifier




Comparison Between Coupling Method

Parameter	RC Coupled	Transformer Coupled	Direct Coupled
Coupling Components	Resistor and Capacitor	Impedance matching transformer	–
Block DC	Yes	Yes	No
Frequency response	Flat at middle frequencies	Not uniform, high at resonant frequency and low at other frequencies	Flat at middle frequencies and improvement in the low frequency response
Impedance matching	Not achieved	Achieved	Not achieved
DC amplification	No	No	Yes
Weight	Light	Bulky and heavy	
Drift	Not present	Not present	Present
Hum	Not present	Present	Not present
Application	Used in all audio small signal amplifiers. Used in record players, tape recorders, public address systems, radio receivers and television receivers.	Used in amplifier where impedance matching is an important criteria. Used in the output stage of the public address system to match the impedance of loudspeaker. Used in the RF amplifier stage of the receiver as a tuned voltage amplifier.	Used in amplification of slow varying parameters and where DC amplification is required.


CE-CE Cascade Amplifier

 

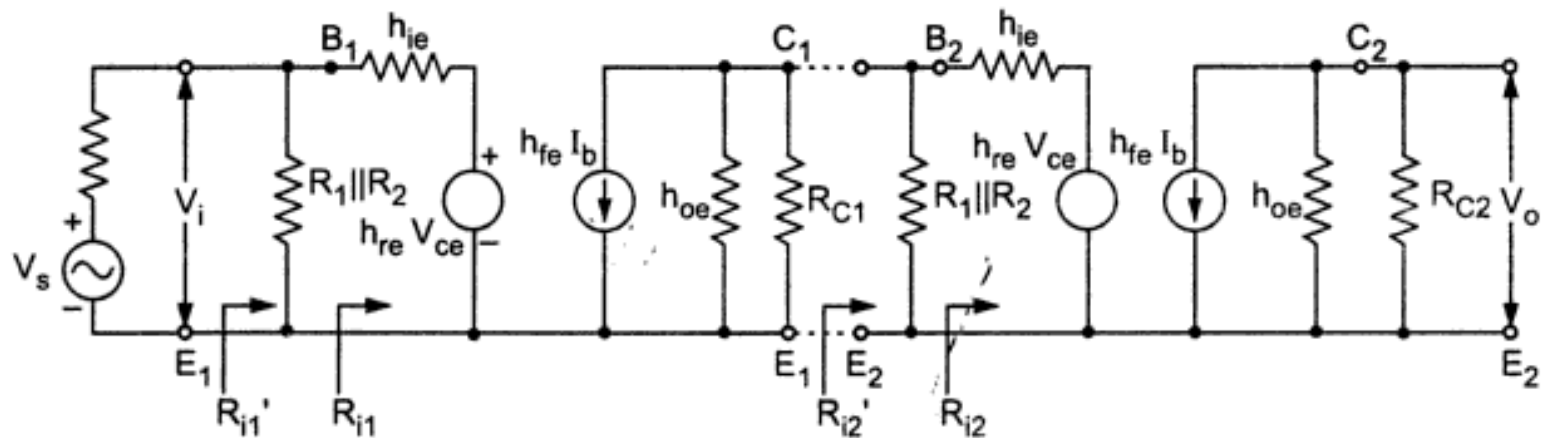
h-parameter equivalent circuit for CE-CE cascade amplifier




Cascode Amplifier

 


AC equivalent circuit

 

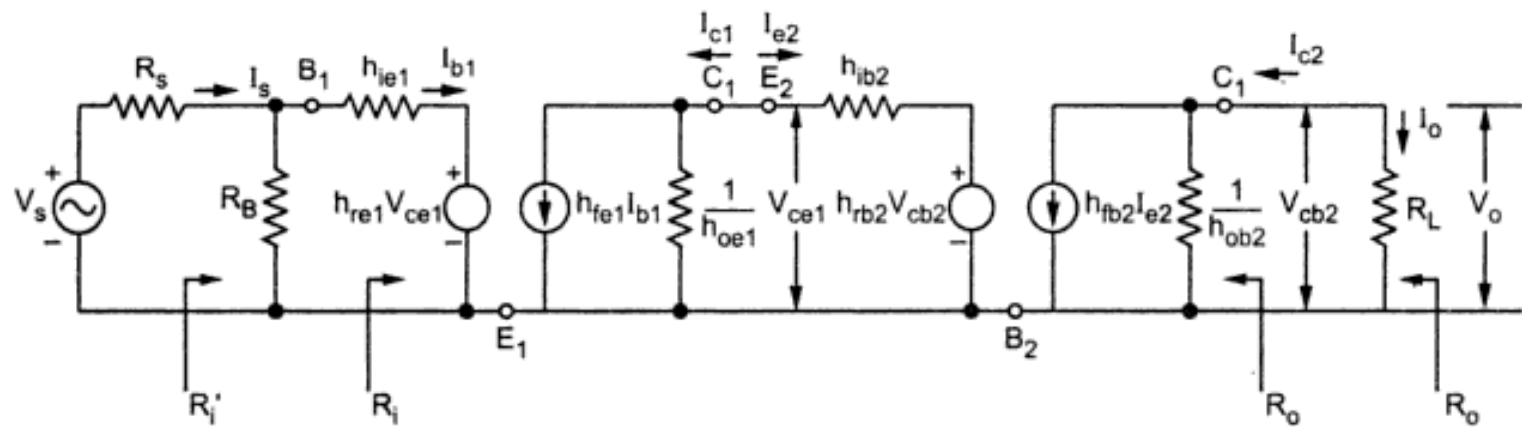
h-parameter equivalent circuit for cascode amplifier



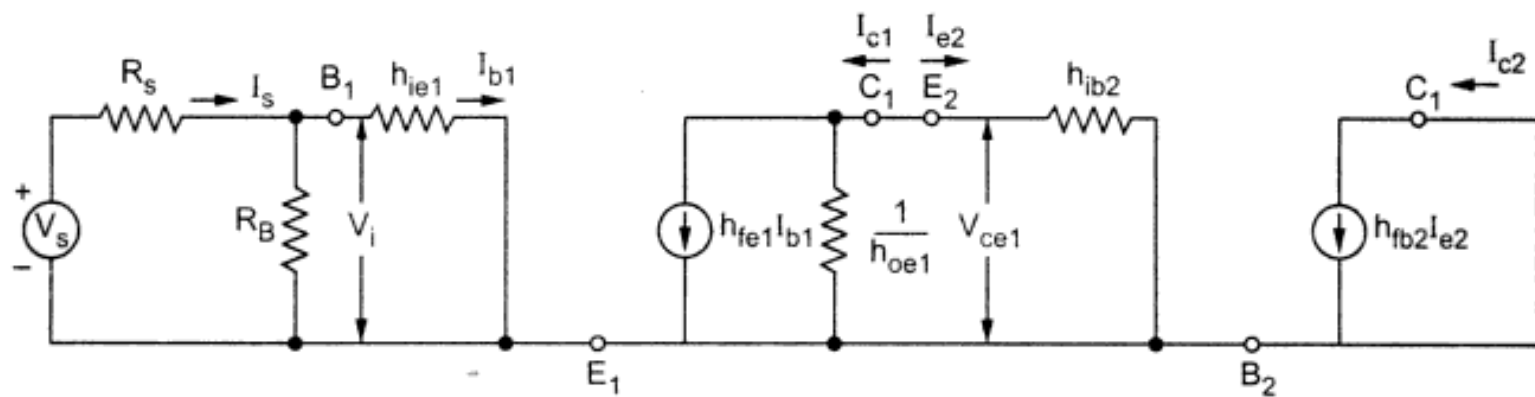
h-parameter equivalent circuit when output shorted



 
h-parameter equivalent circuit when $I_b = 0$



CE-CC Amplifier

 


Analysis for first stage



 



Darlington Transistors

Darlington Transistors $+V_{CC}$

 



AC Equivalent Circuit :

   

 


Parameter	Single stage	Darlington
Input Resistance	$R_i = (1 + h_{fe}) R_E = 168.3 \text{ k} \Omega$	$R_i = \frac{(1 + h_{fe})^2 R_E}{1 + h_{oe} (1 + h_{fe}) R_E} \approx 1.65 \text{ M} \Omega$
Current Gain	$A_i = 1 + h_{fe} = 51$	$A_i = \frac{(1 + h_{fe})^2}{1 + h_{oe} (1 + h_{fe}) R_E} \approx 500$


Bootstrap Emitter Follower

  


$$R_{M1} = \frac{R_3}{1 - A_v}$$

$$R_{M2} = \frac{R_3 A_v}{A_v - 1}$$

 


 


Bootstrapped Darlington circuit

 

 
AC Equivalent circuit for bootstrapped Darlington circuit




(a)

 



(b)

 



(c)

 

(d)

  


  
Bootstrapped Darlington Circuit Alternative Approach



AC equivalent circuit

 
Bootstrapped Darlington Circuit Alternative Approach



 


AC equivalent circuit

 Frequency Response of an RC Coupled Amplifier




Bandwidth of an Amplifier

 

Frequency response, half power frequencies and bandwidth of an RC coupled amplifier

 Hybrid – π Common Emitter Transconductance Model



Hybrid - π C.E BJT Model

UNIT-III


Feedback Amplifiers & Oscillators

CLASSIFICATION OF AMPLIFIERS

- Amplifiers can be classified broadly as,
- 1. Voltage amplifiers.
- 2. Current amplifiers.
- 3. Transconductance amplifiers.
- 4. Transresistance amplifiers.

VOLTAGE AMPLIFIER

 
This circuit is a 2-port network and it represents an amplifier (see in Fig 7.1). Suppose $R_i \gg R_s$, drop across R_s is very small.



Equivalent circuit of voltage amplifiers.

CURRENT AMPLIFIER

 
- An ideal current amplifier is one which gives output current proportional to input current and
- the proportionality factor is independent of R_S and R_L .



TRANSCONDUCTANCE AMPLIFIER

Ideal Transconductance amplifier supplies output current which is proportional to input voltage

 
independently of the magnitude of R_s and R_L .




TRANS RESISTANCE AMPLIFIER

It gives output voltage V_o proportional to I_s , independent of R_s and R_L . For *ideal amplifiers*

$$R_j = 0, R_o = 0$$

 


GENERALIZED BLOCK SCHEMATIC

 

Introduction To Feedback

- The process of injecting a fraction of output energy of some device back to the input is known as **feedback**.
- some of the short comings(drawbacks) of the amplifier circuit are:
 1. Change in the value of the gain due to variation in supplying voltage, temperature or due to components.
 2. Distortion in wave-form due to non linearities in the operating characters of the amplifying device.
 3. The amplifier may introduce noise (undesired signals)
- The above drawbacks can be minimizing if we introduce feedback

basic types of feedback in amplifiers

 

Positive feedback

- When the feedback energy (voltage or current) is in phase with the input signal and thus aids it, it is called *positive feedback*.
- *Both amplifier and feedback network introduce a phase shift of 180° . The result is a 360° phase shift around the loop, causing the feedback voltage V_f to be in phase with the input signal V_{in} .*

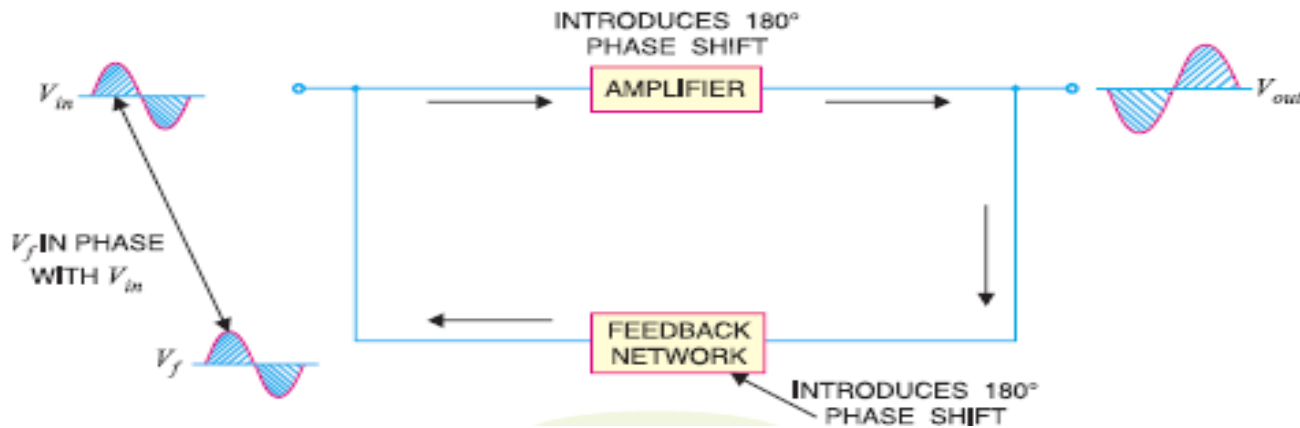


Fig. Block diagram for positive feedback

Negative feedback.

- When the feedback energy (voltage or current) is out of phase with the input signal and thus opposes it, it is called *negative feedback*.
- The amplifier introduces a phase shift of 180° into the circuit while the feedback network is so designed that it introduces no phase shift (*i.e.*, 0° phase shift).
- Negative feedback is also called as *degenerative feedback*.



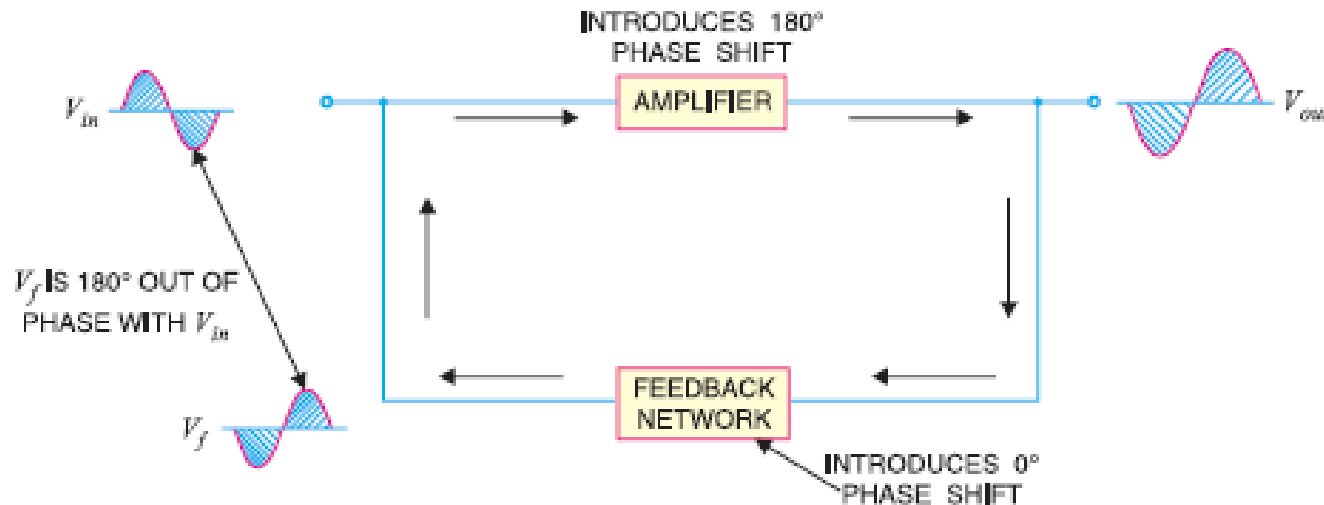


Fig.negative feedback amplifier


CLASSIFICATION OF FEEDBACK AMPLIFIERS

 


voltage series feedback.

 

Voltage shunt Feedback

 

Current Shunt Feedback

 

Current Series Feedback

$$A_{Vf} = \frac{V_o}{V_s}$$

$$A_{If} = \frac{I_o}{I_s}$$

$$G_{Mf} = \frac{I_o}{V_s}$$

$$R_{Mf} = \frac{V_o}{I_s}$$

EFFECT OF NEGATIVE FEEDBACK ON TRANSFER GAIN

❖ REDUCTION IN GAIN

$$A'_v = \frac{A_v}{1 + \beta A_v} \quad \text{Denominator is } > 1. \quad \therefore \quad A'_v < A_v$$

❖ INCREASE IN BANDWIDTH

$$f_H' = f_H (1 + \beta_v A_{v(\text{mid})})$$

$$f_L' = \frac{f_L}{1 + \beta_v A_{v(\text{mid})}}$$

❖ REDUCTION IN DISTORTION


$$\frac{D}{1 + \beta_v A_v} \text{ is } < D$$

❖ FEEDBACK TO IMPROVE SENSITIVITY

❖ FREQUENCY DISTORTION

❖ BAND WIDTH

$$(BW)_f = (1 + \beta A_m) BW$$

 

❖ SENSITIVITY OF TRANSISTOR GAIN

$$\text{Sensitivity} = \frac{\left| \frac{dA_f}{A_f} \right|}{\left| \frac{dA}{A} \right|}$$

$$\text{Density} \quad \boxed{D = (1 + \beta A).$$

❖ REDUCTION OF NONLINEAR DISTORTION

$$B_{2f} = \frac{B_2}{1 + \beta A} \quad B_{2f} < B_2$$


❖ REDUCTION OF NOISE

$$N_F = \frac{N}{1 + \beta A}$$

$N_F < N$. Noise is reduced with negative feedback.

TRANSFER GAIN WITH FEEDBACK

 Consider the generalized feedback amplifier



$$A_f = \frac{A}{1 + \beta A}$$

A_f = gain with feedback.

A = transfer gain without feedback.

If $|A_f| < |A|$ the feedback is called as negative or degenerative, feedback

If $|A_f| > |A|$ the feedback is called as positive or regenerative, feedback

LOOP GAIN

Return Ratio

βA = Product of feedback factor β and amplification factor A is called as *Return Ratio*.

Return Difference (D)


The difference between unity (1) and return ratio is called as *Return difference*.

$$D = 1 - (-\beta A) = 1 + \beta A.$$


CLASSIFICATION OF FEEDBACK AMPLIFIERS

There are four types of feedback,

 
1. Voltage series feedback.
2. Voltage shunt feedback.
3. Current shunt feedback.
4. Current series feedback




voltage series feedback.

 

Voltage shunt Feedback

 

Current Shunt Feedback

 

Current Series Feedback

EFFECT OF FEEDBACK ON INPUT RESISTANCE

Voltage shunt Feedback

$$R'_i = \frac{R_i}{(1 + \beta_i A_i)}$$

Current Shunt Feedback

$$R_{if} = \frac{V_i}{(1 + \beta A_i) I_i} = \frac{R_i}{1 + \beta A_i}$$

voltage series feedback.

$$R_{if} = R_i (1 + \beta A)$$

Current Series Feedback

$$R_{if} = R_i \left(1 + \beta \cdot \frac{V_o}{V_i} \right) = R_i (1 + \beta A_v)$$

EFFECT OF NEGATIVE FEEDBACK ON R_o



voltage series feedback.

$$R_{of}' = \frac{\frac{R_o}{1 + \beta A_v} \times R_L}{\frac{R_o}{1 + \beta A_v} + R_L} = \frac{R_o R_L}{R_o + R_L + \beta A_v R_L}$$

Current Shunt Feedback



$$R_{of}' = R_o (1 + \beta A_i)$$

ANALYSIS OF FEEDBACK AMPLIFIERS

  


Block Schematic

Current shunt feedback.

  


Equivalent circuit.

CURRENT SERIES FEEDBACK

 


VOLTAGE SHUNT FEEDBACK

 


OSCILLATORS

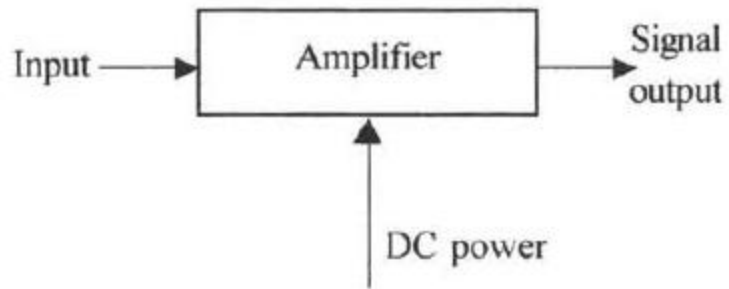Oscillator is a source of AC voltage or current.



(a) Amplifier circuit

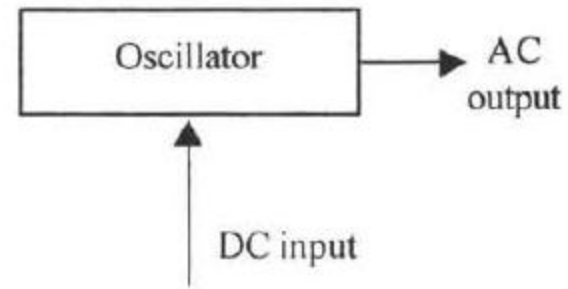

(b) Oscillator circuit

Oscillator Circuit

- Oscillator is an electronic circuit which converts dc signal into ac signal.
- Oscillator is basically a positive feedback amplifier with unity loop gain.
- For an inverting amplifier- feedback network provides a phase shift of 180° while for non-inverting amplifier- feedback network provides a phase shift of 0° to get positive feedback .

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta} \quad \text{If } \beta A = 1 \text{ then } V_o = \infty ; \quad \text{Very high output with zero input.}$$


Use positive feedback through frequency-selective feedback network to ensure sustained oscillation at ω_0

Use of Oscillator Circuits

- ❖ Clock input for CPU, DSP chips ...
- ❖ Local oscillator for radio receivers, mobile receivers, etc
- ❖ As a signal generators in the lab
- ❖ Clock input for analog-digital and digital-analog converters

Oscillators

 - If the feedback signal is not positive and gain is less than unity, oscillations dampen out.
- If the gain is higher than unity then oscillation saturates.



Type of Oscillators

Oscillators can be categorized according to the types of feedback network used:

- RC Oscillators: Phase shift and Wien Bridge Oscillators
- LC Oscillators: Colpitt and Hartley Oscillators
- Crystal Oscillators

There are two types of oscillators circuits:

1. Harmonic Oscillators

2. Relaxation Oscillators


PERFORMANCE MEASURES OF OSCILLATOR CIRCUITS:

- ❖ ***Stability:***
- ❖ ***Amplitude stability:***
- ❖ ***Output Power:***
- ❖ ***Harmonics:***

Total phase shift = 360° ($180 + 180$). Therefore, to get sustained oscillations,

1. The loop gain must be unit 1.
2. Total Loop phase shift must be 0° or 360° . (Amplifier circuit produces 180° phase shift and feedback network another 180°).

SINUSOIDAL OSCILLATORS

 


Block schematic

BARKHAUSEN CRITERION


$$|\beta A| = 1 \text{ and phase of } -A\beta = 0.$$

R - C PHASE-SHIFT OSCILLATOR

 

(a)

Transistor phase shift oscillator.

 

R - C Equivalent circuit.


$$h_{fe} K > 4K^2 + 23K + 29$$

$$K < 2.7$$


$$h_{fe} > 4K + 23 + \frac{29}{K}$$

$$h_{fe} > 44.5$$


A GENERAL FORM OF LC OSCILLATOR CIRCUIT

 

(a)

 

(b)

 


$$-A\beta = \frac{A_v X_1}{X_2}.$$

- $A\beta$ must be positive, and at least unity in magnitude. Then X_1 and X_2 must have the same sign.

So if X_1 and X_2 are capacitive, X_3 should be inductive and vice versa.

If X_1 and X_2 are capacitors, the circuit is called ***Colpitts Oscillator***

 
If X_1 and X_2 are inductors, the circuit is called ***Hartely Oscillators***



(a) Colpitts oscillator

$$f = \frac{1}{2\pi\sqrt{LC_T}}$$


where $C_T = \frac{C_1 C_2}{C_1 + C_2}$

 



(b) Hartely oscillator circuit


$$f = \frac{1}{2\pi\sqrt{(L_1 + L_2)C_3}}$$

Wien bridge oscillator circuit.

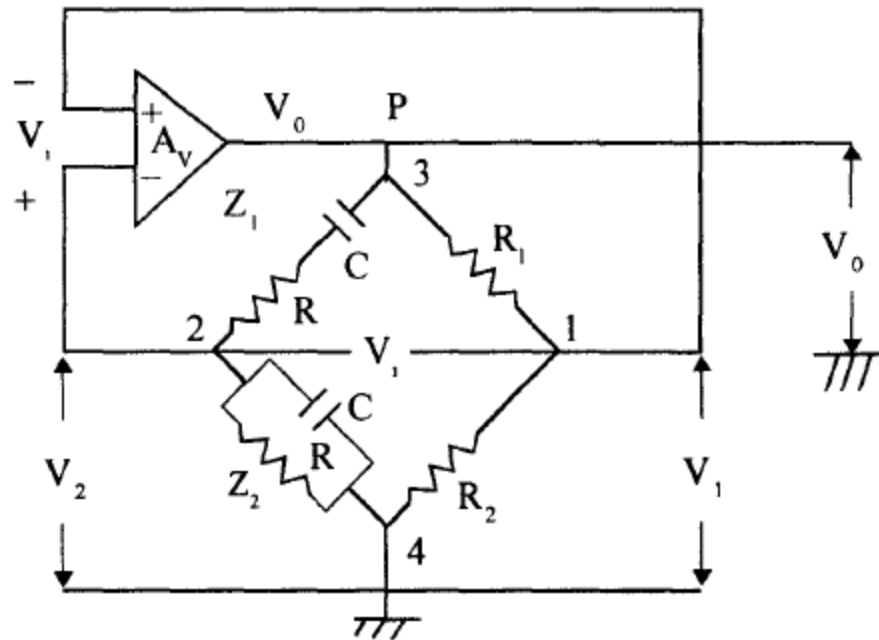

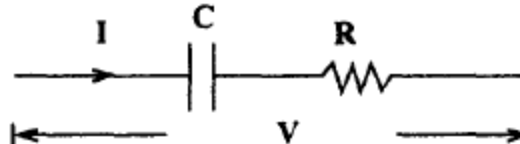Lead Network :  Same I is passing through C and R.
So I leads V.

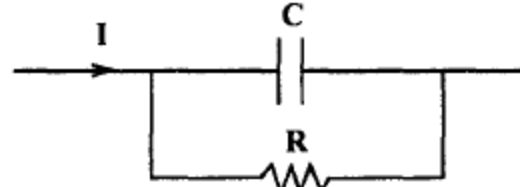Lag Network :  I lags with respect to V.


 


Wien Bridge oscillator circuit.

$$f = \frac{1}{2\pi RC}$$

$$h_{fe} = 4k + 23 + \frac{29}{K}.$$

CRYSTAL OSCILLATORS

  

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$


Transistor Audio Power Amplifier

- A transistor amplifier which raises the power level of the signals that have audio frequency range is known as **transistor audio power amplifier**.
- A transistor that is suitable for power amplification is generally called a *power transistor*.
- The typical power output rating of a power amplifier is 1W or more.

Factors to be considered in large signal amplifiers:

- Output power
- Distortion
- Operating region
- Thermal considerations
- Efficiency (η)

block diagram of an audio amplifier

 

Difference Between Voltage and Power Amplifiers

S. No.	Particular	Voltage amplifier	Power amplifier
1.	β	High (> 100)	low (5 to 20)
2.	R_c	High (4 – 10 k Ω)	low (5 to 20 Ω)
3.	<i>Coupling</i>	usually R – C coupling	Invariably transformer coupling
4.	<i>Input voltage</i>	low (a few mV)	High (2 – 4 V)
5.	<i>Collector current</i>	low (≈ 1 mA)	High (> 100 mA)
6.	<i>Power output</i>	low	high
7.	<i>Output impedance</i>	High (≈ 12 k Ω)	low (200 Ω)

Performance Quantities of Power Amplifiers

(i) Collector efficiency

*The ratio of a.c. output power to the zero signal power (i.e. d.c. power) supplied by the battery of a power amplifier is known as **collector efficiency**.*

(ii) Distortion

*The change of output wave shape from the input wave shape of an amplifier is known as **distortion**.*

(iii) Power dissipation capability


*The ability of a power transistor to dissipate heat is known as **power dissipation capability**.*

Classification of Power Amplifiers

- Class A: It is one, in which the active device conducts for the full 360° .
- Class B: Conduction for 180° .
- Class C: Conduction for $< 180^\circ$.
- Class AB :Conduction angle is between 180° . and 360° .
- Class D: These are used in *transmitters because their efficiency is high: 100%*.
- Class S:Switching regulators are based on class'S' operation.

Class A power amplifier

 - If the collector current flows at all times during the full cycle of the signal, the power amplifier is known as **class A power amplifier**.
- If the Q point is placed near the centre of the linear region of the dynamic curve, class A operation results. Because the transistor will conduct for the complete 360°, distortion is low for small signals and conversion efficiency is low.



Types of class-A power Amplifiers

1. Series fed

There is no transformer in the circuit. R_L is in series with V_{cc} . There is DC power drop across R_L . Therefore efficiency = 25% (maximum).

2. Transformer coupled

- The load is coupled through a transformer. DC drop across the primary of the transformer is negligible. There is no DC drop across R_L . Therefore efficiency = 50% maximum.

Series Fed class-A power Amplifier

 


Fig.(a)Series fedClass A power amplifier circuit

 


Fig.(b)Transter curve

Transformer Coupled class-A power Amplifier

 
 


Fig.(a)Transformer Coupled Class A power amplifier circuit


Fig.(b)Transfer curve

Important Points About Class A Power Amplifier

- A transformer coupled class A power amplifier has a maximum collector efficiency of **50%**
- The power dissipated by a transistor is given by :
$$P_{dis} = P_{dc} - P_{ac}$$
- When no signal is applied to a class A *power amplifier*, $P_{ac} = 0$.
$$\therefore P_{dis} = P_{dc}$$
- When a class A *power amplifier* is used in the *final stage*, it is called **single ended class A power amplifier**.

Class B power amplifier

 - If the collector current flows only during the positive half-cycle of the input signal, it is called a **class B power amplifier**.
- For class B operation the Q point is set near cutoff. So output power will be more and conversion efficiency is more. Conduction is only for 180



Transfer curve

Types of class-B power Amplifiers

- **Push-Pull Amplifier**

The standard class B push-pull amplifier requires a centre tapped transformer

- **Complimentary Symmetry Circuits (Transformer Less Class B Power Amplifier)**

Complementary symmetry circuits need only one phase

They don't require a centre tapped transformer.

Advantages & Disadvantages of Class B power Amplifier


Advantages

1. More output power; efficiency = 78.5%. Max.
2. Efficiency is higher. Since the transistor conducts only for 180° , when it is not conducting, it will not draw DC current.
3. Negligible power loss at no signal.



Disadvantages:

1. Supply voltage V_{cc} should have good regulation. Since if V_{cc} changes, the operating point changes (Since I_c changes). Therefore transistor may not be at cut off.
2. Harmonic distortion is higher. (This can be minimized by pushpull connection).

Class B Push-Pull Amplifier

 

Push Pull amplifier circuit

  

Complimentary Symmetry Circuits (Transformer Less Class B Power Amplifier)

 


Fig. Complimentary Symmetry circuit

Advantages & Disadvantages of Class B complementary power Amplifier

- **Advantages**

- (i) This circuit does not require transformer. This saves on weight and cost.
- (ii) Equal and opposite input signal voltages are not required.

- **Disadvantages**

- (i) It is difficult to get a pair of transistors (nnp and pnp) that have similar characteristics.
- (ii) We require both positive and negative supply voltages.

Differences between class-A & B power Amplifiers

Class A	Class B
Less power	More power
Lesser η	More η upto 78.5%
Less Harmonic distortion	Harmonic distortion is more

Heat Sinks

- The metal sheet that serves to dissipate the additional heat from the power transistor is known as **heat sink**.
- The purpose of heat sinks is to keep the operating temperature of the transistor low, to prevent thermal breakdown.
- Almost the entire heat in a transistor is produced at the collector-base junction. If the temperature exceeds the permissible limit, this junction is destroyed and the transistor is rendered useless.
- Most of power is dissipated at the collector-base junction. This is because collector-base voltage is much greater than the base-emitter voltage, although currents through the two junctions are almost the same.

Mathematical Analysis Of Heat Sinks

$$\theta_{ja} = \theta_{jc} + \theta_{cn} + \theta_{na}$$

$$\theta_{jc} = (T_j - T_c) / P$$

$$\theta_{cs} = (T_c - T_s) / P$$

$$\theta_{sa} = (T_s - T_a) / P$$

θ_{ja} = Junction to ambient thermal resistance

θ_{jc} = Junction to casing thermal resistance

θ_{cs} = Casing to heat sink thermal resistance

θ_{sa} = Heat sink to ambient thermal resistance

T_j = Average junction temperature

T_c = Average case temperature

T_{sa} = Average heat sink temperature

T_a = Ambient temperature

P = Power dissipated in Watts.

Classification of heat Sinks


1. Low Power Transistor Type.
2. High Power Transistor Type.

Low Power Transistor Type.


- Low Power Transistors can be mounted directly on the metal chassis to increase the heat dissipation capability. The casing of the transistor must be insulated from the metal chassis to prevent shorting.
- Beryllium oxide insulating washers are used for insulating casing from the chassis. They have good thermal conductivity.
- Zinc oxide film silicon compound between washer and chassis, improves the heat transfer from the semiconductor device to case to the chassis.

High Power Transistor Type.

 - re TO-3 and TO-66 types. These are diamond shaped. For power transistors, usually, the ease itself in the collector convention and radiation
- Finned aluminium heat sinks yield the best heat transfer per unit cost.



Fin-type heat sink

 

Power transistor heat sink

Alternate Methods to prevent Thermal breakdown

- It should be realized that the use of heat sink alone may not be sufficient to prevent thermal runaway under all conditions. In designing a transistor circuit, consideration should also be given to the choice of
 - (i) operating point
 - (ii) ambient temperatures which are likely to be encountered and
 - (iii) the type of transistor e.g. metal case transistors are more readily cooled by conduction than plastic ones.

Tuned Amplifiers

- Amplifiers which amplify a specific frequency or narrow band of frequencies are called **tuned amplifiers**.
- Tuned amplifiers are mostly used for the amplification of high or radio frequencies.
- It offers a very high impedance at *resonant frequency* and very small impedance at all other frequencies.


Advantages of Tuned Amplifiers

- 1. Small power loss.**
- 2. High selectivity**
- 3. Smaller collector supply voltage**
- 4. Used in RF amplifiers,
Communication receivers, Radar ,
Television ,I.F amplifiers**
- 5. harmonic distortion is very small**

Why not Tuned Circuits for Low Frequency Amplification?


- *Low frequencies are never single*
- *High values of L and C .*

Classification

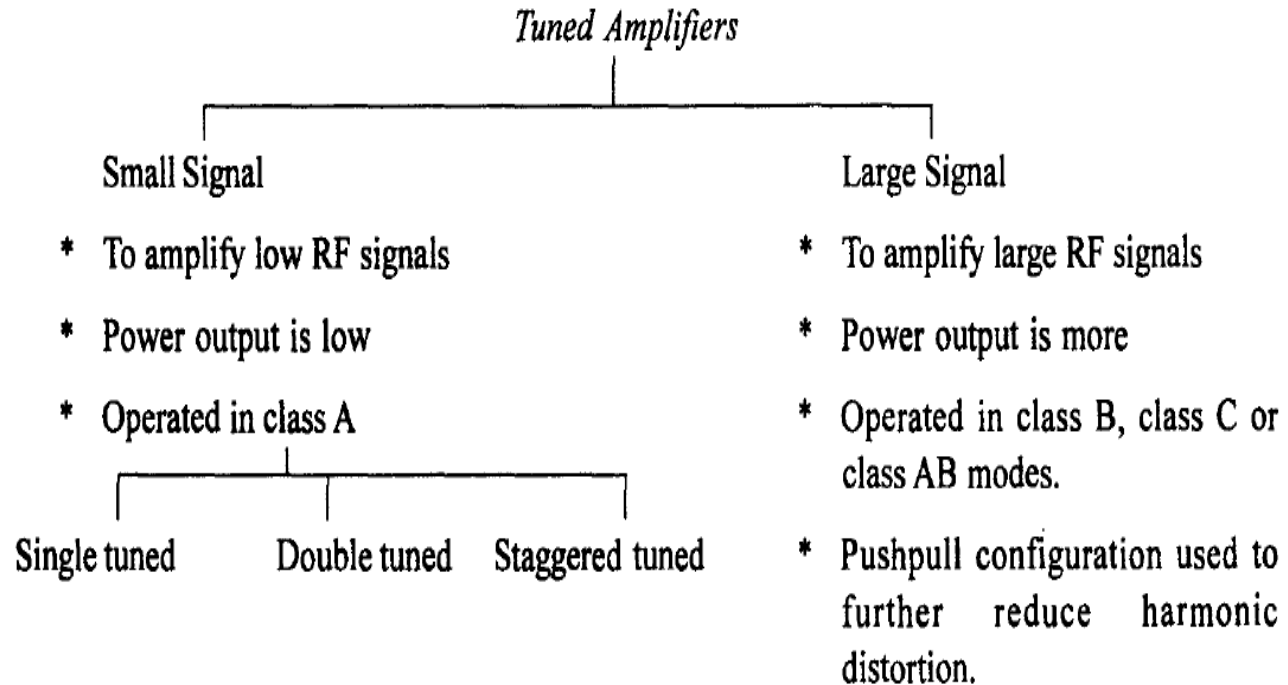


Single Tuned Amplifier

 
- Uses one parallel tuned circuit as the load IZI in each stage and all these tuned circuits in different stages are tuned to the same frequency. To get large A_v or A_p , multistage amplifiers are used. But each stage is tuned to the same frequency, one tuned circuit in one stage.



 
Single Tuned Capacitive Coupled Amplifier



 
Equivalent circuit of Single Tuned Capacitive Coupled Amplifier



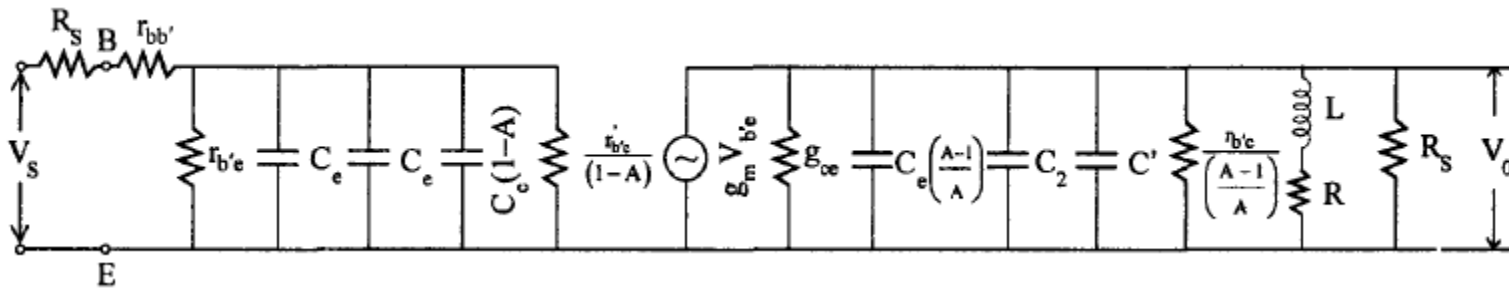
Equivalent circuit of Single Tuned Capacitive Coupled Amplifier (applying Miller's Theorem)




Simplified equivalent circuit

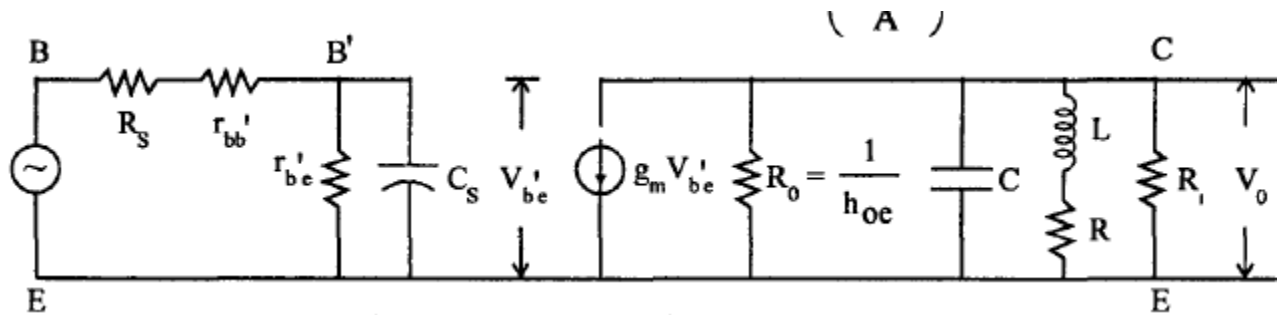


Simplified output circuit

 

 
Tapped Single Tuned Capacitance Coupled Amplifier



 
Equivalent Circuit on the Output Side of the I Stage



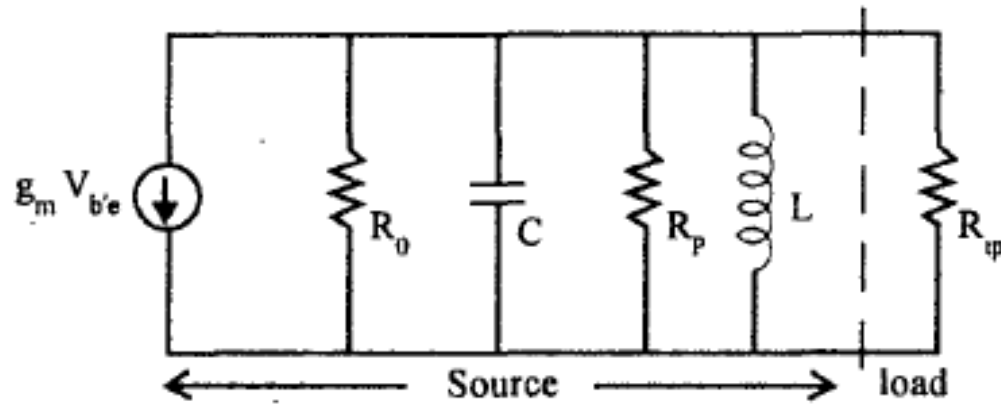
Equivalent circuit of Tapped Single Tuned Capacitance Coupled Amplifier



Equivalent circuit after simplification

 


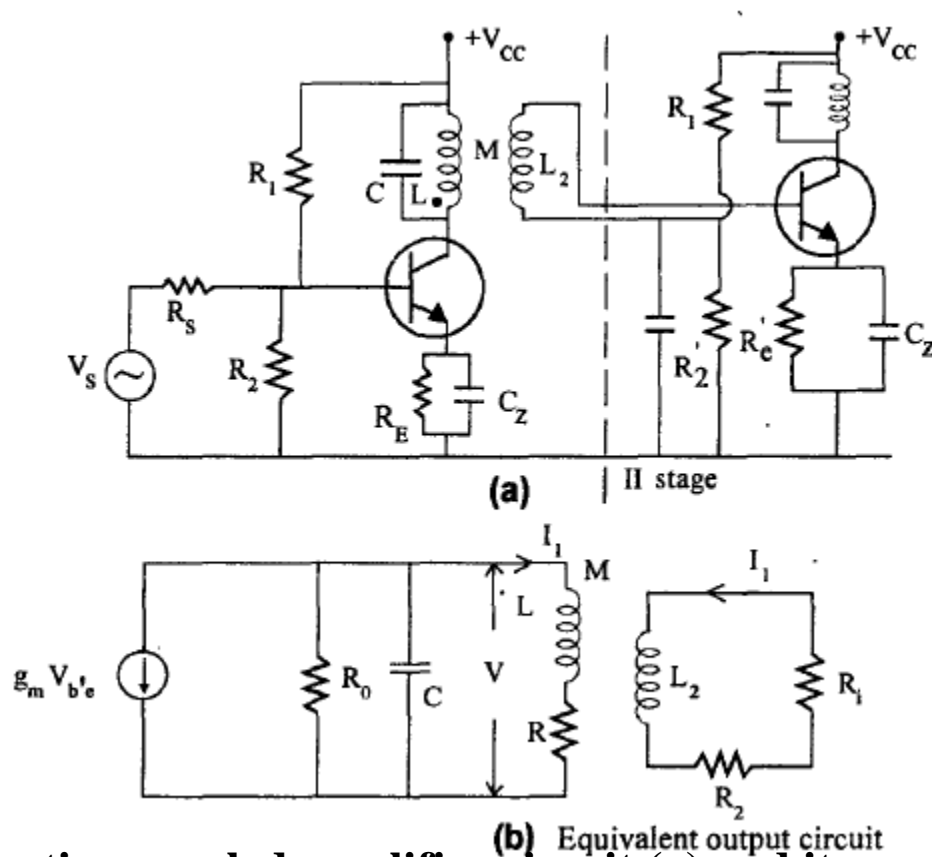Single Tuned Transformer Coupled or Inductively Coupled Amplifier




Inductive coupled amplifier circuit (a) and its equivalent (b)

 
Single Tuned Transformer Coupled or Inductively Coupled Amplifier



(a) Equivalent circuit

 

(b) Simplified circuit

 


©Equivalent circuit


Double Tuned Amplifier

- It uses two inductively coupled tuned circuits, for each stage of the amplifier. Both the tuned circuits are tuned to the same frequency, two tuned circuits in one stage, to get sharp response.
- It provides larger 3-db band width than the single tuned amplifier. Therefore Gain x Bandwidth product is more.
- It provides gain - frequency curve having steeper sides and flatter top.


Double tuned amplifier circuit

 

 Double tuned amplifier Equivalent circuit




(a) Equivalent circuit

 

 (b) Modified circuit

Stagger Tuned Amplifier

- This circuit uses number of single tuned stages in cascade. The successive tuned circuits are tuned to slightly different frequencies.



Variation of A_v with f

Stability Considerations

- Thermal Effects
- Bias Considerations: Distortion in Audio amplifiers and other types of circuits depends on :
 - (i) Input signal level (in mv)
 - (ii) Source Resistance
 - (iii) Bias Conditions
 - (iv) Type of output load and its impedance
 - (v) Loading effect.

Relation between hybrid- π and h-parameters

Sr. No	Parameter Relation
1	$g_{m1} = \frac{I_C}{V_T}$
2	$r_{b'e} = \frac{h_{fe}}{g_m}$
3	$r_{bb'} = h_{ie} - r_{b'e}$
4	$r_{b'c} = \frac{r_{b'e}}{h_{re}}$
5	$g_{ce} = \frac{1}{r_{ce}} = h_{oe} - g_{b'e} h_{fe}$

Hybrid - π Parameter Values

Typical values of the hybrid- π parameter at $I_C = 1.3$ mA are as follows :


$$\begin{aligned} g_m &= 50 \text{ mA/V} & r_{bb'} &= 100 \text{ } \Omega & r_{b'e} &= 1 \text{ k}\Omega \\ r_{ce} &= 80 \text{ k}\Omega & C_c &= 3 \text{ pf} & C_e &= 100 \text{ pf} \\ r_{b'c} &= 4 \text{ M}\Omega \end{aligned}$$

These values depend upon :

1. Temperature
2. Value of I_C

The Hybrid- π Capacitances

$$C_e = C_{De} + C_{Te} \approx C_{De}$$

 

$$Q_B = \frac{1}{2} p'(0) A W q$$

$$\begin{aligned} I &= -Aq D_B \frac{dp'}{dx} \\ &= Aq D_B \frac{p'(0)}{W} \end{aligned}$$

Combining equations (1) and (2) we get

$$Q_B = \frac{IW^2}{2 D_B}$$

$$\begin{aligned} C_{De} &= \frac{dQ_B}{dV} = \frac{W^2}{2 D_B} \frac{dI}{dV} \\ &= \frac{W^2}{2 D_B} \frac{1}{r_e} \end{aligned}$$


$r_e = dV/dI = V_T/I_E$ is the emitter junction incremental resistance.

$$C_{De} = \frac{W^2 I_E}{2 D_B V_T}$$


$$= g_m \frac{W^2}{2 D_B}$$

$$C_e \approx \frac{g_m}{2 \pi f_T}$$

 CE Short-Circuit Current Gain using Hybrid π Model




 The hybrid- π circuit for a single transistor with a resistive load R_L





Simplified hybrid- π model for short circuit CE transistor


Simple view of a MOS

 


MOSFET Structure

  

Substrate connection.

 




(a)

 


(b)


(a) Simple PMOS device, (b) PMOS inside an n -well.

MOS symbols.

   


 


(a)

 

(b)

 


(c)

 



(d)

 (a) A MOSFET driven by a gate voltage, (b) formation of depletion region, (c) onset of inversion, (d) formation of inversion layer.

$$V_{TH} = \Phi_{MS} + 2\Phi_F + \frac{Q_{dep}}{C_{ox}},$$



  
Implantation of p^+ dopants to alter the threshold.



Formation of inversion layer in a PFET.


Derivation of I/V Characteristics

$$I = Q_d \cdot v.$$

 


 (a) A semiconductor bar carrying a current I , (b) snapshots of the carriers one second apart.

Channel charge with (a) equal source and drain voltages, (b) unequal source and drain voltages.




(a)

 

(b)
 
$$I_D = WC_{ox}[V_{GS} - V(x) - V_{TH}]\mu_n \frac{dV(x)}{dx},$$




Drain current versus drain-source voltage in the triode region.


$$I_{D,max} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2.$$

$$I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_{DS},$$

 
$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}.$$





Linear operation in deep triode region.

 

 With the condition $V_{DS} \ll 2(V_{GS} - V_{TH})$, we say the device operates in deep triode region.



Saturation of drain current.

  


Pinch-off behavior.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2,$$

$$I_D = -\mu_p C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$
 
$$I_D = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2.$$



Saturated MOSFETs operating as current sources.


$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}, \text{const.}}$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}).$$


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$= \frac{2I_D}{V_{GS} - V_{TH}}.$$

 
MOS transconductance as a function of overdrive and drain current.



W/L Constant

 


W/L Constant

 


I_D Constant

NMOS device with negative bulk voltage.

 


 Variation of depletion region charge with bulk voltage.



Channel-Length Modulation
 
$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}),$$




Finite saturation region slope resulting from channel-length modulation.

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})(1 + \lambda V_{DS}).$$


$$= \sqrt{\frac{2\mu_n C_{ox} (W/L) I_D}{1 + \lambda V_{DS}}},$$

Subthreshold Conduction

 
$$I_D = I_0 \exp \frac{V_{GS}}{\zeta V_T},$$




MOS subthreshold char-

 


(a)

 

(b)

 

(c)

 


(d)

(a) Basic MOS small-signal model, (b) channel-length modulation represented by a dependent current source, (c) channel-length modulation represented by a resistor, (d) body effect represented by a dependent current source.

$$\begin{aligned}
r_O &= \frac{\partial V_{DS}}{\partial I_D} \\
&= \frac{1}{\partial I_D / \partial V_{DS}}. \\
&= \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} \\
&\approx \frac{1}{\lambda I_D}.
\end{aligned}$$

$$\begin{aligned}
g_{mb} &= g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \\
&= \eta g_m,
\end{aligned}$$

Complete MOS small-signal model.

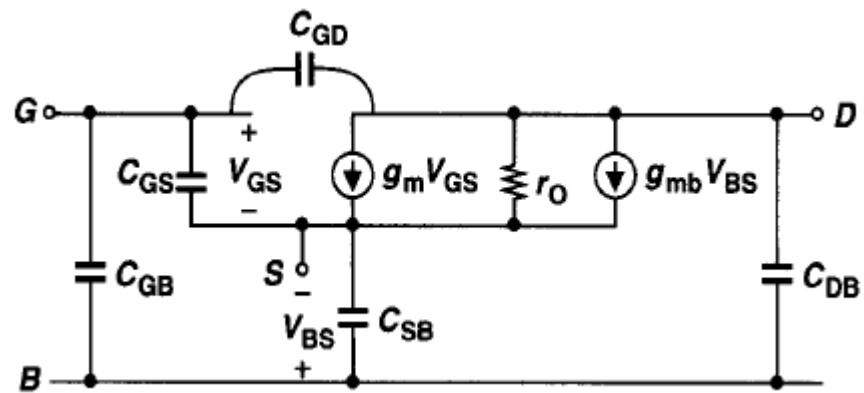

R15**Code No: 124CV****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, April - 2018****ELECTRONIC CIRCUIT ANALYSIS****(Common to ECE, EIE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Draw the circuit diagram of Darlington Pair. [2]
- b) What is the expression for harmonic distortion in single stage amplifiers? [3]
- c) Define Gain-Bandwidth Product in detail. [2]
- d) Draw the Small signal model of MOS amplifier. [3]
- e) List out the Conditions for Oscillations in detail. [2]
- f) Explain different Classification of Feedback Amplifiers. [3]
- g) Define Thermal Stability and Thermal Runway. [2]
- h) What is Heat sink and explain its advantages? [3]
- i) Define Q factor. [2]
- j) What is the expression for harmonic distortion in tuned amplifiers? [3]

PART-B**(50 Marks)**

- 2.a) Discuss about effect of C_b on frequency response of RC coupled amplifier.
- b) Draw the circuit diagram of Direct Coupled Amplifier and explain its operation in detail. [5+5]

OR

- 3.a) With a neat circuit diagram. Explain about Boot-Strap emitter follower amplifier.
 - b) Derive the Analysis of CE amplifier with Emitter Resistance and explain its operation along with circuit diagram. [5+5]
- 4.a) Find the voltage gain, input and output resistances of a emitter follower at high Frequencies.
 - b) A common source amplifier uses a MOSFET with the following parameters $g_m=1.5\text{mA/V}$, $r_d=40\text{kohms}$, $C_{gs}=3\text{pF}$, $C_{ds}=1\text{pF}$, $C_{gd}=3.2\text{pF}$. The value of $R_d=200\text{Kohms}$. The amplifier operates at 30KHz. Find Voltage gain, input resistance, output resistance and input capacitance. [5+5]

OR

- 5.a) Draw the circuit diagram of Common source amplifier with Resistive load and explain its operation.
- b) Derive the expression for f_T of a transistor in detail. [5+5]

- 6.a) Derive the expression for frequency of oscillation of BJT RC phase-shift oscillator with necessary explanation.
- b) What is the equivalent circuit of a crystal? Derive the expressions for series and parallel resonances. A crystal oscillator has the following parameters: $L=0.33\text{H}$, $C=0.065\text{pF}$, $C_m=1.0\text{pF}$ and $R=5.5\text{ k ohm}$.
- i) Find the series resonant frequency.
- ii) Find the Q of the crystal. [5+5]

OR

- 7.a) Draw the block diagrams of four types of negative feedback amplifier circuits and explain the advantages and disadvantages with necessary derivations.
- b) Explain why RC Phase shift oscillators are not used at high frequencies. [5+5]
- 8.a) Explain the operation of a class A push-pull power amplifier and list out its advantages and disadvantages.
- b) A single transistor is operating as an ideal class B amplifier with a 10-K load. A dc meter in the collector circuit reads 8mA. How much signal power is delivered to the load? [5+5]

OR

- 9.a) Draw the circuit diagram of Complementary Symmetry Class B Push-Pull Amplifier and explain its operation.
- b) List out the few difference between Class A, Class B and Class AB Push-Pull amplifiers with examples. [5+5]

- 10.a) What is a stagger tuned amplifier? Explain its advantages and disadvantages.
- b) Write short notes on Small Signal Tuned Amplifiers in detail. [5+5]

OR

- 11.a) What are the different Effect of Cascading Single Tuned Amplifiers on Bandwidth in detail.
- b) Explain the concept of Stability of Tuned Amplifiers with one example. [5+5]

---ooOoo---

Code No: 124CV**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, May - 2017****ELECTRONIC CIRCUIT ANALYSIS****(Common to ECE, EIE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Why is a CE amplifier widely used? List down its main limitations. [2]
- b) What are the typical values of h-parameters of CE configuration? [3]
- c) What is f_T of a BJT? [2]
- d) State Miller's theorem. [3]
- e) Compare Frequency stability of crystal oscillator, RC and LC oscillators. [2]
- f) What are the advantages of negative feedback? [3]
- g) What is Class-A power amplifier? [2]
- h) Classify power Amplifiers. [3]
- i) What is effect of cascading on single tuned amplifier? [2]
- j) What is stagger tuned amplifier? [3]

PART-B**(50 Marks)**

- 2.a) Draw the CE amplifier with un bypassed emitter resistance and derive expression for R_i and A_v .
- b) A transistor in CB circuit has the following set of 'h' parameters. $h_{ib} = 20$, $h_{rb} = 0.98$, $h_{fb} = 3 \times 10^{-4}$, $h_{ob} = 0.5 \times 10^{-6}$. Find the values if R_i , R_o , A_i and A_v , if $R_s = 600\Omega$ and $R_L = 1.5 k\Omega$. [5+5]

OR

- 3.a) Draw the Darlington circuit and derive the expressions for the overall current gain, voltage gain, input impedance and output impedance.
- b) With the help of a neat circuit diagram describe the working of a cascade amplifier. [5+5]
- 4.a) Draw the hybrid-II model of common emitter configuration and describe each component in the II-model.
- b) Derive the equation for voltage gain bandwidth product for CE amplifier. [5+5]

OR

- 5.a) Discuss the effect of different types of loads to a common source MOS amplifier.
- b) Draw the CS FET amplifier equivalent circuit looking into the drain and find its gain and output impedance. [5+5]

- 6.a) Explain the principle of negative feedback in amplifiers. Show quantitatively the effect of negative feedback on (i) Gain (ii) Stability (iii) Noise (iv) Distortion.
b) Show that current-series negative feedback increases the input impedance and increases the output impedance. [5+5]

OR

7. Starting from the description of a generalized Oscillator, derive the expression for frequency of Oscillation in a Colpitts Oscillator. [10]
8. Describe the operation of Class B Push pull amplifier and show how even harmonics are eliminated. [10]

OR

- 9.a) Derive the expression for maximum conversion efficiency for a simple series fed Class A power amplifier.
b) A push pull amplifier utilizes a transformer whose primary has a total of 160 turns and whose secondary has 40 turns. It must be capable of delivering 40W to an $8\ \Omega$ load under maximum power conditions. What is the minimum possible value of V_{cc} ? [5+5]

10. Explain the operation of doubled-tuned amplifier with a neat circuit diagram and derive the equation for its gain bandwidth product. [10]

OR

11. What is the effect of cascading double tuned Amplifiers on Band width? Derive the related equations. [10]

---ooOoo---

Code No: 124CV

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year II Semester Examinations, December - 2017****ELECTRONIC CIRCUIT ANALYSIS****(Common to ECE, EIE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**


- 1.a) Draw a small signal low frequency model of a transistor. [2]
- b) State dual of Miller's theorem and also write its applications. [3]
- c) What is unity crossover frequency? [2]
- d) Define a short circuit gain of a transistor in CE configuration at high frequencies. [3]
- e) What is effect of negative feedback on amplifier gain? [2]
- f) State Barkhausen criterion of oscillator. [3]
- g) Why heat sinks are needed? [2]
- h) What is mean by crossover distortion? [3]
- i) Define Q factor of tuned amplifier. [2]
- j) What are the limitations of Single tuned amplifier? [3]

PART-B**(50 Marks)**

- 2.a) The h parameters of a transistor used in single stage amplifier circuit are $h_{ic} = 1100$, $h_{rc} = 1$, $h_{fe} = 51$ and $h_{oc} = 25\mu A$. Determine the amplifier parameters for CC configuration when $R_S = R_L = 10K$.
- b) For any single-stage amplifier express input resistance in terms of current gain and h-parameters only. [5+5]

OR

- 3.a) Derive the bandwidth of a multistage amplifier, assuming that each stage has same upper and lower cut off frequencies.
- b) For the two stage amplifier of the figure 1, calculate the input and output impedance, and the individual and overall voltage gains. Assume $h_{fe} = 50$, $h_{ie} = 1.1k\Omega$, $h_{re} = h_{oc} = 0$. [5+5]

 www.ManaResults.co.in**Figure: 1**

- 4.a) A transistor biased at 20mA, 20V, it has the h-parameters at room temperature $h_{ie}=500\Omega$, $h_{fe}=100$, $h_{re}=10^{-4}$, $h_{oe}=4\times 10^{-5}\Omega$. It has $f_T=50\text{MHz}$ and $C_C=3\text{pF}$. Find all the values of hybrid π components.
- b) The 3-db bandwidth of an amplifier extends from 20 Hz to 20 kHz. Find the frequency range over which the voltage gain differs by only 1 dB from the mid band value. [5+5]

OR

- 5.a) The amplifier of figure 2 uses a FET with $I_{DSS}=3\text{mA}$, $V_p=-3\text{V}$, $r_d \gg R_d$. Find the quiescent drain current, quiescent drain to source voltage and A_v .

 


Figure: 2

- b) Derive the equation for voltage gain of a CS FET amplifier. [5+5]
- 6.a) An amplifier has an open loop voltage gain of 1000 and delivers 10W output with 10% second harmonic distortion when the input is 10mV. Find the distortion of 60dB of negative feedback is applied.
- b) Calculate $A_{vf} = V_o/V_s$, R_{if} and R_{of} for the circuit shown in figure 3 use typical h parameter values. $R_s=R_C=10\text{K}$ and $R_e=1\text{K}$. [5+5]

 


Figure: 3

OR

- 7.a) Derive an expression for frequency of oscillations of a RC phase shift oscillator using transistor.
- b) A colpitts oscillator is designed with $C_1 = 100\text{pF}$ and $C_2=7500\text{pF}$. Find the range of inductance values if the frequency of oscillations vary between 950 and 2050KHz. [5+5]

- 8.a) Classify amplifiers based on operating point selection. Compare them in terms of efficiency and distortion.
- b) A transformer coupled class A large signal amplifier has maximum and minimum values of collector-to-emitter voltage of 25V and 2.5V. Determine its collector efficiency. [5+5]

OR

- 9.a) What is push pull configuration and how does this circuit reduce the harmonic distortion?
- b) Given an ideal class B Push Pull amplifier whose collector supply voltage is V_{cc} , and $R_L' = n^2 R_L$ are fixed as base current excitation is varied, show that the collector dissipation P_c is zero at no signal, rises as V_m increases and passes through a maximum at $V_m = 2V_{cc}/\pi$. [5+5]

10. Draw the circuit diagram of double tuned amplifier and explain its working and derive the equation for bandwidth. [10]

OR

- 11.a) How to reduce the instability in tuned amplifier? Explain them with neat circuit diagram.
- b) What are the advantages of stagger tuned amplifier? Draw its frequency response. [5+5]

---ooOoo---

Code No: 124CV

R15

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, December - 2018

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- 1.a) How the amplifiers are classified? [2]
- b) State and prove Miller's theorem. [3]
- c) What is gain bandwidth product? [2]
- d) Why emitter bypass capacitor is needed? [3]
- e) How the stability of amplifier will affect by negative feedback amplifier? [2]
- f) State the necessary conditions for oscillator. [3]
- g) Define conversion efficiency of power amplifiers. [2]
- h) How is crossover distortion eliminated in class AB amplifier? [3]
- i) What are the applications of tuned amplifier? [2]
- j) What is the coefficient coupling in a double tuned amplifier? [3]

PART-B

(50 Marks)

- 2.a) Draw the equivalent circuit for the CE and CC configurations subject to the restriction that $R_L = 0$. Show that the input impedance of the two circuits are identical.
- b) The transistor amplifier shown in figure 1 uses a transistor with typical h parameter values. Calculate A_i , A_v , A_{v_s} , R_o and R_i . [5+5]

 


Figure: 1

OR

- 3.a) Draw the circuit diagram of Darlington emitter follower and derive the expression for input impedance.
- b) Explain the working of cascade amplifier with neat circuit diagram. [5+5]

- 4.a) Draw the hybrid π equivalent circuit of a transistor in CE configuration and explain the various parameters in it.
- b) A transistor biased at 5mA, 10V, $h_{ie}=600\Omega$, $h_{fe}=100$, $C_C=3pF$ and current gain of 10 at a frequency of 20MHz. Find β cut off frequency, gain band width product, C_e , $r_{b'e}$ and $r_{bb'}$ [5+5]

OR

- 5.a) Calculate the voltage gain of the FET amplifier shown in the figure 2. Assuming blocking capacitor to be large. $g_m=4mA/V$ and $r_d=5K$.

 


Figure: 2

- b) Sketch the small signal model of a CD FET amplifier and derive equation for the voltage gain. [5+5]
- 6.a) Draw the negative feedback topologies and explain them.
- b) An open loop amplifier has a midband gain of 500 and a pass band from 50Hz to 50KHz. Find voltage gain and cut off frequencies if 10% of output voltage is fed back. [5+5]

OR

7. Derive an expression for frequency of oscillations of a wien bridge oscillator using transistor. [10]
- 8.a) Explain how the efficiency of the class A power amplifier is improved by the transformer coupled amplifier configuration?
- b) A transformer coupled class A power amplifier supplies the power to an 80Ω load connected across the secondary of a transformer having turns ration of 5:1. If $I_c=120mA$, find maximum output power? [6+4]

OR

- 9.a) Derive an equation of output power of a class B power amplifier.
- b) Draw the circuit diagram of complementary symmetry class B pushpull amplifier and explain its working. [5+5]
- 10.a) Why is double tuning employed in tuned amplifier? What are the advantages of it?
- b) What are applications of stagger tuned amplifier? [5+5]

OR

- 11.a) What are the high frequency limitations of a tuned amplifier? How are they eliminated?
- b) How is the bandwidth of tuned amplifier improved? Draw such a circuit and explain its working. [5+5]

---ooOoo---

Code No: 154AW

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year II Semester Examinations, November/December - 2020

ELECTRONIC CIRCUIT ANALYSIS


(Common to ECE, EIE)

Time: 2 Hours

Max. Marks: 75

**Answer any Five Questions
All Questions Carry Equal Marks**

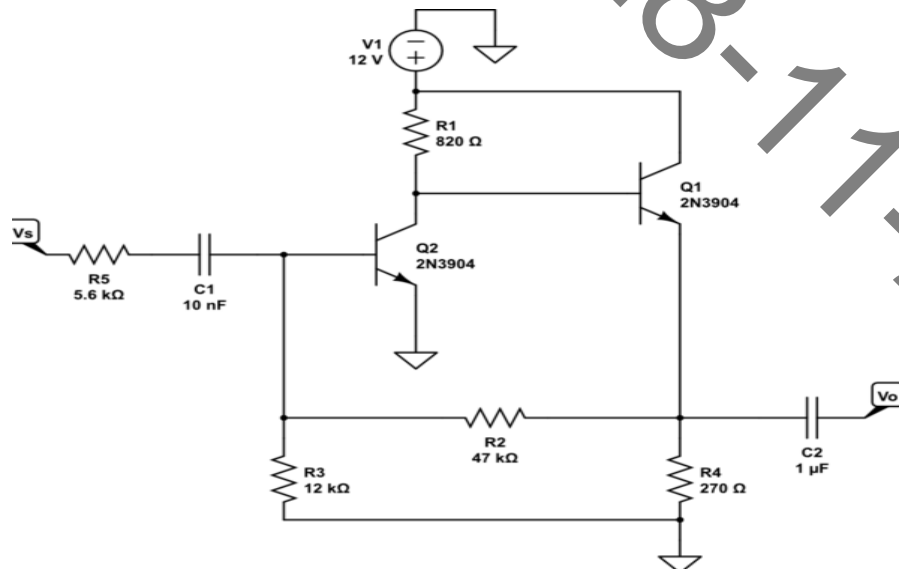- 1.a) Derive the upper and lower cutoff frequencies of the common emitter amplifier.
b) Why 3dB frequency for the current gain is not same as the 3dB frequency for voltage gain? [9+6]
- 2.a) The bandwidth of a single stage amplifier extends from 10Hz to 100kHz. Find the frequencies at which the voltage gain is down by 1dB from its mid-band value.
b) Draw the circuit diagram of Darlington pair and explain how it provides high input impedance. [6+9]
- 3.a) A voltage amplifier is characterized by an open loop voltage gain of 100. Input resistance of $50K\Omega$ and output resistance of $2K\Omega$, Negative feedback of 10% of output voltage is introduced in series with the input to bring the distortion below acceptable level. Find the modified values of these parameters.
b) Draw the current shunt feedback circuit diagram. [8+7]
4. Determine the feedback factor, current gain, voltage gain, input and output impedances for the following circuit. Assume ideal h parameters for the transistors. [15]



5. Derive the expression for the phase shift as a function of frequency for the feedback network of RC phase shift oscillator. [15]

- 6.a) How does the frequency stability of an LC oscillator depend upon the Q-factor of the LC circuit? Explain.
- b) Determine the minimum amplifier gain and the phase shift required to be introduced by the amplifier for the following case: Feedback factor = 2%, oscillator type is Hartley oscillator. [8+7]
- 7.a) A class B amplifier provides a 15V peak output signal to 10Ω load. The system operates on a power supply of 20V. Determine the efficiency of the amplifier.
- b) Draw the circuit diagram of push-pull class-B power amplifier and explain its working. [7+8]
- 8.a) Define the terms slope error, displacement error, transmission error.
- b) With the help of circuit diagram explain the principle of operation of a constant current sweep circuit. [7+8]

---ooOoo---

R13**Code No: 114DN****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, October/November - 2016****PULSE AND DIGITAL CIRCUITS****(Common to ECE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) What do you mean by linear network? [2]
- b) Why RC circuits are commonly used compared to RL circuits. [3]
- c) Distinguish between comparators and clipping circuits. [2]
- d) What do you mean by double ended clipper? [3]
- e) How does diode acts as a switch? [2]
- f) What do you mean by turn ON time of a transistor? [3]
- g) What are the applications of Schmitt trigger? [2]
- h) What are the applications of time-base generators? [3]
- i) What do you mean by synchronization? [2]
- j) Name the technologies which use bipolar transistors. [3]

PART - B**(50 Marks)**

- 2.a) Prove that for any periodic input waveform the average level of the steady state output signal from the RC high pass circuit is always zero.
- b) Derive an expression for the rise time of the output of a low pass RC circuit excited by a step input. [5+5]

OR

- 3.a) Prove that a low pass RC circuit with a large time constant acts as an integrator.
- b) Derive the expression for percentage tilt of a square wave output of RC high pass circuit. [5+5]

- 4.a) Draw the basic circuit diagram of negative peak clamper circuit and explain its operation.
- b) With help of a neat circuit diagram explain the working of a two – level diode clipper. [5+5]

OR

- 5.a) State and prove clamping circuit theorem.
- b) Write short notes on transistor clippers. [5+5]

- 6.a) Explain the operation of transistor switch in saturation.
b) For a common emitter amplifier, $V_{cc} = 15V$, $R_c = 1.5k\Omega$ and $I_B = 0.3 \text{ mA}$. Determine the value of $h_{FE(min)}$ for saturation to occur, if R_c is changed to 500Ω will the transistor be saturated. [5+5]

OR

- 7.a) With the help of a neat circuit diagram and waveforms, explain the operation of Four diode sampling gate.
b) With the help of a neat circuit diagram and waveforms, explain the operation of Six diode sampling gate. [5+5]

- 8.a) Explain the operation of fixed-bias binary with a triggering circuit and waveforms.
b) Design a Schmitt trigger circuit to have $UTP=6V$ and $LTP=3V$ using silicon Transistor Whose $h_{FE(min)}=40$. Assume necessary data. [5+5]

OR

- 9.a) Draw the circuit diagram of Bootstrap time base generator and explain its operation with necessary waveforms.
b) Compare the voltage and current time base generators with some examples. [5+5]
- 10.a) Illustrate the terms synchronization and frequency division of a sweep generator.
b) With the help of neat waveforms explain sine wave frequency division with a sweep circuit. [5+5]

OR

- 11.a) With a neat circuit diagram explain the operation of a TTL tristate output.
b) With the help of neat circuit diagram and truth table explain
(i) RTL OR gate
(ii) RTL AND gate. [5+5]

Code No: 114DN**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, May - 2015****PULSE AND DIGITAL CIRCUITS****(Common to ECE, BME)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

Part- A**(25 Marks)**

- 1.a) Define rise time. [2M]
- b) Draw and briefly explain the RC differentiator circuit. [3M]
- c) What is meant by clipping in wave shaping? [2M]
- d) Explain Clipping at two independent levels with circuit. [3M]
- e) Compare unidirectional and bi-directional Sampling Gates. [2M]
- f) Draw the Piecewise Linear Diode Characteristics. [3M]
- g) Write a basic principle of time base generator. [2M]
- h) Write the Methods of Generating Time Base Waveform. [3M]
- i) Define positive and negative logic systems. [2M]
- j) List out the applications of sweep circuits. [3M]

Part-B**(50 Marks)**

2. Draw the output of the low pass RC circuit for different time constant to
 - a) Pulse input.
 - b) Step voltage input. [5+5]

OR

- 3.a) Prove that for any periodic input waveform the average level of the steady state output signal from RC high pass circuit is always zero.
- b) Draw and explain the response of RLC circuit for step input. [5+5]

4. Classify different types of clipper circuits. Draw their circuits and explain their operation and also transfer characteristics. [10]

OR

- 5.a) State and prove clamping circuit theorem.
- b) Explain negative peak clipper with and without reference voltage. [5+5]

- 6.a) Explain the operation of linear bidirectional sampling gate using transistors.
- b) Explain in detail the junction diode switching times. [5+5]

OR

- 7.a) Explain about basic operation principles of sampling gates.
- b) Write the advantages and disadvantages of unidirectional diode gate. [5+5]

8. Explain with neat diagram the following methods of linearizing a voltage sweep.

a) Miller Sweep

b) Bootstrap sweep.

Compare their merits and limitations.

[5+5]

OR

9. Draw and explain the working principle of bistable multivibrator circuit and also explain the merits and limitations of it. [10]

10.a) Explain about DTL NAND gate.

b) Distinguish between voltage and current sweep circuit.

[4+6]

OR

11. Draw the circuit of a linear current sweep and explain its operation with wave forms. Explain the necessity of generating trapezoidal wave form. [10]

--ooOoo--

Code No: 114DN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, May - 2017

PULSE AND DIGITAL CIRCUITS

(Common to ECE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**


- 1.a) Obtain the response of high pass RC circuit for a ramp input. [2]
- b) Define % tilt of RC circuit. [3]
- c) Write the applications of voltage comparator. [2]
- d) Draw Negative biased Negative clipper circuit. [3]
- e) Draw the piecewise linear diode characteristics. [2]
- f) When transistor acts as a switch? [3]
- g) Define multivibrator. [2]
- h) Compare different multivibrators. [3]
- i) Explain the frequency division in the sweep circuit. [2]
- j) Define positive and negative logic systems. [3]

PART-B**(50 Marks)**

2. Draw the output of the low pass RC circuit for different time constant to:
 - a) Pulse input
 - b) Step input. [10]

OR

- 3.a) Derive the expression for percentage tilt for a square wave output of RC high pass circuit.
- b) A symmetrical square wave whose peak to peak amplitude is 2μ and whose average value in zero is applied to an RC integrator circuit. The time constant is equal to half the period of square wave, find the peak to peak value of output amplitude. [6+4]
- 4.a) Draw the circuit diagram of a DC restorer circuit with and without reference voltage and explain its operation for a sinusoidal input signal.
- b) Explain the operation of the following double diode clipper and sketch the output waveform for a sinusoidal input shown in figure. [5+5]

 **OR**

- 5.a) State and prove clamping circuit theorem.
- b) Explain negative peak clipper with and without reference voltage. [5+5]

- 6.a) Explain the operation of linear bidirectional sampling gate using transistor. [6+4]
 b) Explain in detail the junction diode switching times. **OR**
- 7.a) Explain with relevant diagram the various transistor switching times.
 b) For a CE circuit $V_{CC} = 10V$, $R_C = 1K\Omega$, $I_B = 0.2A$. Determine
 i) The value of $h_{fe(min)}$ for saturation to occur.
 ii) If R_C is change to 220Ω , will the transistor be saturated? [5+5]
- 8.a) Draw the circuit of a self biased transistor binary and develop the design and steps of analysis.
 b) For a mono stable vibrator calculate the input pulse width for the design values of $R_C = 2k\Omega$, $R_B = 10K\Omega$, $C = 0.1\mu F$, $V_{CC} = 10V$ and $V_{BE(Sat)} = 0.8V$. [5+5] **OR**
9. Draw and explain the working principle of astable multivibrator circuit and also explain the merits and limitations of it. And also derive the expression for its pulse width. [10]
10. Discuss in detail the sine wave frequency division with a sweep circuit. [10] **OR**
11. Draw and explain 2-input NAND gate with functional table. [10]

---ooOoo---

Code No: 114DN**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, May - 2016****PULSE AND DIGITAL CIRCUITS****(Common to ECE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) Why does resistive attenuator need to be compensated. [2]
- b) Derive an expression for the output of a high-pass circuit excited by a ramp input. [3]
- c) Draw the basic circuit diagram of negative peak clamper circuit. [2]
- d) Explain the working of an emitter coupled clipper. [3]
- e) Explain the effect of pedestal in gate circuit. [2]
- f) Explain the variation of saturation parameters of transistor with temperature? [3]
- g) Define UTP and LTP. [2]
- h) Write the difference between current time base generator and voltage time base generators. [3]
- i) Draw the diagram of OR gate using diodes. [2]
- j) Explain the principle of synchronization. [3]


PART - B**(50 Marks)**

- 2.a) A symmetrical square wave whose peak-to-peak amplitude is 8V and whose average value is zero is applied to an RC integrating circuit. The time constant is equal to half -period of the square wave. Find the peak to peak value of the output amplitude.
- b) Explain the working of high-pass RC circuit as a differentiator. [5+5]

OR

- 3.a) Derive the expression for rise time of integrating circuit and prove that it is proportional to time constant and inversely proportional to upper 3 dB frequency.
- b) Draw the response of the circuit for step input critically damped and over damped cases for a fixed value of R and C. [5+5]

 - 4.a) For the circuit shown in figure, an input voltage V_i linearly varies from 0 to 120 V is applied. Sketch the output voltage V_o to the same time scale. (Assume ideal diodes).



- b) State and prove the clamping circuit theorem. [5+5]

OR

- 5.a) Classify different types of clipper circuits. Give their circuits and explain their operation with the aid of transfer characteristics.
- b) Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. [7+3]
- 6.a) Write a short note on switching times of a transistor.
- b) With the neat circuit diagram, explain the operation of unidirectional sampling gate for multiple inputs. [5+5]

OR

- 7.a) Discuss in detail about breakdown voltages of a transistor.
- b) Illustrate the errors encountered in series sampling and what is the design procedure to minimize these errors? [5+5]
- 8.a) With the help of neat circuit diagram and waveform, explain the principle of operation of collector coupled monostable multivibrator.
- b) Explain how the deviation from linearity is expressed in terms of errors. [6+4]

OR

- 9.a) With the help of a neat circuit diagram and waveforms, explain the working of a transistor bootstrap time base generator.
- b) What is hysteresis? Explain how hysteresis can be eliminated in a Schmitt trigger? [6+4]

- 10.a) Explain working of monostable relaxation device as a divider.
- b) Why totem pole is used in DTL? Draw the circuit diagram and explain a DTL NAND gate with this. [5+5]

OR

- 11.a) What is phase jitter? How to reduce it in frequency division?
- b) Draw and explain a diode AND circuit for negative logic and how it works. And how an OR circuit acts as a buffer circuit? [5+5]

--ooOoo--